

邹佳驹 4班  
12012127

# 《Fundamentals of Electric Circuits》 homework 3

4.14 Apply the superposition principle to find  $v_o$  in the circuit of Fig. 4.82. (10')

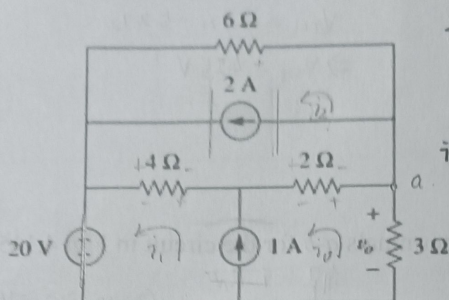


Figure 4.82

4.24 Use source transformation to find the voltage  $V_x$  in the circuit of Fig. 4.92. (10')

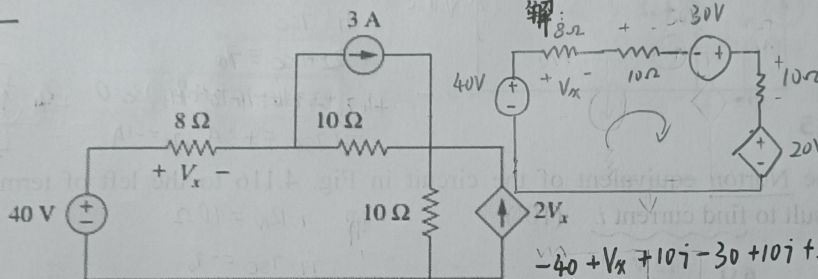


Figure 4.92

4.44 For the circuit in Fig. 4.111, obtain the Thevenin equivalent as seen from terminals:

(a) a-b (b) b-c. (10')

a):

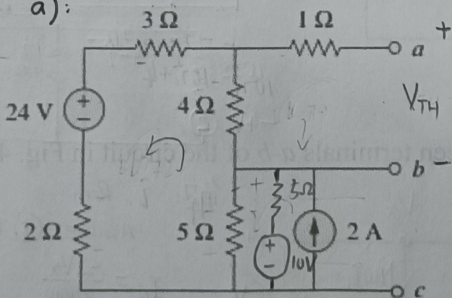


Figure 4.111

4.X Find the Thevenin equivalent at terminals a-b of the circuit in Fig. 4.x. (10')

解:  
i. 保留  $\oplus 20V$   
 $V_o = 3 \times \frac{20}{6 \parallel 6 + 3} = 10V$  □

ii. 保留  $\leftarrow 2A$

$$+2 + i + i + 2i = 0 \Rightarrow i = -0.5A$$

$$V_o = 3 \times 2 \times (-0.5) = -3V$$
 □

iii. 保留  $\uparrow 1A$

$$i_1 - i_0 = 1A$$

$$6i_2 + 4(i_2 - i_1) + 2(i_2 - i_0) = 0$$

$$4(i_1 - i_2) - V_o + 2(i_0 - i_2) = 0$$

$$V_o = -3i_0$$

$$\Rightarrow V_o = +1V, i_0 = -\frac{1}{3}A$$

$$\therefore V_o = 10 - 3 + 1 = 8V$$

$$-40 + V_x + 10i_1 - 30 + 10i_1 + 20V_x = 0$$

$$\Rightarrow V_x = \frac{140}{47} V = 2.979 V$$

$$\frac{V_x}{8} = i$$

解: a) i.  $R_{TH} = 1 + 10 \parallel 4 = \frac{34}{14} = \frac{17}{7} \Omega$

ii.  $V_{TH}$  ?

$$+24 + 2i - 10 + 5i + 4i + 3i = 0, i = -1A$$

$$V_{TH} = -i \cdot 4 = 4V$$

b) i.  $R_{TH} = 5 \parallel (3 + 4 + 2) = \frac{45}{14} \Omega$

ii.  $V_{TH}$

$$+24 + 2i - 10 + 5i + 4i + 3i = 0, i = -1A$$

$$V_{TH} = 10 + 5(-1) = 5V$$



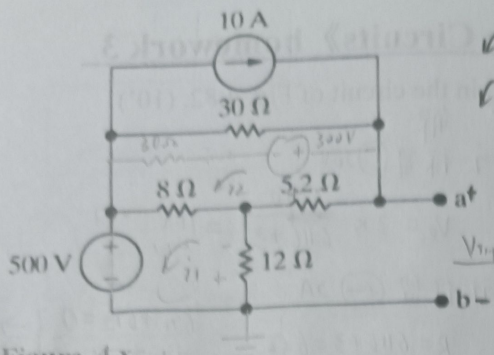


Figure 4.115

4.48 Determine the Norton equivalent at terminals  $a-b$  for the circuit in Fig. 4.115. (10')

解: i.  $R_{TH} = 30 \parallel (8 \parallel (12 + 5.2)) = 7.5 \Omega$

ii.  $V_{TH}$

$$\begin{aligned} i_1: & +500 + 12i_1 + 8(i_1 - i_2) = 0 \\ i_2: & +300 + 30i_2 + 8(i_2 - i_1) + 5.2i_2 = 0 \end{aligned} \quad \left. \begin{aligned} i_1 &= -30A \\ i_2 &= -12.5A \end{aligned} \right\}$$

$$V_{TH} = -12i_1 - 5.2i_2$$

$$\Rightarrow V_{TH} = 425V$$

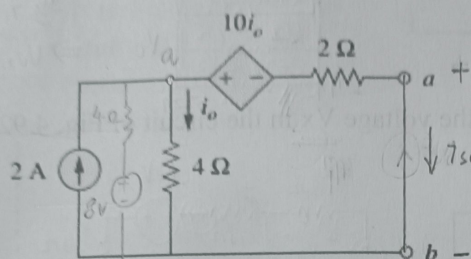


Figure 4.116

4.50 Obtain the Norton equivalent of the circuit in Fig. 4.116 to the left of terminals  $a-b$ . Use the result to find current  $i$ . (10')

解: i.  $R_N$

Assume  $\uparrow 1A \Rightarrow i_0 = 1A$

$$2 - 10 + 4 + 8 - V_{ab} = 0, V_{ab} = 4V$$

$$R_{eq} = \frac{V_{ab}}{1} = 4\Omega$$

ii.  $i_{sc}$

$$+2 - i_{sc} = i_0$$

$$+4i_0 = +10i_0 + 2(1 + i_{sc})$$

$$\Rightarrow i_{sc} = +3A, i_0 = -1A$$

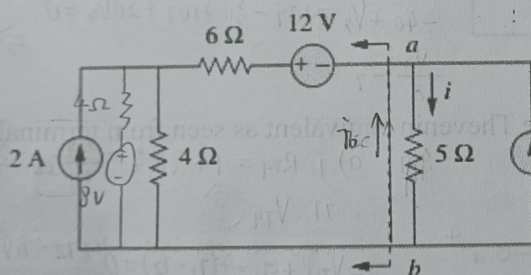
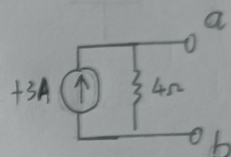



Figure 4.120

4.54 Find the Thevenin equivalent between terminals  $a-b$  of the circuit in Fig. 4.120. (10')

解: i.  $R_N = 10\Omega$

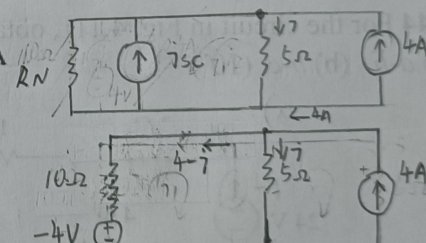ii.  $i_{sc} = -i_0$

$$-12 + 10i_0 + 8 = 0, i_0 = 0.4A, i_{sc} = -0.4A$$



$$5i = (-4) + 10(4 - i)$$

$$\Rightarrow i = 2.4A$$

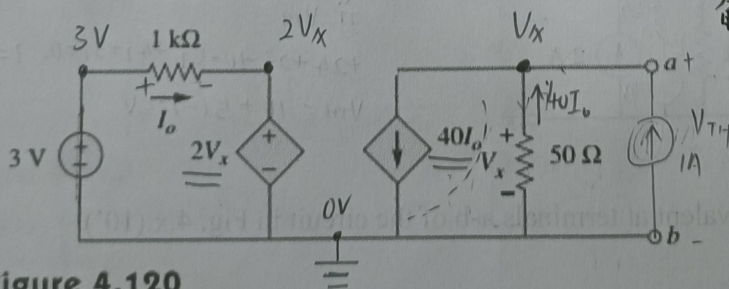


Figure 4.120

4.Y Determine the Norton equivalent at terminals  $a-b$  for the circuit in Fig. 4.120. (10')

解: i.  $R_{TH}$

Assume  $\uparrow 1A$

$$I_0 = \frac{-2V_x}{1000}$$

$$+1 - \frac{V_x}{50} - 40I_0 = 0 \Rightarrow V_{ab} = -\frac{50}{3}V$$

$$R_{TH} = \frac{+\frac{50}{3}}{+1} = \frac{50}{3}\Omega = 16.67\Omega$$

ii.  $V_{TH}$

$$I_0 = \frac{-2V_x}{1000}$$

$$40I_0 = \frac{-V_x}{50}$$

$$\Rightarrow V_x = 2V$$

$$V_{ab} = 2V = V_{TH}$$



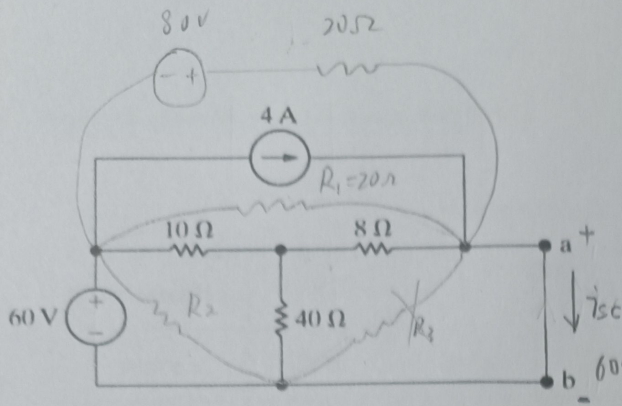


Figure 4.138

- 4.72 (a) For the circuit in Fig. 4.138, obtain the Thevenin equivalent at terminals a-b.  
 (b) Calculate the current in  $R_L = 8\Omega$ .  
 (c) Find  $R_L$  for maximum power deliverable to  $R_L$ .  
 (d) Determine that maximum power.

(10')

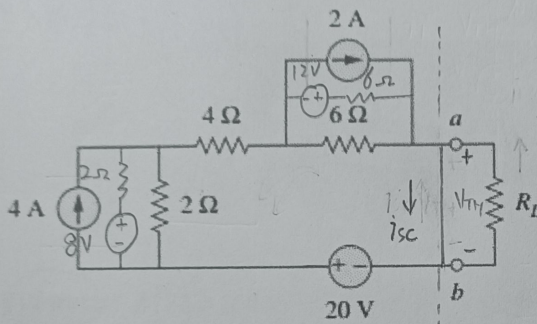


Figure 4.138

- 4.74 For the bridge circuit shown in Fig. 4.140, find the load  $R_L$  for maximum power transfer and the maximum power absorbed by the load. (10')

$i_{sc}$ ?

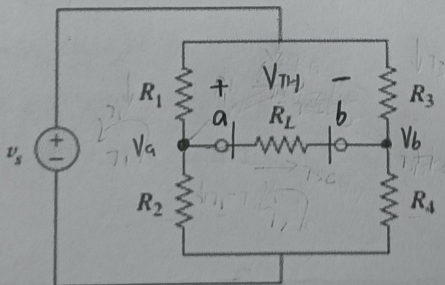



Figure 4.140

解:  $R_{TH} = R_1 \parallel R_2 + R_3 \parallel R_4$

$V_{TH} = i_{sc} \cdot R_{TH}$

$$\begin{cases} V_s + R_2(i_1 - i_3) + R_1(i_1 - i_2) = 0 \\ R_1(i_2 - i_1) + R_3 i_2 = 0 \\ R_2(i_3 - i_1) + R_4 i_3 = 0 \end{cases} \Rightarrow \begin{cases} i_1 = \frac{-V_s R_1 (R_2 + R_4)}{R_1 R_2 + R_3 R_4} \\ i_2 = \dots \\ i_3 = \dots \end{cases}$$

since we need to find  $R_L$

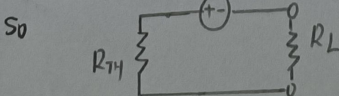

So


解: i.  $R_N = 8 + 10 \parallel 40 = 16\Omega$

ii.  $i_{sc}$


$R_1 = \frac{10 \times 40 + 40 \times 8 + 10 \times 8}{40} = 20\Omega$

$R_2 = \frac{800}{8} = 100\Omega$

$R_3 = \frac{800}{10} = 80\Omega$

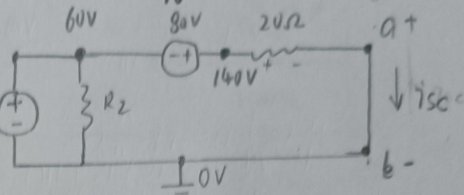

$i_{sc} = \frac{+140}{20} = 7A$

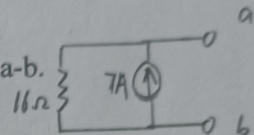


解:

a) i.  $R_{TH} = 2 + 4 + 6 = 12\Omega$

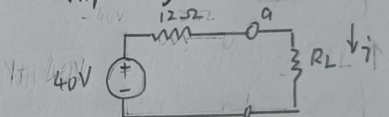ii.  $V_{TH} = i_{sc} \cdot R_{TH}$

$6i_{sc} - 12 + 4i_{sc} + 2i_{sc} - 8 - 20 = 0$   
 $i_{sc} = +\frac{10}{3} A$

$V_{TH} = +\frac{10}{3} \times 12 = +40V$



b)  $i = \frac{40}{12+8} = 2A$  c)  $P = R_L \left( \frac{40}{R_L+12} \right)^2$

$= \frac{1600}{R_L + 144 + 24}$   
 $= \frac{1600}{R_L + 168}$

当  $R_L = 12\Omega$  时,  $P_{max}$

d)  $P_{max} = \frac{1600}{12+12+24}$   
 $= \frac{100}{3} W = 33.33W$

load absorbed:  $P_L = R_L \left( \frac{V_{TH}}{R_{TH} + R_L} \right)^2$  ①

$= R_L \cdot \frac{V_{TH}^2}{R_{TH}^2 + R_L^2 + 2R_L \cdot R_{TH}}$

$= \frac{V_{TH}^2}{\frac{R_{TH}^2}{R_L} + R_L + 2R_{TH}}$  ,  $P_L \max$

$R_L = R_{TH} = R_1 \parallel R_2 + R_3 \parallel R_4$   
 $= \frac{R_1 R_2}{R_1 + R_2} + \frac{R_3 R_4}{R_3 + R_4}$

$V_{TH} = V_a - V_b$

$= \frac{V_s}{R_1 + R_2} \cdot R_1 - \frac{V_s}{R_3 + R_4} \cdot R_3 = V_s \left( \frac{R_1}{R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right)$

代入①式得:  $P_L = \frac{V_s^2 \cdot \left( \frac{R_1}{R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right)^2}{4 \left( \frac{R_1 R_2}{R_1 + R_2} + \frac{R_3 R_4}{R_3 + R_4} \right)}$