

# 《Fundamentals of Electric Circuits》 homework CH.13

13.14 Obtain the Thevenin equivalent circuit for the circuit in Fig. 13.83 at terminals a-b. (10')

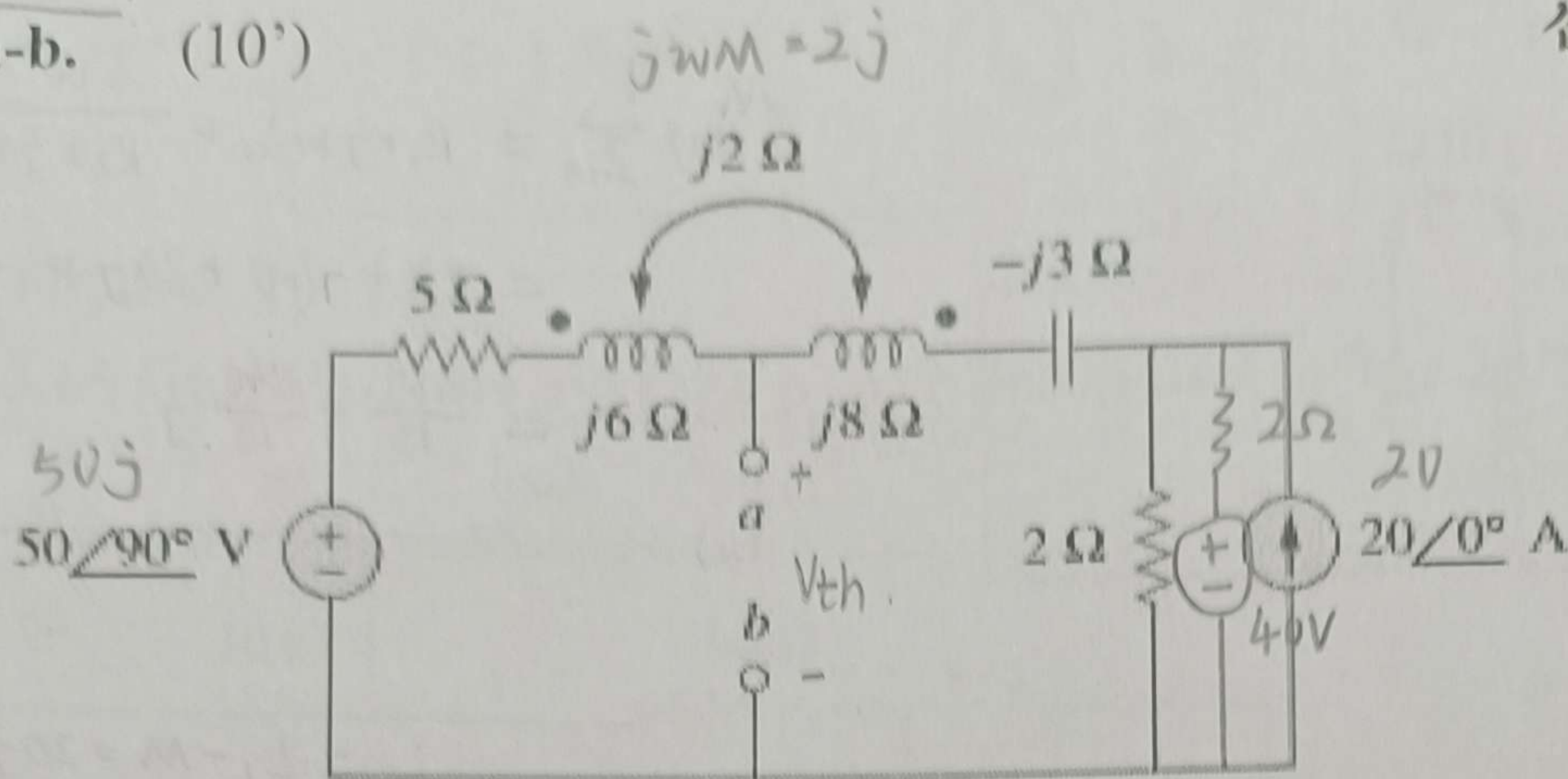


Figure 13.83

解: for the whole loop:  $I$


$$L_{eq} = L_1 + L_2 - 2M = 10j \Omega$$

$$-50j + (5 + 10j - 3j + 2)I + 40 = 0$$

$$I = \frac{5}{7} + \frac{45}{7}j$$

$$V_{th} - 50j + (5 + 6j)I - 2jI = 0$$
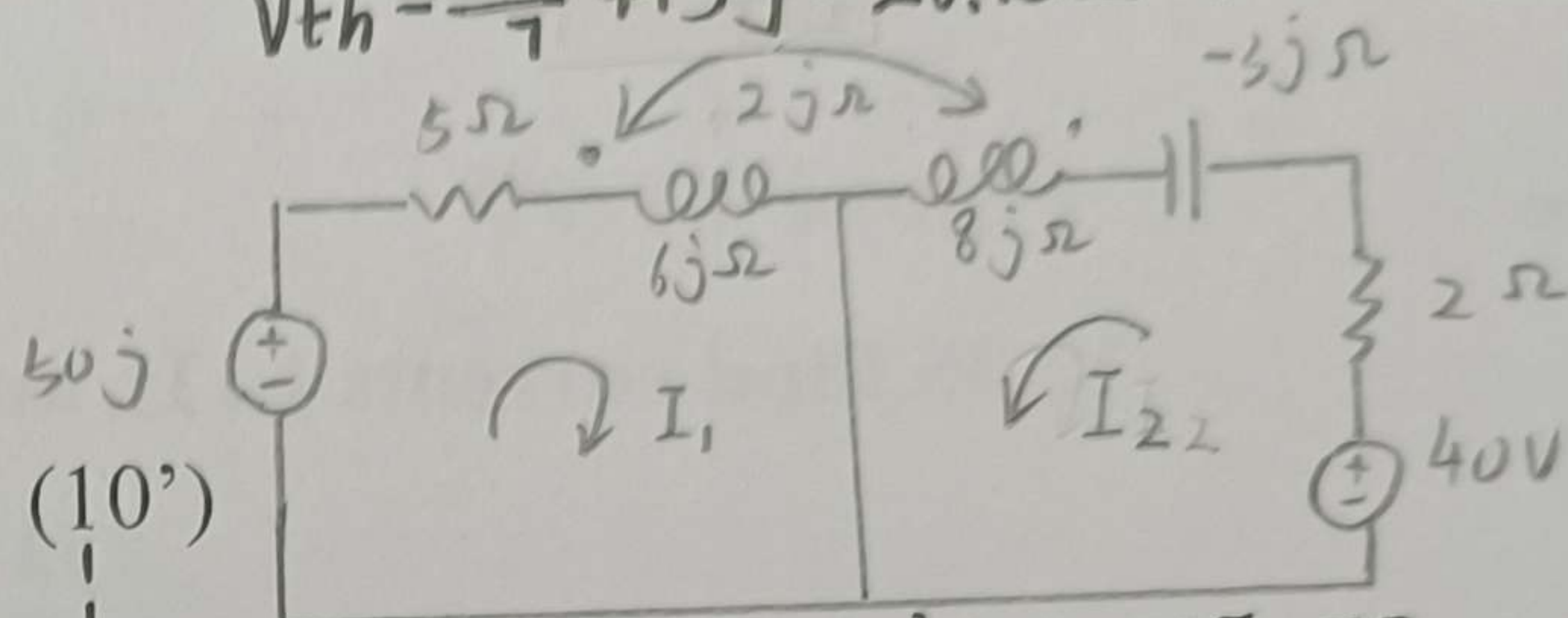
$$V_{th} = \frac{155}{7} + 15j = 26.75 \angle 34.11^\circ \quad \text{ANS}$$



13.25 For the network in Fig. 13.94, find  $Z_{ab}$  and  $I_o$ . (10')

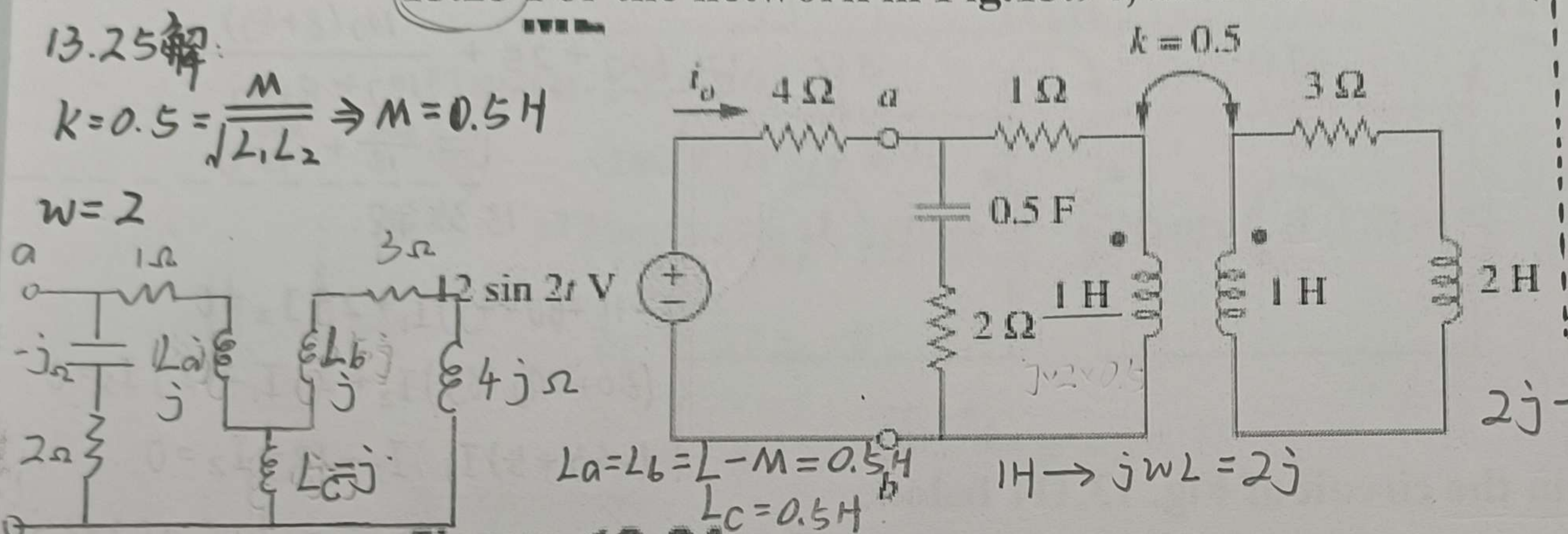


Figure 13.94

Loop 1:  $-50j + (5 + 6j)I_1 + 2jI_2 = 0$

Loop 2:  $-40 + (2 - 3j + 8j)I_2 + 2jI_1 = 0$

$$I_{ab} = I_1 + I_2 = \frac{1764}{325} - \frac{1202}{325}j$$

$$Z_{th} = \frac{V_{th}}{I_{ab}} = 1.5 + 3.786j = 4.072 \angle 68.39^\circ \quad \text{ANS}$$

13.28 In the circuit of Fig. 13.97, find the value of  $X$  that will give maximum power transfer to the 20-Ω load. (10')


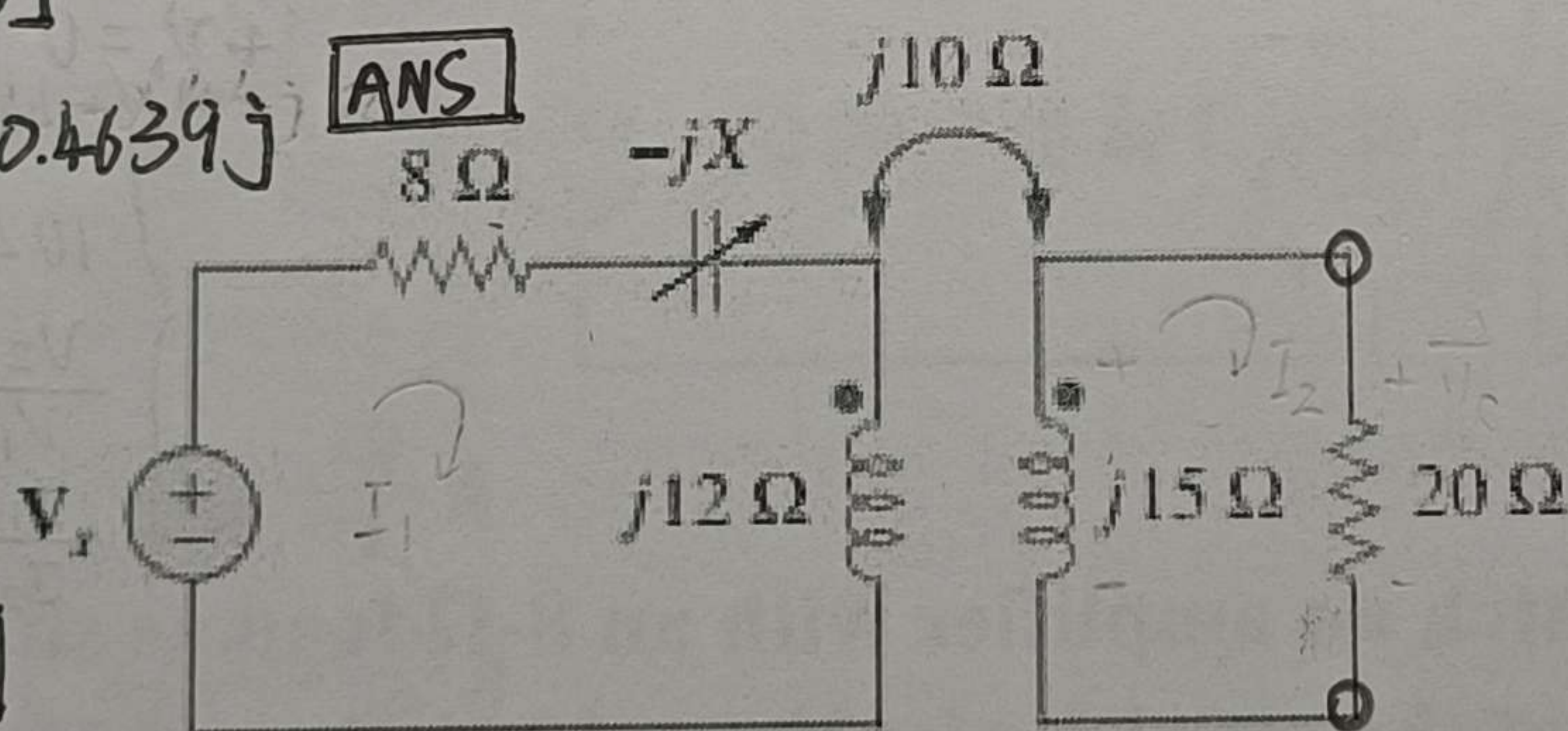


Figure 13.97

解: if  $|Z_{th}| = 20$ , we get  $\max P_L$

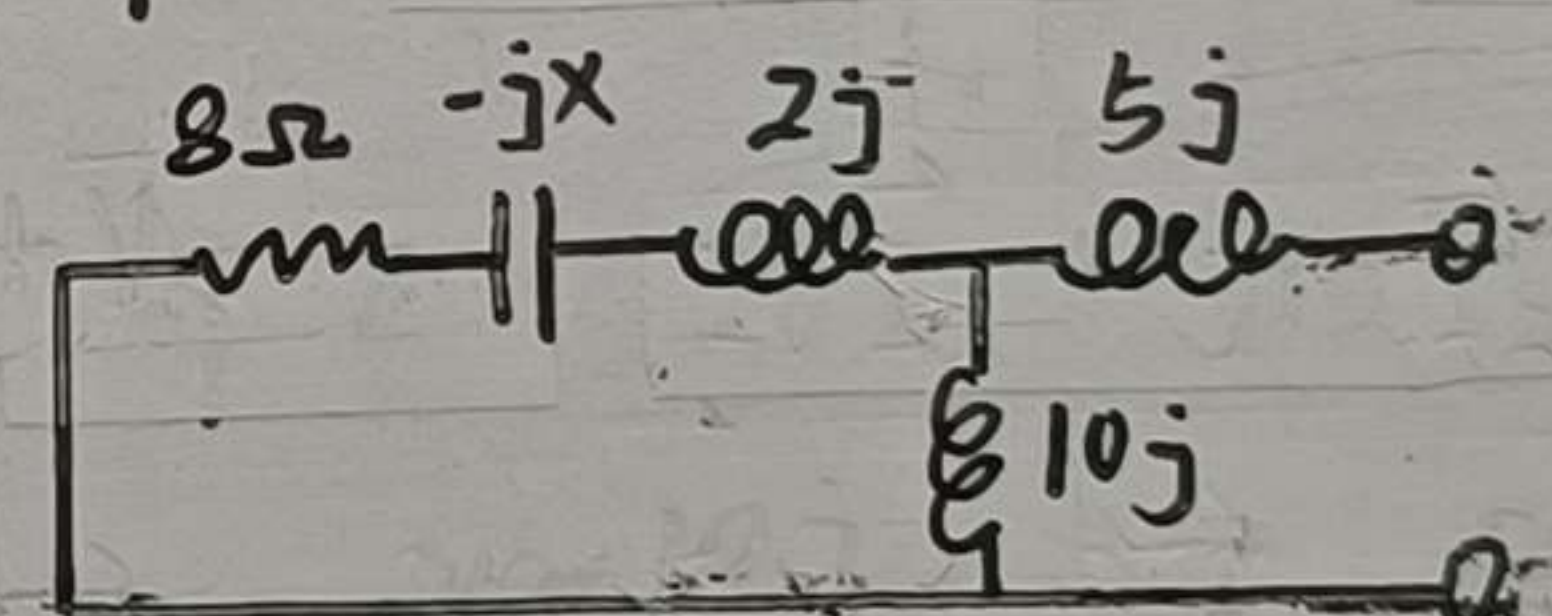

$$Z_{th} = [8 + (2 - X)j] \parallel j10j + 5j$$

$$= \frac{(15X - 80) + 120j}{8 + (12 - X)j}$$

$$\frac{(15X - 80)^2 + 120^2}{8^2 + (12 - X)^2} = 20^2 \Rightarrow X_1 = 28.73, X_2 = 12.41 \quad \text{ANS}$$

13.29 In the circuit of Fig. 13.98, find the value of the coupling coefficient  $k$  that will make the 10-Ω resistor dissipate 320 W. For this value of  $k$ , find the energy stored in the coupled coils at  $t = 1.5$  s. (10')

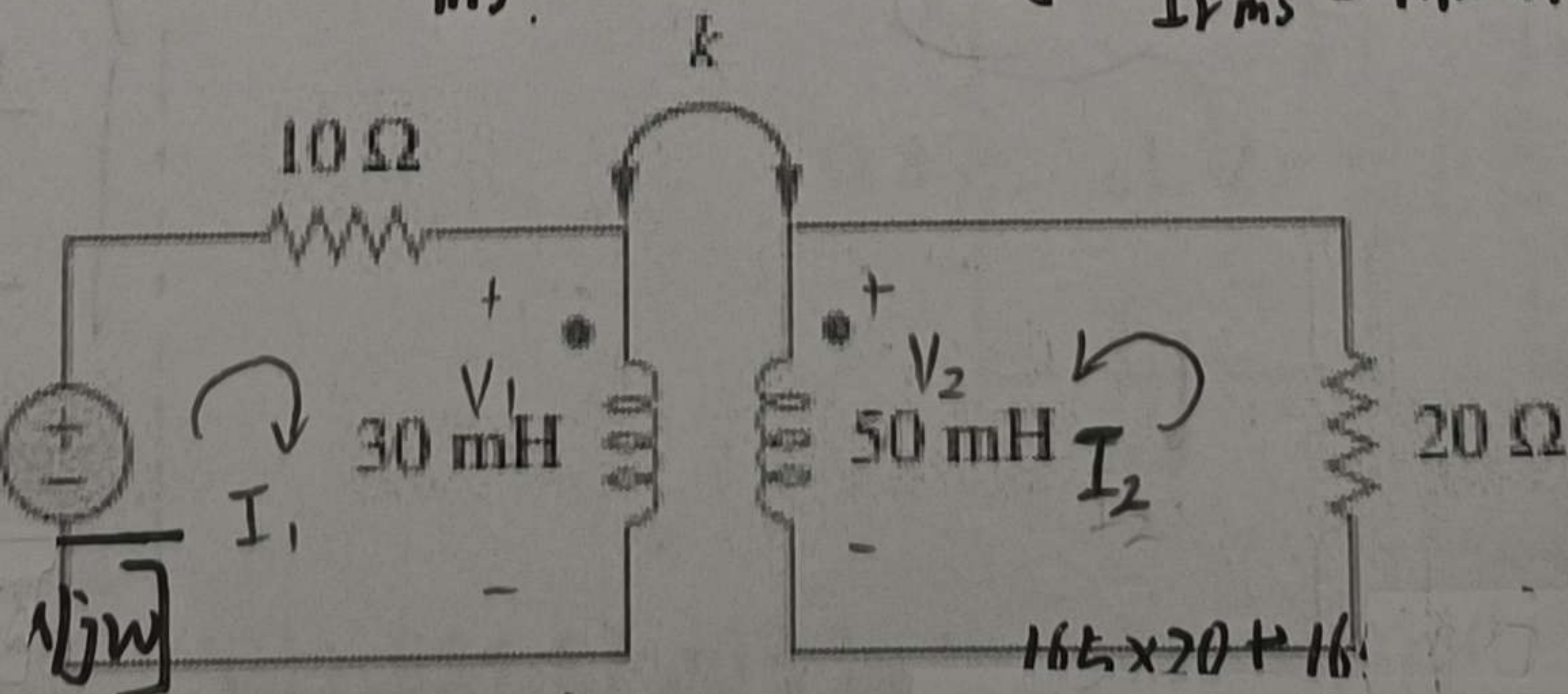


Figure 13.98

$$j\omega L_2 I_2 + j\omega M I_1 + 20 I_2 = 0$$

$$I_2 = \frac{-j\omega M I_1}{j\omega L_2 + 20}$$

$$= \frac{-j \times 38.73 \times 0.9845 \times (7.768 - 1.913j)}{j \times 50 + 20}$$

对  $I_1$  的求解

$$\Rightarrow k = 0.9845 \quad \text{ANS}$$

$$W = \frac{1}{2} L_1 I_1^2 + \frac{1}{2} L_2 I_2^2 + M I_1 I_2$$

$$I_1 = 7.768 - 1.913j = 8.00 \cos(\omega t - 13.83^\circ)$$

$$= -5.610 - 0.7851j = 5.665 \cos(\omega t - 172.0^\circ)$$

$$i_1 = 8 \cos(\frac{1.5 \times 180^\circ}{\pi} - 13.83^\circ) = 2.457 \text{ A}$$

$$i_2 = 5.665 \cos(\frac{1.5 \times 180^\circ}{\pi} - 172^\circ) = 0.3896 \text{ A}$$

$$W = 130.88 \text{ mJ} \quad \text{ANS}$$

13.29 解:

$$k = \frac{M}{\sqrt{L_1 L_2}} \Rightarrow M = 38.73 \text{ mH}$$

$$|I_1| = 8 \text{ A}, \omega = 1000 \text{ rad/s}$$

$$I_1 = \frac{V}{Z_{in}} = \frac{165 \angle 0^\circ}{10 + j30 + \frac{38.73^2 k^2}{20 + j50}}$$

$$= \frac{165(20 + 50j)}{(10 + 30j)(20 + 50j) + 38.73^2 k^2}$$

$$= \frac{165 \times 20 + 165 \times 50j}{(200 - 1500 + 38.73^2 k^2) + 1100j}$$

$$= \frac{(165 \times 20)^2 + (165 \times 50)^2}{(-1300 + 38.73^2 k^2)^2 + 1100^2} = 8^2$$



13.30 (a) Find the input impedance of the circuit in Fig.13.99 using the concept of reflected impedance.

(b) Obtain the input impedance by replacing the linear transformer by its T equivalent. (10')

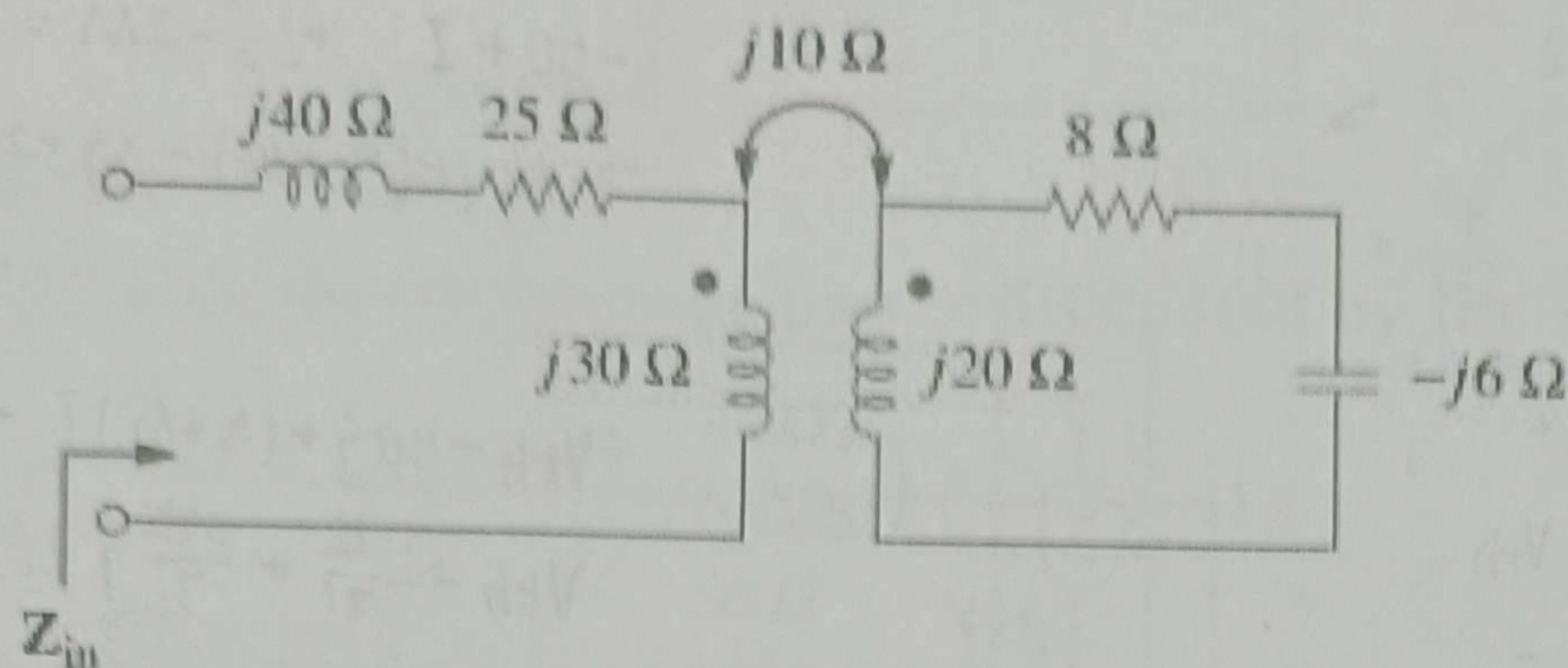



Figure 13.99

解:

$$a) \vec{Z}_{in} = R_1 + j\omega L_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$

$$= 25 + j40 + 30j + \frac{100}{8 - 6j + 20j}$$

$$= \frac{365}{13} + \frac{840}{13}j$$

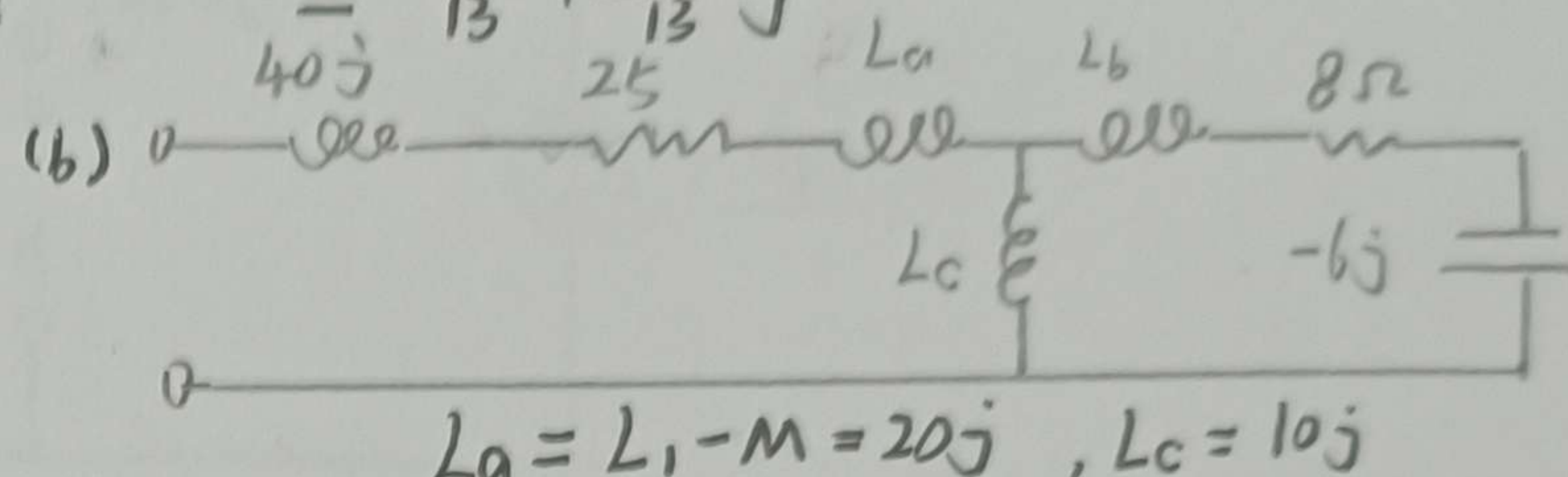

13.35 Find currents  $I_1$ ,  $I_2$ , and  $I_3$  in the circuit of Fig.13.104.

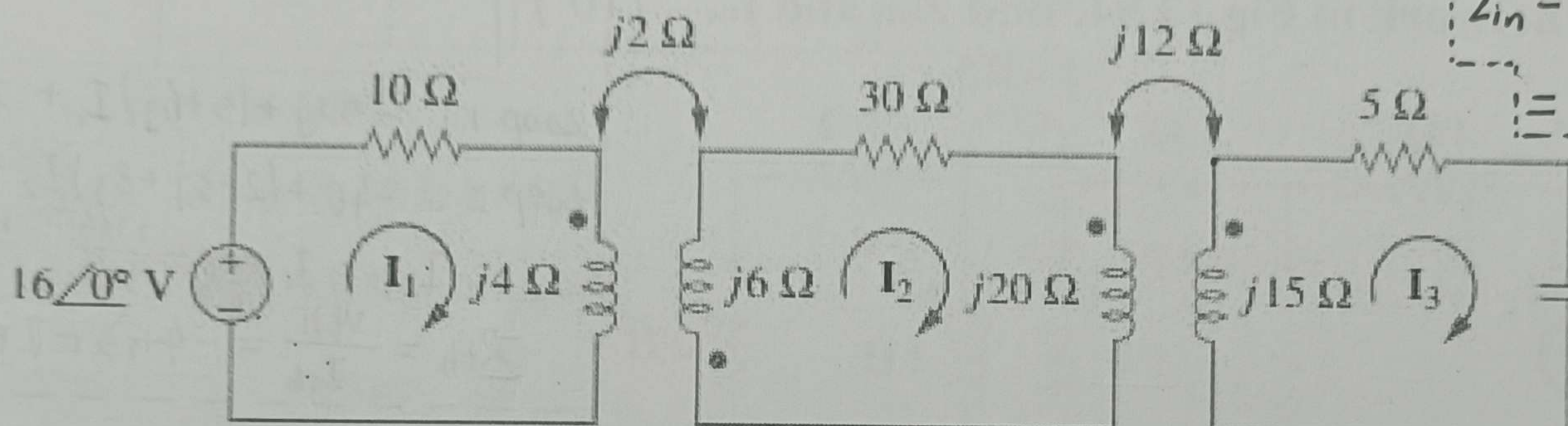


Figure 13.104

(10')

$$\vec{Z}_{in} = 40j + 25 + 20j + 10j \parallel (8 - 6j + 20j)$$

$$= 60j + 25 + \frac{10j(8 + 4j)}{10j + 8 + 4j}$$

$$= \frac{365}{13} + \frac{840}{13}j$$

13.46 (a) Find  $I_1$  and  $I_2$  in the circuit of Fig. 13.111 below.

(b) Switch the dot on one of the windings. Find  $I_1$  and  $I_2$  again. (10')

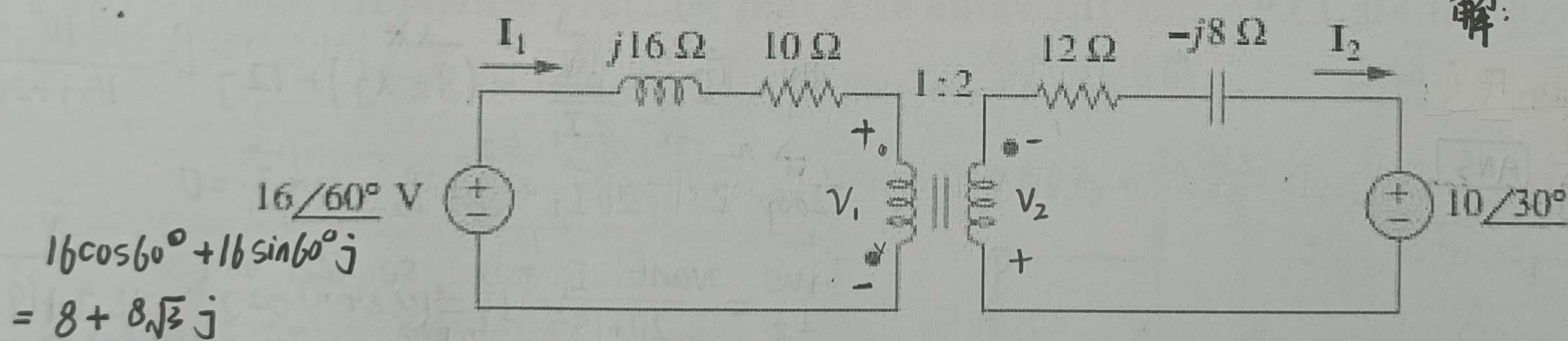


Figure 13.111

13.35 解:

$$\begin{cases} -16 + (10 + 4j)I_1 + 2jI_2 = 0 \\ (30 + 20j + 6j)I_2 + 2jI_1 - 12jI_3 = 0 \\ (5 - 4j + 15j)I_3 - 12jI_2 = 0 \end{cases}$$

13.46 解:

$$\begin{cases} I_1 = 1.374 - 0.5383j \\ I_2 = -0.0554 - 0.0557j \\ I_3 = -0.0272 - 0.0731j \end{cases}$$

13.54 A transformer is used to match an amplifier with an 8-Ω load as shown in Fig. 13.119. The Thevenin equivalent of the amplifier is:  $V_{Th} = 10$  V,  $Z_{Th} = 128$  Ω.  $\Rightarrow I_1 = 1.067 + 0.1096j$

(a) Find the required turns ratio for maximum energy power transfer.

(b) Determine the primary and secondary currents.

(c) Calculate the primary and secondary voltages. (10')

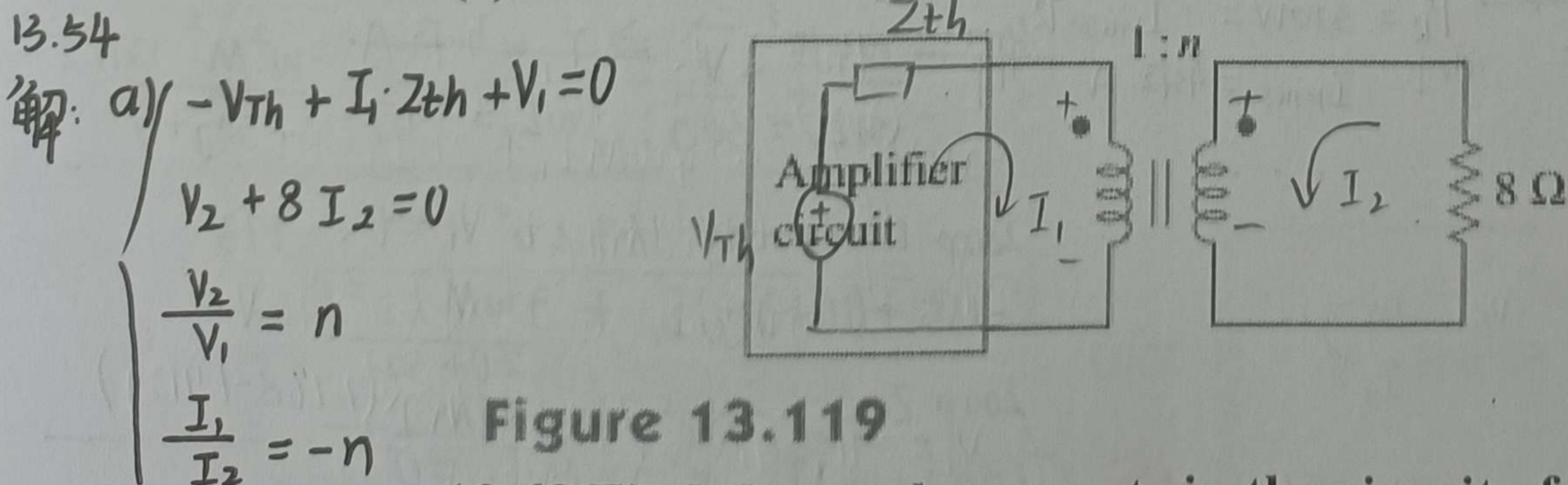


Figure 13.119

13.63 Find the mesh currents in the circuit of Fig. 13.128. (10')

$$\Rightarrow I_2 = \frac{-10}{128n + \frac{8}{n}}$$

$$I_2 \max \Rightarrow 128n = \frac{8}{n}$$

$$n = \frac{1}{4}$$

b)  $I_2 = \frac{-10}{64} = -\frac{5}{32} A$

$$I_1 = -\frac{1}{4} \times \frac{-10}{64} = \frac{5}{128} A$$

c)  $V_2 = -8I_2 = 1.25 V$

$$V_1 = 5 V$$

a)  $\begin{cases} -16\angle 60^\circ + (16j + 10)I_1 + V_1 = 0 \\ 10\angle 30^\circ + V_2 + (12 - 8j)I_2 = 0 \\ \frac{V_2}{V_1} = +n = 2 \\ \frac{I_1}{I_2} = -n = -2 \end{cases}$

b) Switch dot  $\Rightarrow \begin{cases} -16\angle 60^\circ + (16j + 10)I_1 + V_1 = 0 \\ 10\angle 30^\circ + V_2 + (12 - 8j)I_2 = 0 \\ \frac{V_2}{V_1} = -2 \\ \frac{I_1}{I_2} = 2 \end{cases}$

$$\Rightarrow I_1 = 0.5630 + 0.2637j = 0.63\angle 25^\circ$$

$$I_2 = 0.2831 + 0.1319j = 0.31\angle 25^\circ$$



13.63 解: 
$$\begin{cases} -12 \angle 0^\circ + I_1 + V_1 = 0 \\ +V_{21} + I_2(7 - j6) + V_{22} = 0 \\ +V_3 + I_3(9 + j18) = 0 \end{cases}$$

$$\frac{I_1}{I_2} = 2 \quad \frac{V_{21}}{V_1} = -2$$

$$\frac{I_2}{I_3} = -3 \quad \frac{V_3}{V_{22}} = 3$$

$$\Rightarrow \begin{cases} I_1 = 3.6 + j1.2 \\ I_2 = 1.8 + j0.6 \\ I_3 = 0.6 - j0.2 \end{cases}$$

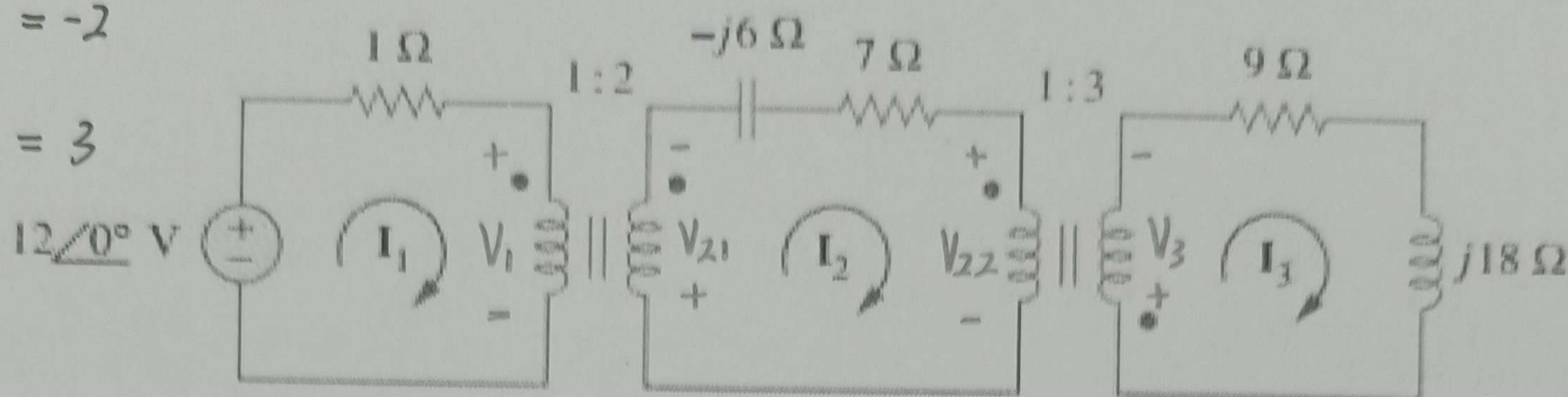


Figure 13.128

13.65 Calculate the average power dissipated by the 20-Ω resistor in Fig. 13.130. (10')

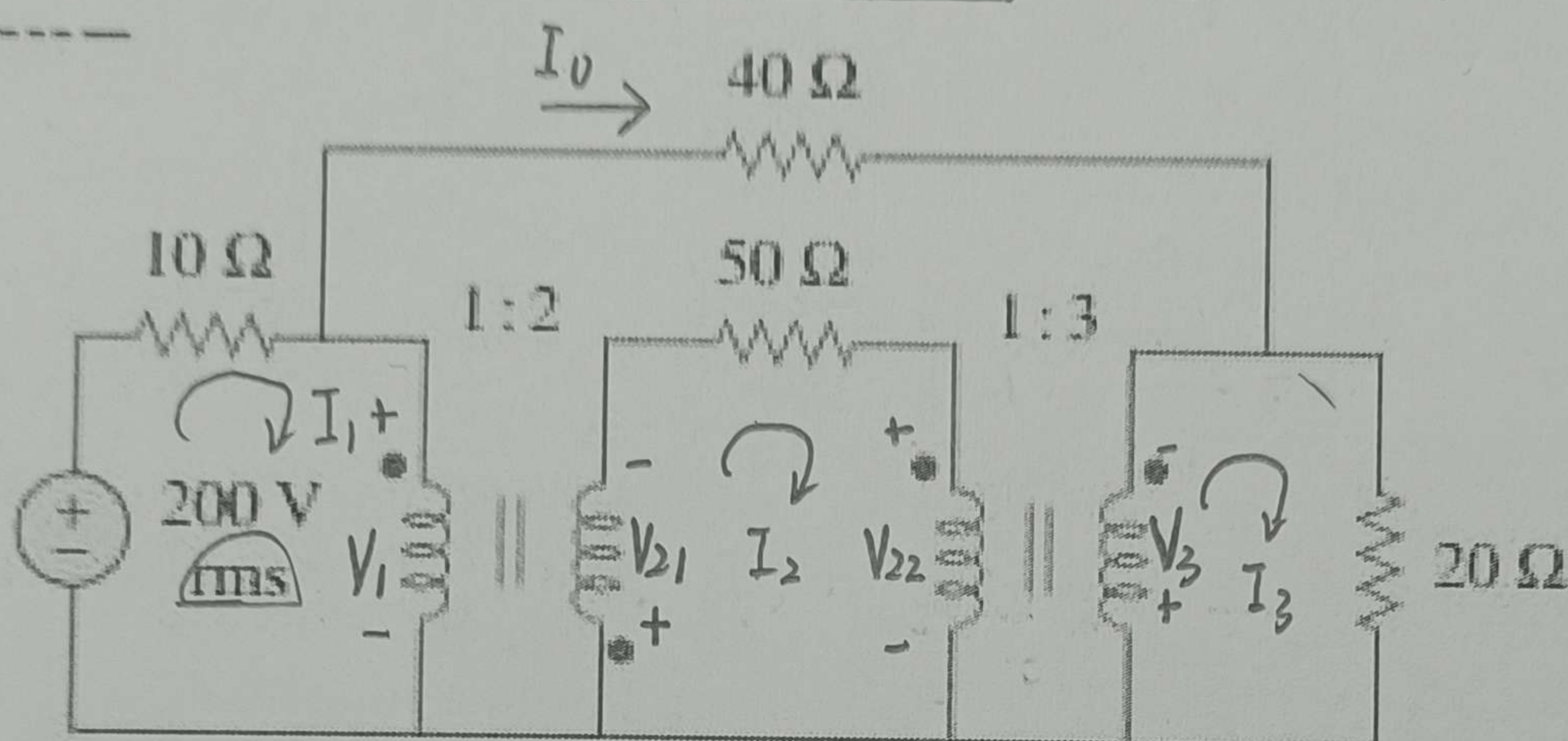


Figure 13.130

解:  $-200 + 10I_1 + V_1 = 0$

$$+V_{21} + 50I_2 + V_{22} = 0$$

$$V_3 + 20I_3 = 0$$

$$\frac{V_{21}}{V_1} = 2 \quad \frac{I_1 - I_0}{I_2} = -2$$

$$\frac{V_3}{V_{22}} = -3 \quad \frac{I_2}{I_3 - I_0} = 3$$

unknowns:  $I_1, I_2, I_3, V_1, V_{21}, V_{22}, V_3, I_0$ ; 8

the outer loop:  $-200 + 10I_1 + 40I_0 + 20I_3 = 0$

8 equations.

$$\Rightarrow \begin{cases} I_3 = \frac{84}{113} \text{ A} \\ I_2 = -\frac{456}{113} \text{ A} \\ I_1 = \frac{1148}{113} \text{ A} \end{cases}$$

$$P_{\text{avg}} = R \cdot I_3^2 = 11.05 \text{ W}$$