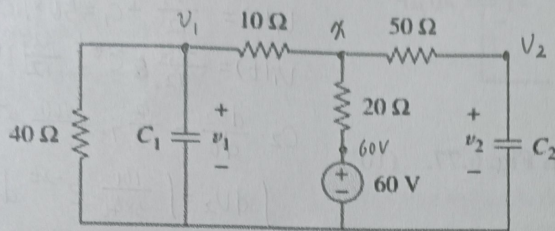


«Fundamentals of Electric Circuits» homework 5

6.13 Find the voltage across the capacitors in the circuit of Fig. 6.49 under dc conditions. (10')




解:

$$\begin{cases} \frac{V_1 - 0}{40} = \frac{x - V_1}{10} \\ \frac{60 - x}{20} = \frac{x - V_1}{10} + \frac{x - V_2}{50} \\ \frac{x - V_2}{50} = 0 \end{cases}$$
$$\Rightarrow V_1 = \frac{240}{7} \text{ V} = 34.29 \text{ V} \quad V_2 = \frac{300}{7} \text{ V} = 42.86 \text{ V}$$

Figure 6.49


6.19 Find the equivalent capacitance between terminals a and b in the circuit of Fig.

6.53. All capacitances are in μF . (10')

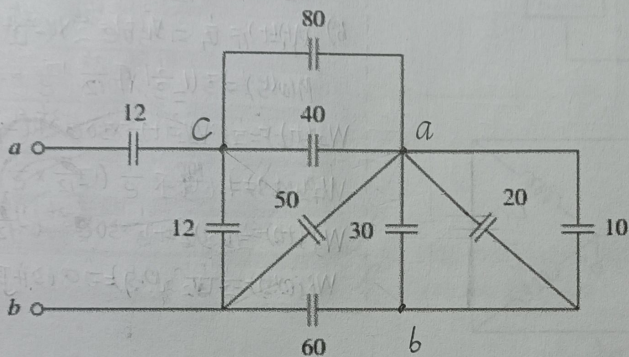

$$C_{ob} = 30 + 20 + 10 = 60 \mu F$$


$$C_{ac} = 80 + 40 = 120 \mu F$$

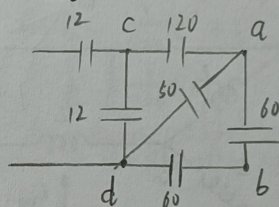

$$C_{adb} = 50 + \frac{60 \times 60}{60 + 60} = 80 \mu F$$

Figure 6.53

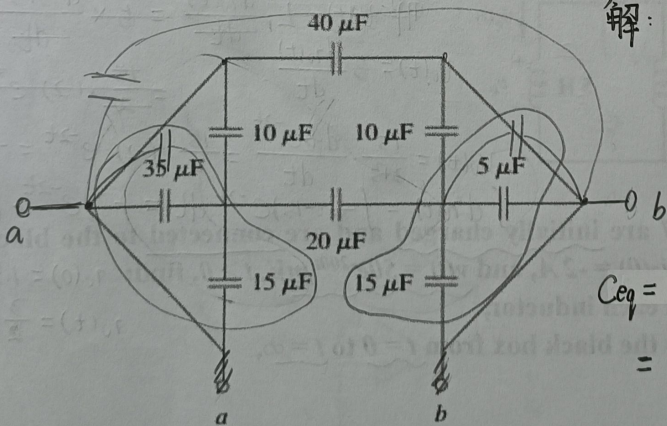6.22 Obtain the equivalent capacitance of the circuit in Fig. 6.56.



解：

$$C_{eq} = [(10+35+15) \parallel 20] \parallel (10+5+15) + 40$$
$$= \frac{20 \times 60}{20+60} \parallel 30 + 40$$
$$= \frac{15 \times 30}{15+30} + 40 = 50 \mu F$$

Figure 6.56

6.32 In the circuit of Fig. 6.64, let $i_s = 50e^{-2t} \text{ mA}$ and $v_1(0) = 50 \text{ V}$, $v_2(0) = 20 \text{ V}$. Determine:

(a) $v_1(t)$ and $v_2(t)$, (b) the energy in each capacitor at $t = 0.5\text{s}$. (10')

$$C \cdot V = q$$

$$C \cdot \frac{dV}{dt} = i$$

$$V_1(t) = -2083.33 e^{-2t} + 2133.33$$

$$V_2(t) = -416.667 e^{-2t} + 436.667$$

$$P_1 = 11.21$$

$$0.803$$

$$1.606$$

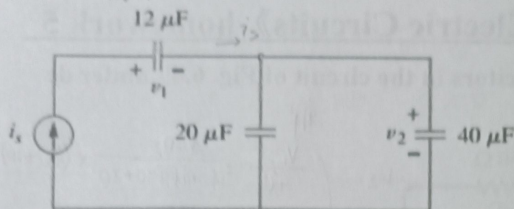


Figure 6.64


6.55 Find L_{eq} in each of the circuits in Fig. 6.77. (10')

解:

$$a) L_{eq} = L + 2L \parallel (2L \parallel L)$$


$$= L + \frac{2L \cdot \frac{1}{2}L}{2L + \frac{1}{2}L}$$

$$= 1.4L$$

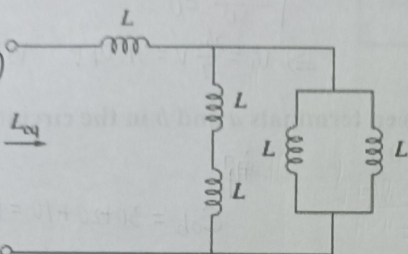

$$b) L_{eq} = L \parallel 2(L \parallel L)$$


$$= \frac{L^2}{L+L} = \frac{L}{2}$$

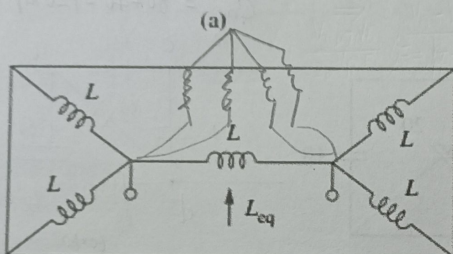

(b)

Figure 6.77

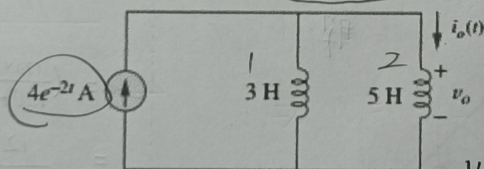6.60 In the circuit of Fig. 6.82, $i_o(0) = 2$ A. Determine $i_o(t)$ and $v_o(t)$ for $t > 0$. (10')



$$v_o(t) = L_1 \frac{di_o(t)}{dt} = 5 \times \frac{d}{dt} \left(\frac{3}{3+5} \times 4e^{-2t} \right)$$

$$v_o(t) = 5 \frac{d i_o(t)}{dt}$$

$$v_o(t) = \frac{15}{3+5} \cdot \frac{d 4e^{-2t}}{dt} = \frac{15}{8} \cdot (-2) \cdot e^{-2t} = -15e^{-2t} \text{ V}$$

Figure 6.82

6.65 The inductors in Fig. 6.87 are initially charged and are connected to the black

box at $t = 0$. If $i_1(0) = 4$ A, $i_2(0) = -2$ A, and $v(t) = 50e^{-200t}$ mV, $t \geq 0$, find: $i_1(0) = 1.5 + C = 2$, $C = 0.5$

(a) the energy initially stored in each inductor,

(b) the total energy delivered to the black box from $t = 0$ to $t = \infty$,

(c) $i_1(t)$ and $i_2(t)$, $t \geq 0$,

(d) $i(t)$, $t \geq 0$. (15')

解: a) $w_1 = \frac{1}{2} L_1 i_1^2 = \frac{1}{2} \times 5 \times 16 = 40 \text{ J}$

$$w_2 = \frac{1}{2} L_2 i_2^2 = \frac{1}{2} \times 20 \times 4 = 40 \text{ J}$$

b) $E = w_1 + w_2 = 80 \text{ J}$

c) $v(t) = L_1 \frac{di_1(t)}{dt}$

$$\int di_1(t) = \int \frac{v(t)}{L_1} dt = \int \frac{-50e^{-200t}}{5} dt = \frac{10}{200} \cdot e^{-200t} + C_1 \text{ mA}$$

$$i_1(0) = 4000 = 0.05 + C_1, C_1 = 3999.95 \text{ mA}$$

$$i_1(t) = \frac{1}{20} e^{-200t} + 3999.95 \text{ mA}$$

解:

$$a) C_1 \frac{dV_1}{dt} = i_s = 50e^{-2t} \text{ mA}$$

$$\int dV_1 = \int \frac{50e^{-2t}}{C_1} dt$$

$$V_1 = \frac{50}{12} \cdot \frac{1}{-2} e^{-2t} + C_1 \text{ kV}$$

$$V_1(0) = \frac{-25}{12} + C_1 = 50 \times 10^{-3} \text{ kV}, C_1 = 2133 \text{ V}$$

$$V_1(t) = -2083 e^{-2t} + 2133 \text{ V} \quad \square$$

$$C_2 \frac{dV_2}{dt} = \frac{2}{3} i_s = \frac{100}{3} e^{-2t} \text{ mA}$$

$$\int dV_2 = \int \frac{100}{3 \times 40} e^{-2t} dt$$

$$V_2 = \frac{5}{6} \times \frac{1}{-2} e^{-2t} + C_2 \text{ kV}$$

$$V_2(0) = \frac{-5}{12} + C_2 = 20 \times 10^{-3} \text{ kV}, C_2 = 436.7 \text{ V}$$

$$V_2(t) = -416.7 e^{-2t} + 436.7 \text{ V} \quad \square$$

b) $w_1(t) = \frac{1}{2} C_1 V_1^2(t) = \frac{1}{2} \times 12 \times 10^{-6} \times (-2083 e^{-2t} + 2133)^2$

$$w_1(0.5) = 11.21 \text{ J} \quad \square$$

$$w_2(t) = \frac{1}{2} C_2 V_2^2(t) = \frac{1}{2} \times 40 \times 10^{-6} \times (-416.7 e^{-2t} + 436.7)^2$$

$$w_2(0.5) = 1.606 \text{ J} \quad \square$$

$$w_3(t) = \frac{1}{2} C_3 V_3^2(t)$$

$$w_3(0.5) = \frac{1}{2} w_2(0.5) = 0.8031 \text{ J} \quad \square$$

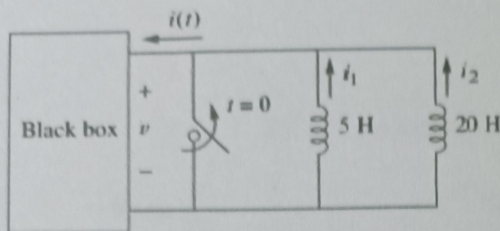


Figure 6.87

$$v(t) = L_2 \frac{di_2(t)}{dt}$$

$$\int di_2(t) = \int \frac{1}{L_2} v(t) dt = \frac{1}{20} \int 50 e^{-200t} dt$$

$$i_2(t) = \frac{5}{2} \cdot \frac{1}{+200} \cdot e^{-200t} + C_2$$

$$i_2(0) = \frac{5}{+400} + C_2 = -2000, C_2 = -2000.0125 \text{ mA}$$

$$i_2(t) = \frac{1}{80} \cdot e^{-200t} - 2000.0125 \text{ mA}$$

$$d) i(t) = i_1(t) + i_2(t)$$

$$= \frac{1}{16} e^{-200t} + 1999.9375 \text{ mA}$$

6.72 At $t = 1.5 \text{ ms}$ calculate v_o due to the cascaded integrators in Fig. 6.89. Assume that the integrators are reset to 0 V at $t = 0$. (15')

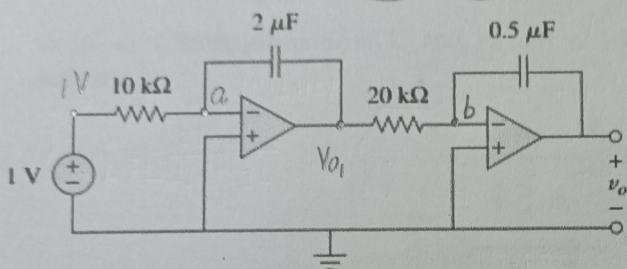


Figure 6.89

$$\begin{cases} \frac{1 - V_a}{10 \times 10^3} = 2 \times 10^{-6} \times \frac{d(V_a - V_{o1})}{dt} \times 10^{-3} \\ \frac{V_{o1} - V_b}{20 \times 10^3} = 0.5 \times 10^{-6} \times \frac{d(V_b - V_o)}{dt} \times 10^{-3} \\ V_a = V_b = 0 \end{cases}$$

$$\Rightarrow V_o = \frac{1}{400} t^2 + \left(\frac{C_1}{-10}\right)t + C_3 \text{ V (ms)}$$


$$V_{o1} = \frac{1}{20} t + C_1 \text{ V (ms)}$$

$$\text{As } V_{o1}(0) = 0 = V_{o1}(0) \Rightarrow C_1 = C_3 = 0, V_o(t) = \frac{t^2}{400}$$

6.74 The triangular waveform in Fig. 6.91(a) is applied to the input of the op amp differentiator in Fig. 6.91(b). Plot the output. (10')

$$V_o(1.5) = \frac{1.5^2}{400} = 5.625 \times 10^{-3} \text{ V}$$


$$= 5.625 \text{ mV}$$

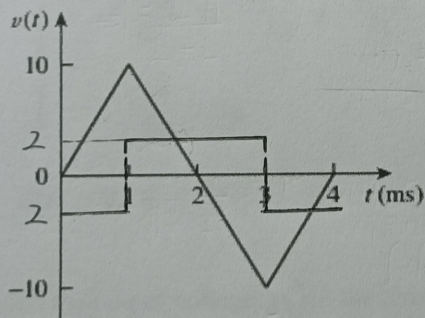

(a)

$$\begin{cases} \frac{d(V_i - V_a)}{dt} \times 0.01 \times 10^{-3} = \frac{V_a - V_o}{20} \times 10^{-3} \\ V_a = 0 \end{cases}$$
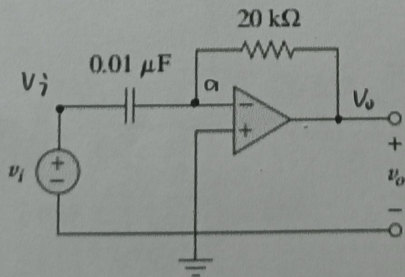
$$\Rightarrow V_o = -0.2 \frac{dv_i}{dt}$$



(b)

Figure 6.91