

《Fundamentals of Electric Circuits》 homework CH.14

14.29 Let $v_s = 20 \cos(\omega t)$ V in the circuit of Fig. 14.77. Find ω_0 , Q , and B , (as seen by the capacitor). (10')

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{60 \times 10^{-3} \times 1 \times 10^{-6}}} = 4082 \text{ rad/s}$$

$$Q = \frac{R}{\omega_0 L} = \frac{12145 \times 10^3}{4082 \times 60 \times 10^{-3}} = 38.68$$

$$B = \frac{\omega_0}{Q} = \frac{4082}{38.68} = 105.5 \text{ rad/s}$$

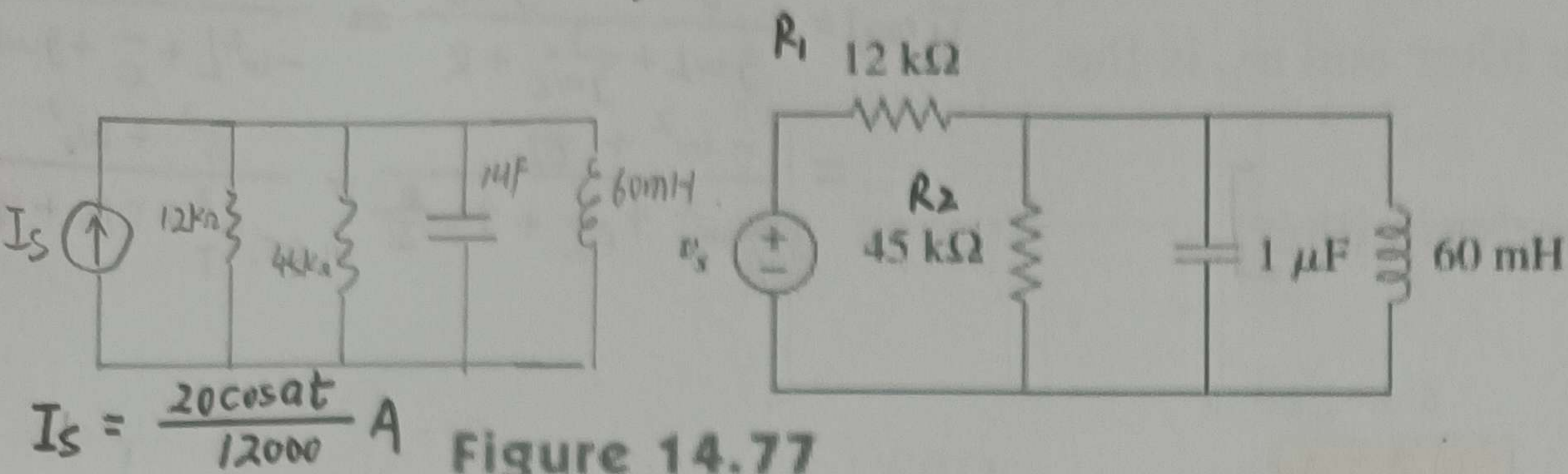


Figure 14.77

14.34 A (parallel RLC) circuit is resonant at 5.6 MHz, has a Q of 80, and has a resistive branch of $40 \text{ k}\Omega$. Determine the values of L and C in the other two branches. (10')

$$\omega_0 = 2\pi \times 5.6 \times 10^6 = 3.519 \times 10^7 \text{ rad/s} \quad L = \frac{R}{Q\omega_0} = \frac{40 \times 10^3}{80 \times 3.519 \times 10^7} = 1.42 \times 10^{-5} \text{ H} \quad C = \frac{Q}{\omega_0 R} = \frac{80}{3.519 \times 10^7 \times 40} = 5.68 \times 10^{-8} \text{ F}$$

14.42 For the circuits in Fig. 14.81, find the resonant frequency ω_0 , the quality factor Q , and the bandwidth B . (10')

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \times 0.4}} = 1.581 \text{ rad/s}$$

$$Q = \frac{\omega_0 L}{R} = \frac{1.581 \times 1}{8} = 0.1976$$

$$B = \frac{R}{L} = \frac{8}{1} = 8 \text{ rad/s}$$

$$b) C = \frac{18}{3+6} = 2 \mu\text{F}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 10^{-3} \times 2 \times 10^{-6}}} = 5000 \text{ rad/s}$$

$$Q = \omega_0 RC = 5000 \times 2000 \times 2 \times 10^{-6} = 20$$

$$B = \frac{1}{RC} = \frac{1}{2000 \times 2 \times 10^{-6}} = 250 \text{ rad/s}$$

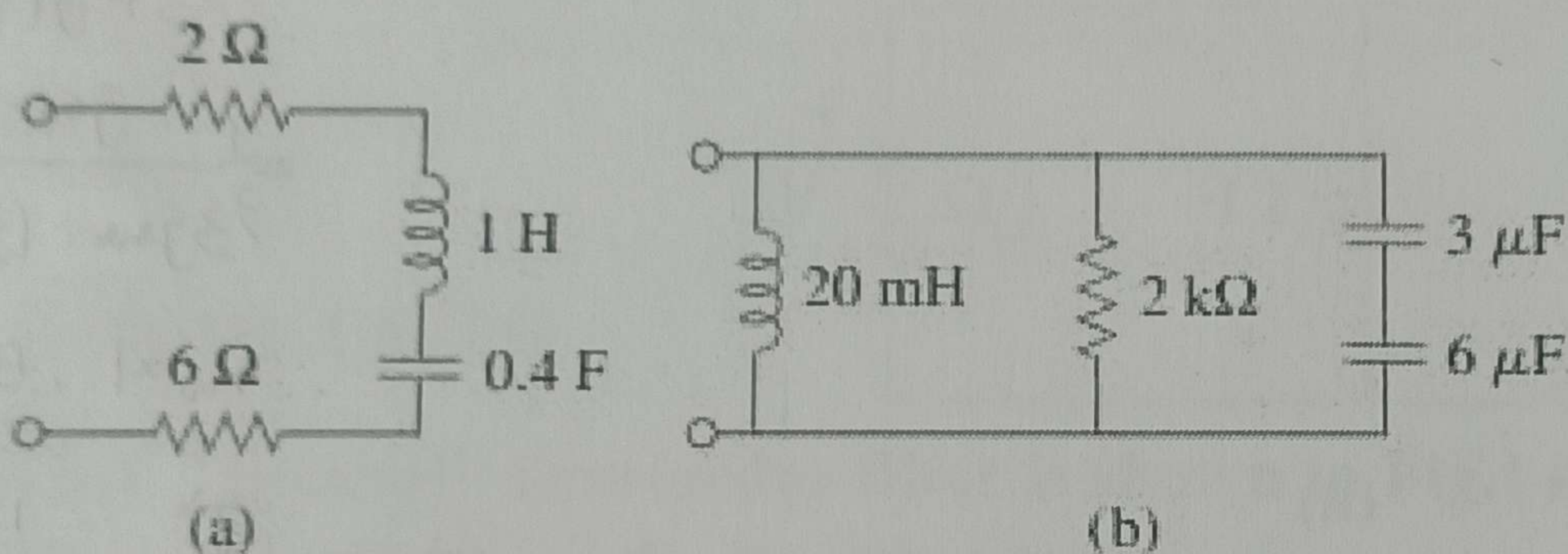


Figure 14.81

14.46 For the network illustrated in Fig. 14.85, find

(a) the transfer function $H(\omega) = V_o(\omega)/I(\omega)$,

(b) the magnitude of H at $\omega_0 = 1 \text{ rad/s}$. (10')


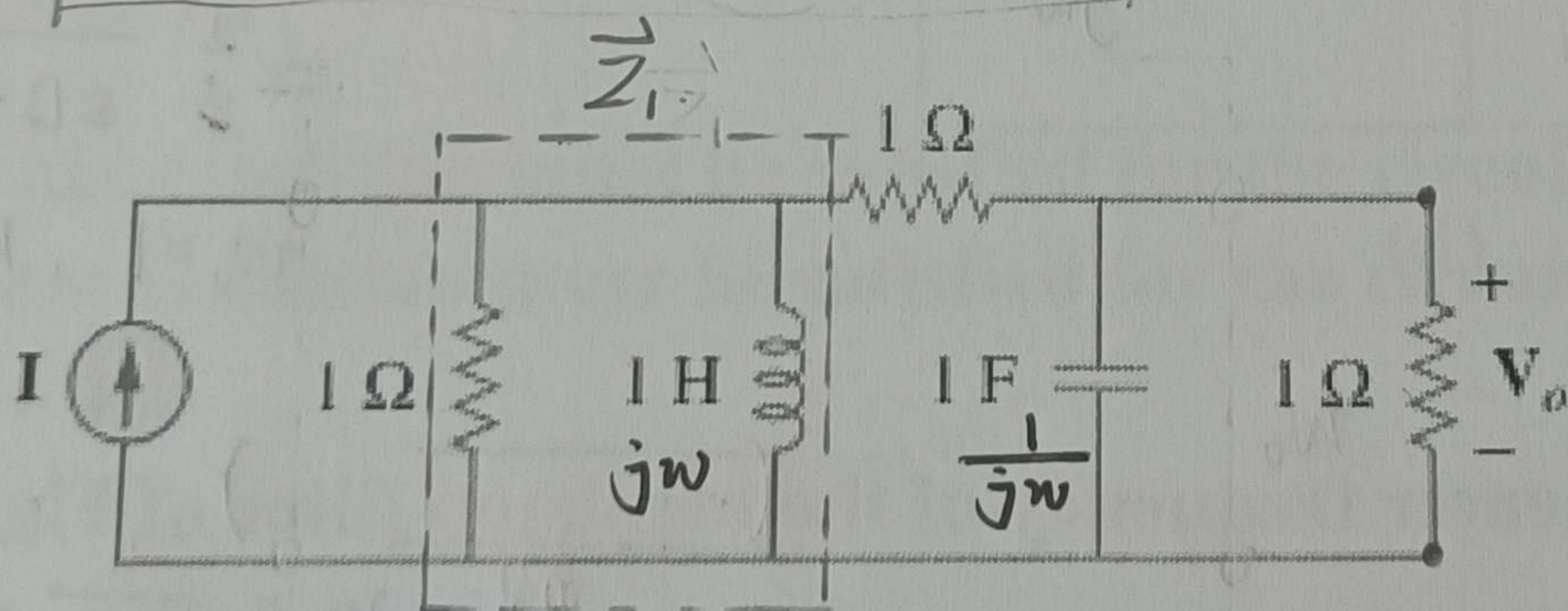



Figure 14.85

14.46 解: a) $\vec{Z}_1 = 1 || j\omega = \frac{j\omega}{1+j\omega}$

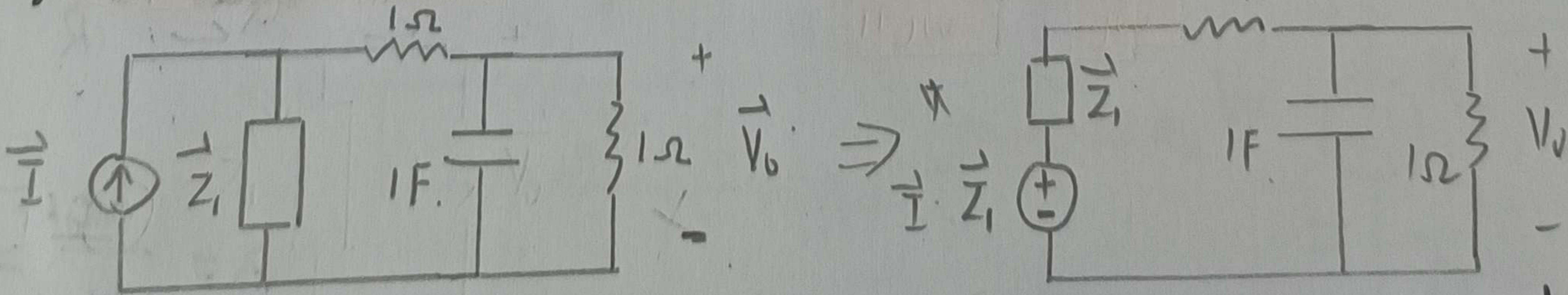

$$\frac{\vec{I} \cdot \vec{Z}_1}{\vec{Z}_1 + 1 + \frac{1}{j\omega} || 1} \cdot (j\omega || 1) = \vec{V}_o \Rightarrow H(\omega) = \frac{\vec{V}_o(\omega)}{\vec{I}(\omega)} = \frac{\vec{Z}_1 \cdot (j\omega || 1)}{\vec{Z}_1 + 1 + \frac{1}{j\omega} || 1} = \frac{j\omega}{2(1+j\omega)^2}$$
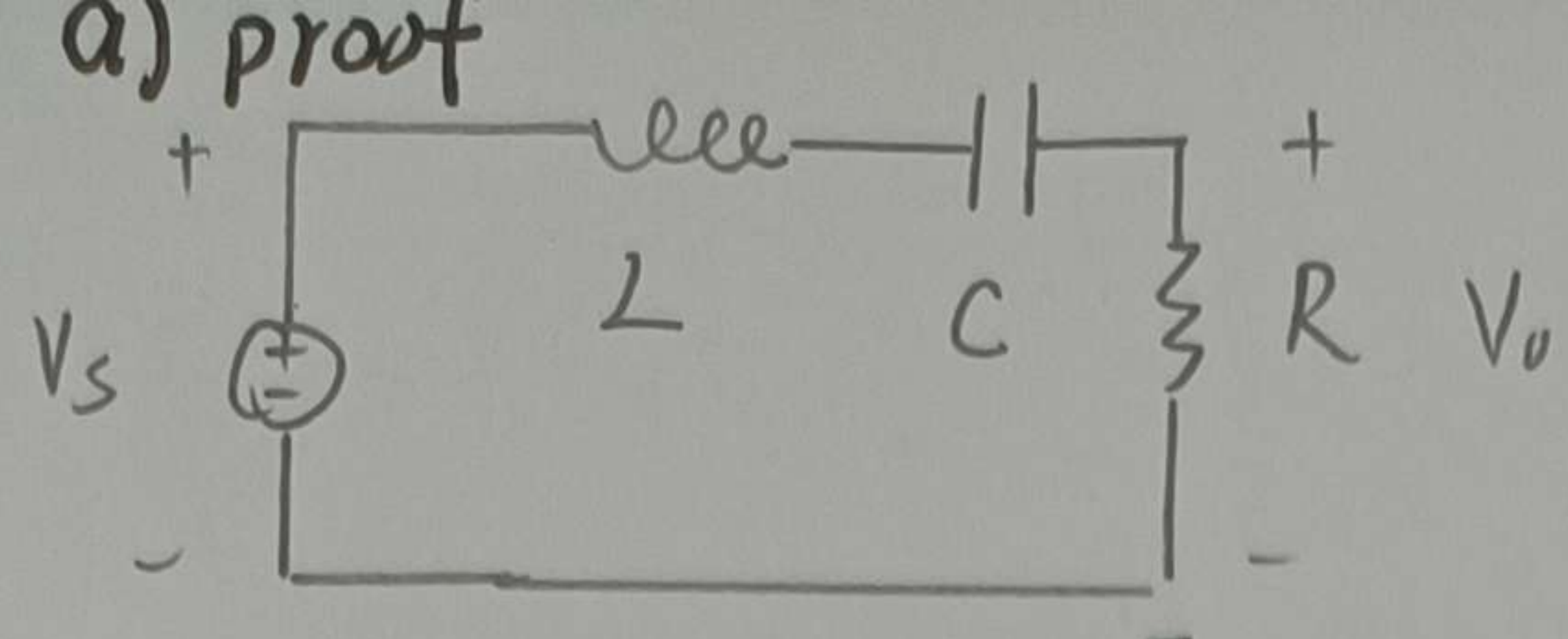
$$b) H(\omega_0) = \frac{j}{2(1+j)^2} = \frac{j}{2[1+(-1)+2j]} = 0.25$$



(a) Show that for a [bandpass filter]

$$H(s) = \frac{sB}{s^2 + sB + \omega_0^2}, \quad s = j\omega$$

where B = bandwidth of the filter and ω_0 is the center frequency.

(b) Similarly, show that for a [bandstop filter]

$$H(s) = \frac{s^2 + \omega_0^2}{s^2 + sB + \omega_0^2}, \quad s = j\omega$$


b) proof:

$$\begin{aligned} \vec{H}(\omega) &= \frac{j\omega L + \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C} + R} = \frac{-\omega^2 L + \frac{1}{C}}{-\omega^2 L + \frac{1}{C} + j\omega R} \\ &= \frac{-\omega^2 + \frac{1}{CL}}{-\omega^2 + \frac{1}{CL} + j\omega \frac{R}{L}} = \frac{s^2 + \omega_0^2}{s^2 + sB + \omega_0^2} \end{aligned}$$

14.57 $\omega_0 = \frac{1}{\sqrt{LC}}$ 不可用.

Determine the center frequency and bandwidth of the [bandpass] filters in Fig.14.88. (10')


解: a) $\vec{H}(\omega) = \frac{V_o}{V_s} = \frac{\frac{1}{j\omega} || (\frac{1}{j\omega} + 1) \times (\frac{1}{j\omega} + 1)}{1 + \frac{1}{j\omega} || (\frac{1}{j\omega} + 1)}$

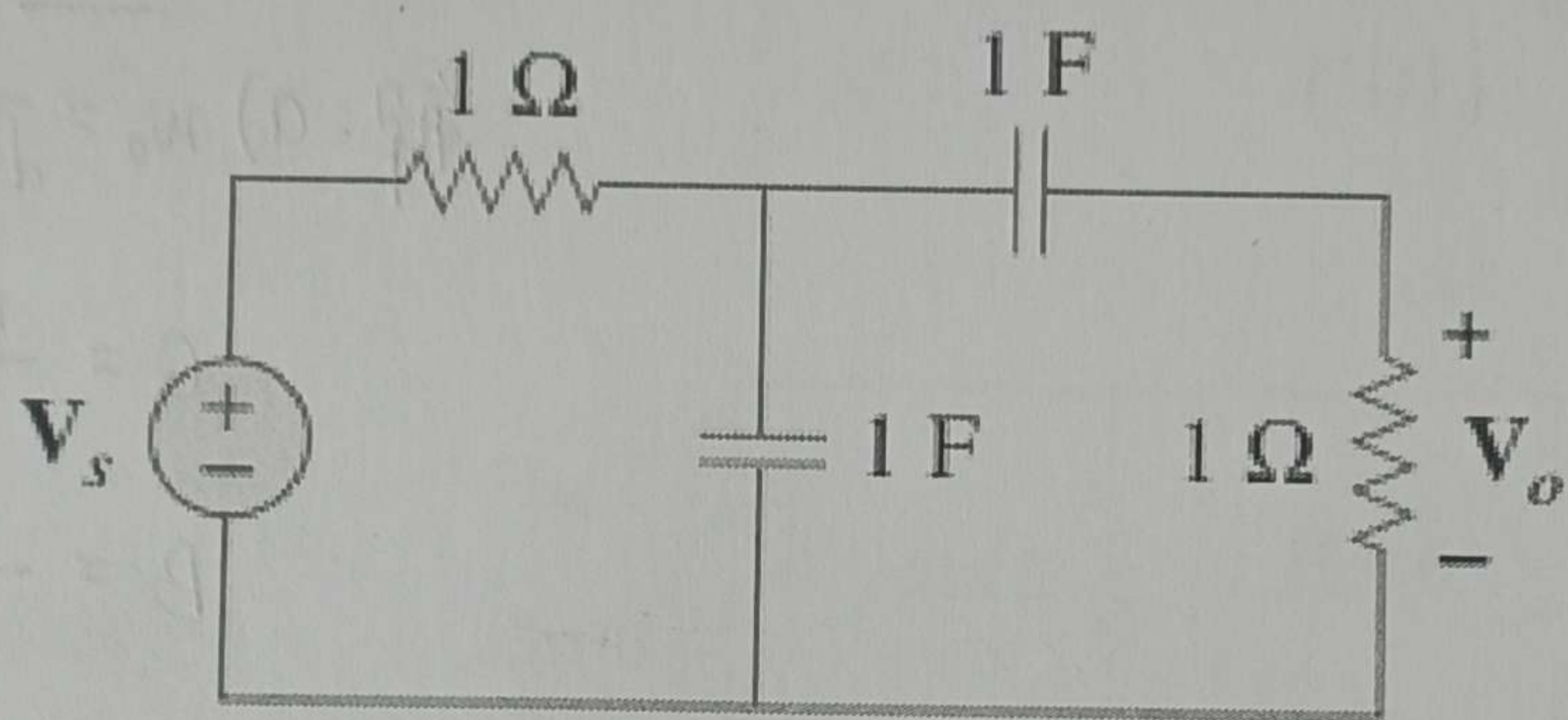

(a)

$$\begin{aligned} &= \frac{1}{3 + 6(\omega - \frac{1}{\omega})} = \frac{1}{3 + j\omega - \frac{1}{\omega}j} \\ &= \frac{1}{3} \frac{j\omega \cdot 3}{3j\omega + (j\omega)^2 + 1} = \frac{1}{3} \frac{s \cdot B}{sB + s^2 + \omega_0^2} \end{aligned}$$

$$\therefore \omega_0 = 1, B = 3$$

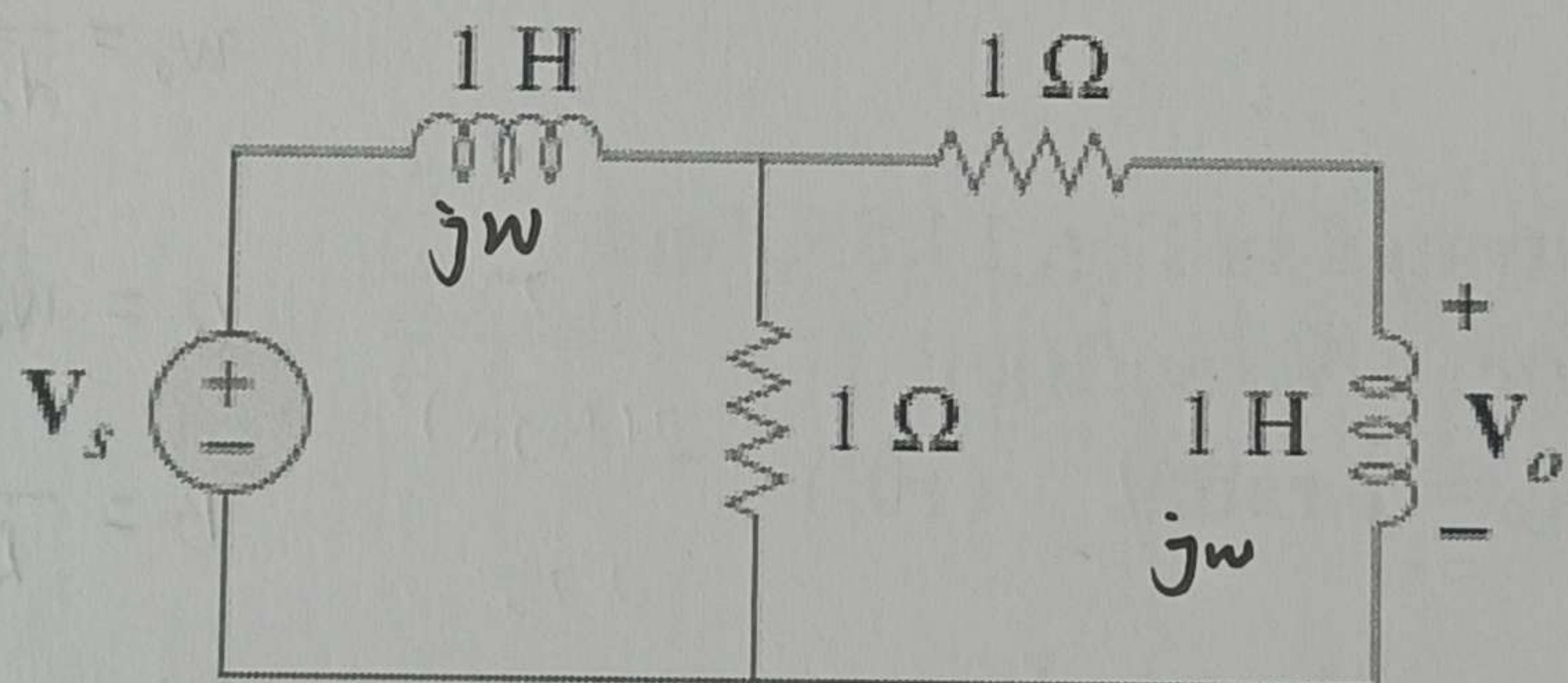

(b)

b) $\vec{H}(\omega) = \frac{V_o}{V_s} = \frac{1 || (1 + j\omega) \cdot \frac{j\omega}{1 + j\omega}}{j\omega + 1 || (1 + j\omega)}$

$$= \frac{1}{3} \frac{3j\omega}{3j\omega + (j\omega)^2 + 1}$$

$$= \frac{1}{3} \frac{sB}{sB + s^2 + \omega_0^2}$$

$$\therefore \omega_0 = 1, B = 3$$

Figure 14.88

14.59 Find the bandwidth and center frequency of the [bandstop] filter of Fig.14.89. (10')

解: $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 4 \times 10^{-6}}} = 15811 \text{ rad/s}$

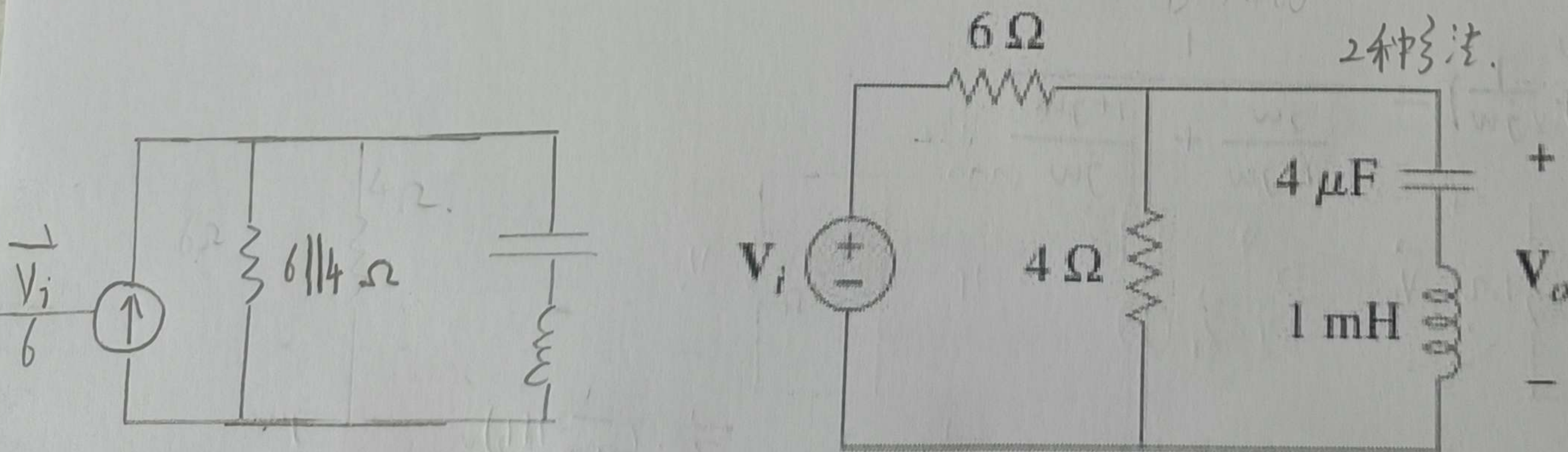



Figure 14.89

$$Q = \frac{\omega_0 L}{R} = \frac{15811 \times 1 \times 10^{-3}}{6114}$$

$$= 6.588$$


$$B = \frac{\omega_0}{Q} = \frac{R}{L} = \frac{6114}{1 \times 10^{-3}} = 2400 \text{ rad/s}$$

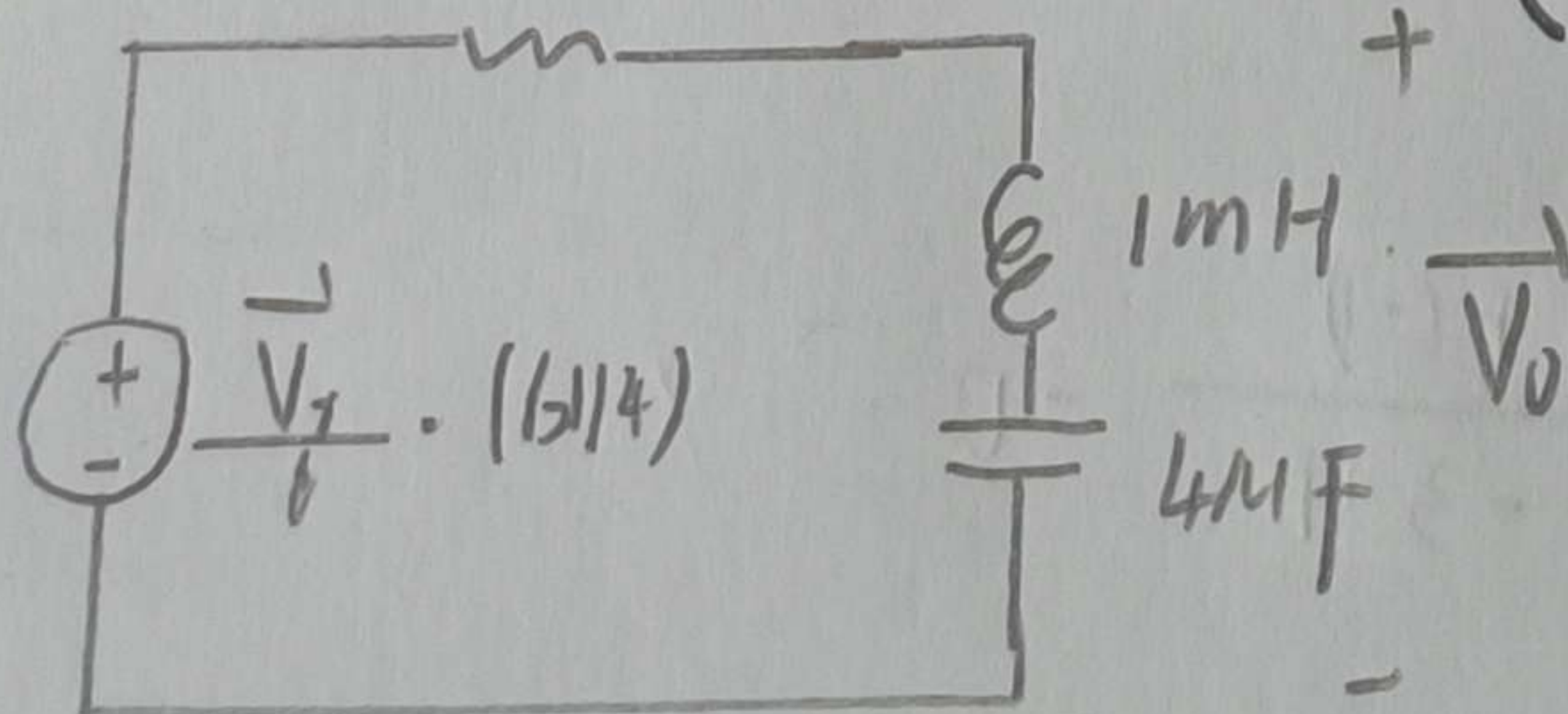14.61 Find the (transfer function) for each of the (active filters) in Fig.14.90. (10')



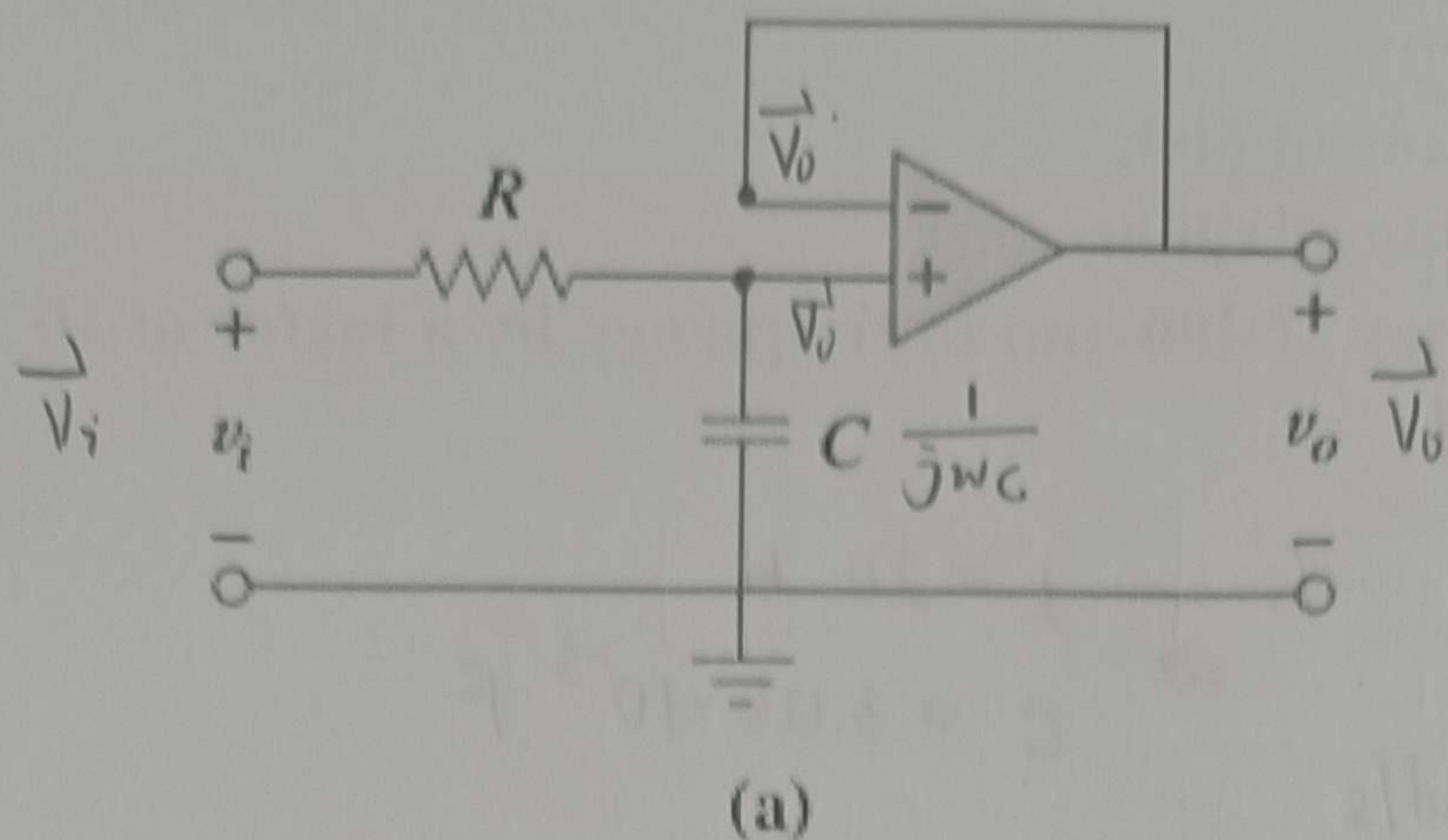14.61 解:

$$a) \vec{H}(\omega) = \frac{\vec{V}_o}{\vec{V}_i} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{j\omega CR + 1}$$



b) $\vec{H}(\omega) = \frac{\vec{V}_o}{\vec{V}_i} = \frac{R}{\frac{1}{j\omega C} + R} = \frac{j\omega CR}{1 + j\omega CR}$

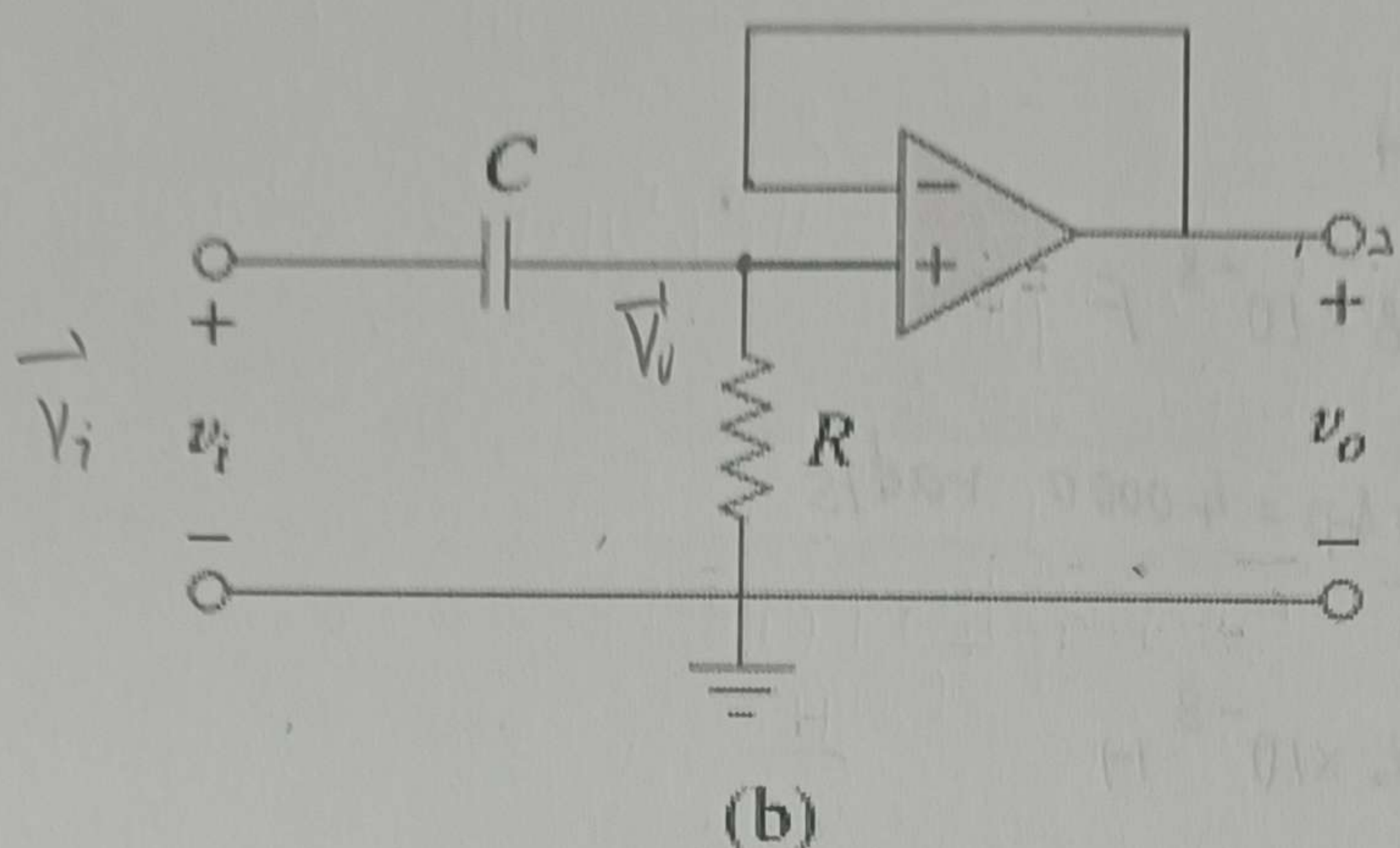


Figure 14.90

14.66 A "general" first-order filter is shown in Fig.14.93.

(a) Show that the transfer function is

$$H(s) = \frac{R_4}{R_3 + R_4} \times \frac{s + (1/R_1 C)[R_1/R_2 - R_3/R_4]}{s + 1/R_2 C}$$

$s = j\omega$

14.66 解:

a) proof:


$$\begin{cases} \vec{V}_i = \vec{V}_s \cdot \frac{R_4}{R_3 + R_4} \\ \frac{\vec{V}_s - \vec{V}_i}{R_1} = \frac{\vec{V}_i - \vec{V}_o}{R_2 \parallel \frac{1}{j\omega C}} \end{cases}$$

$$\Rightarrow \vec{H}(\omega) = \frac{\vec{V}_o}{\vec{V}_s} = \frac{R_4}{R_3 + R_4} - \frac{R_3}{(R_3 + R_4)R_1} \left(R_2 \parallel \frac{1}{j\omega C} \right)$$

(b) What condition must be satisfied for the circuit to operate as a highpass filter?

(c) What condition must be satisfied for the circuit to operate as a lowpass filter?

(10')

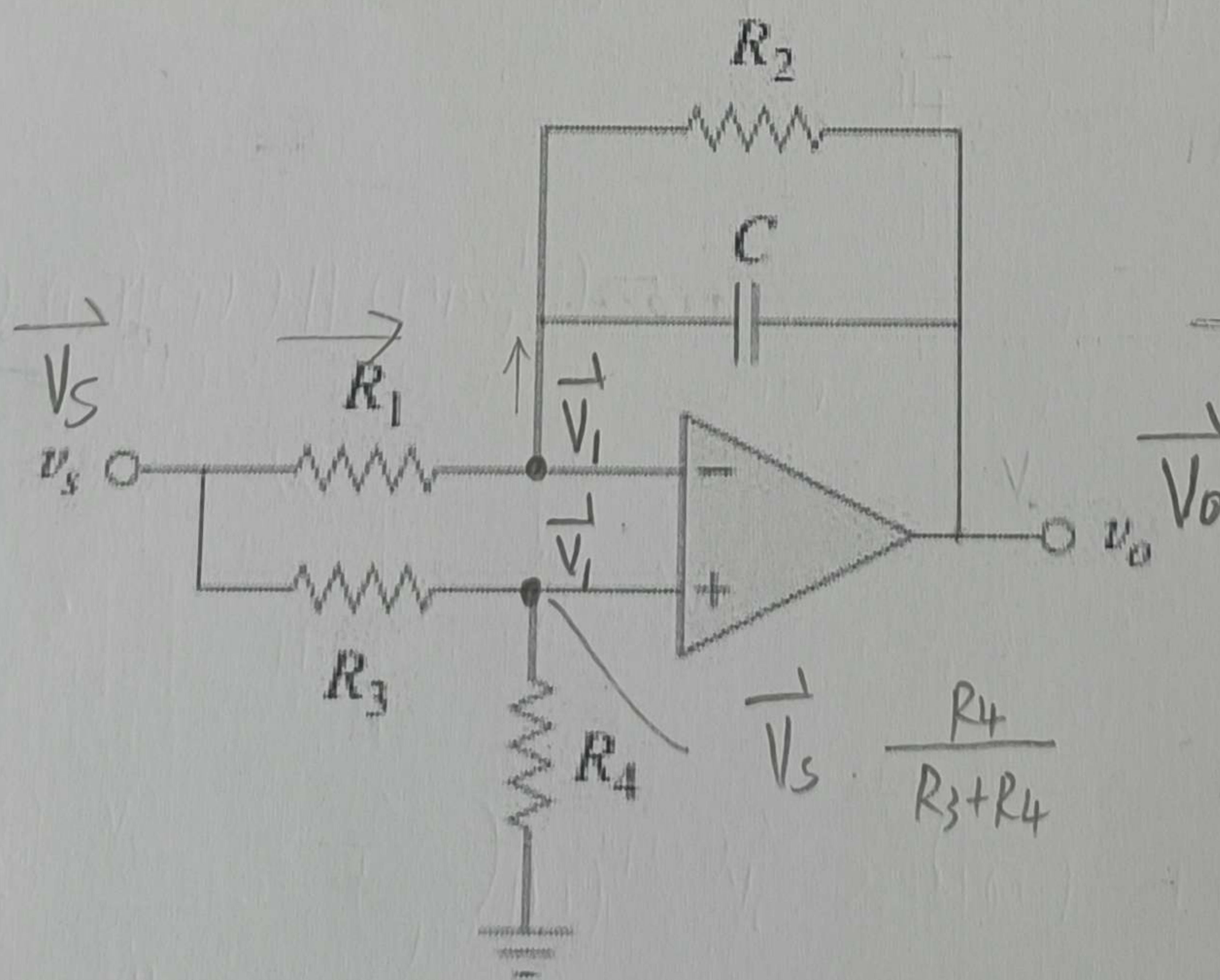

$$\begin{aligned} &= \frac{R_4}{R_3 + R_4} \cdot \left[1 - \frac{R_3}{R_1 R_4} \left(R_2 \parallel \frac{1}{j\omega C} \right) \right] \\ &= \frac{R_4}{R_3 + R_4} \cdot \frac{R_1 R_4 - R_3 \cdot \frac{R_2}{1 + j\omega C R_2}}{R_1 R_4} \\ &= \frac{R_4}{R_3 + R_4} \cdot \frac{1 + j\omega C R_2 - \frac{R_2 R_3}{R_1 R_4}}{1 + j\omega C R_2} \\ &= \frac{R_4}{R_3 + R_4} \cdot \frac{\frac{1}{C R_2} + j\omega - \frac{R_3}{R_1 R_4 C}}{j\omega + \frac{1}{C R_2}} \\ &= \frac{R_4}{R_3 + R_4} \cdot \frac{s + \frac{1}{C R_2} \left(\frac{R_1}{R_2} - \frac{R_3}{R_4} \right)}{s + 1/C R_2} \end{aligned}$$

Figure 14.93

b) high pass filter.

$$\omega \rightarrow 0, H \rightarrow 0$$

$$\therefore \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

c) lowpass filter

$$\omega \rightarrow \infty, H \rightarrow 0$$

$$\lim_{\omega \rightarrow \infty} \vec{H}(s) = \frac{R_4}{R_3 + R_4} \rightarrow 0$$

$$R_3 \gg R_4, (R_3 \rightarrow \infty)$$

$$\frac{R_3}{R_4} \rightarrow \infty$$

14.77 A (series RLC) circuit has $R = 100$, $\omega_0 = 40$ rad/s, and $B = 5$ rad/s. Find L and C when the circuit is scaled:

(a) in magnitude by a factor of 600,

(b) in frequency by a factor of 1,000,

(c) in magnitude by a factor of 400 and in frequency by a factor of 10^5 . (10')

解: a) without scaled.

$$\omega_0 = \frac{1}{\sqrt{LC}} = 40 \text{ rad/s} \Rightarrow L = 20 \text{ H}$$

$$B = \frac{R}{L} = 5 \text{ rad/s}$$

$$C = 3.125 \times 10^{-5} \text{ F}$$

$$k_m = 600$$

$$L' = k_m L = 12000 \text{ H}$$

$$C' = \frac{C}{k_m} = 5.208 \times 10^{-8} \text{ F}$$

$$b) L' = \frac{L}{k_f} = 0.02 \text{ H}$$

$$C' = \frac{C}{k_f} = 3.125 \times 10^{-8} \text{ F}$$

$$c) L' = \frac{k_m L}{k_f} = \frac{400 \times 20}{10^5} = 0.08 \text{ H}$$

$$C' = \frac{C}{k_f k_m} = \frac{3.125 \times 10^{-5}}{10^5 \times 400} = 7.8125 \times 10^{-13} \text{ F}$$