

《Fundamentals of Electric Circuits》 homework 6

7.7 Assuming that the switch in Fig. 7.87 has been in position A for a long time and is moved to (position B at $t = 0$). Then at $t = 1$ second, the switch moves from B to C. Find $v_C(t)$ for $t \geq 0$. (10')

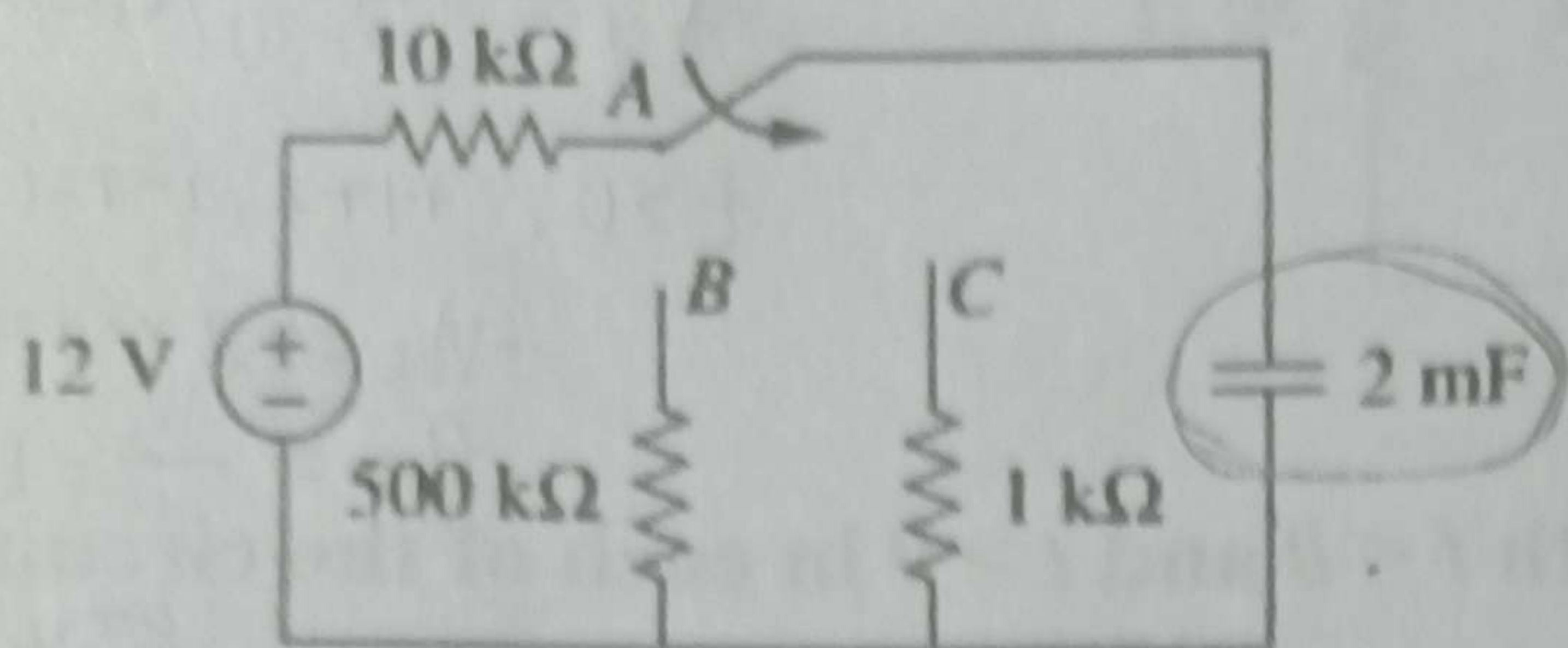


Figure 7.87

7.16 Determine the time constant for each of the circuits in Fig. 7.96. (10')

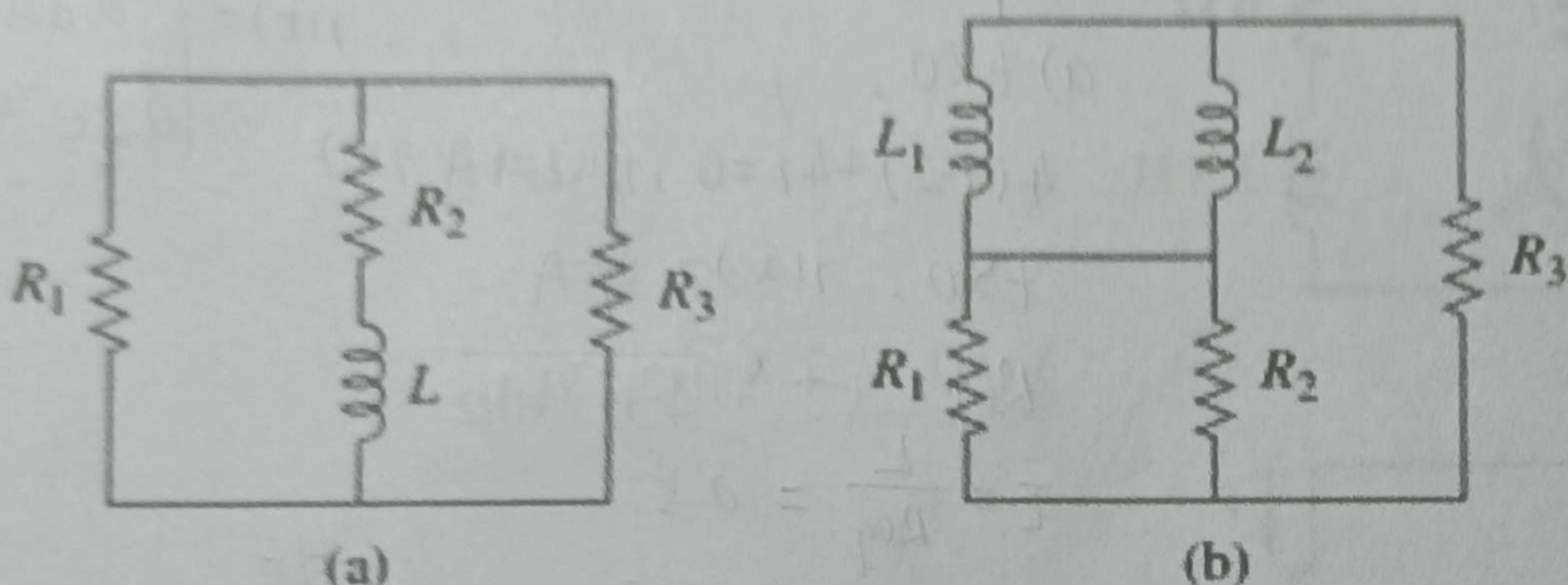


Figure 7.96

7.19 In the circuit of Fig. 7.99, find $i(t)$ for $t > 1$ if $i(0) = 6$ A. (10')

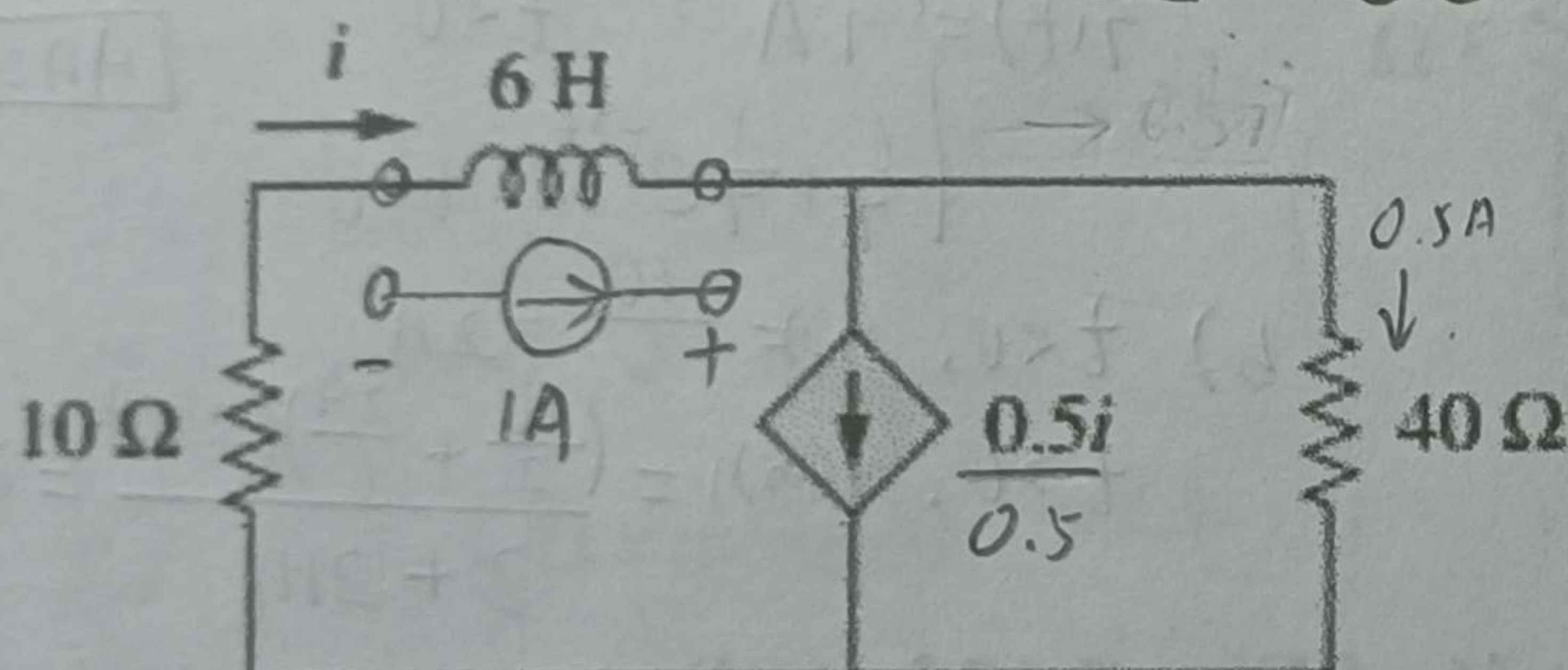


Figure 7.99

7.29 Sketch the following functions:

(a) $x(t) = 10e^{-t}u(t-1)$


(b) $y(t) = 10e^{-(t-1)}u(t)$

(c) $z(t) = \cos 4t\delta(t-1)$

解: a) $x(t) = \begin{cases} 0 & t < 1 \\ 10e^{-t} & t \geq 1 \end{cases}$

(10') b) $y(t) = \begin{cases} 0 & t < 0 \\ 10e^{-(t-1)} & t \geq 0 \end{cases}$

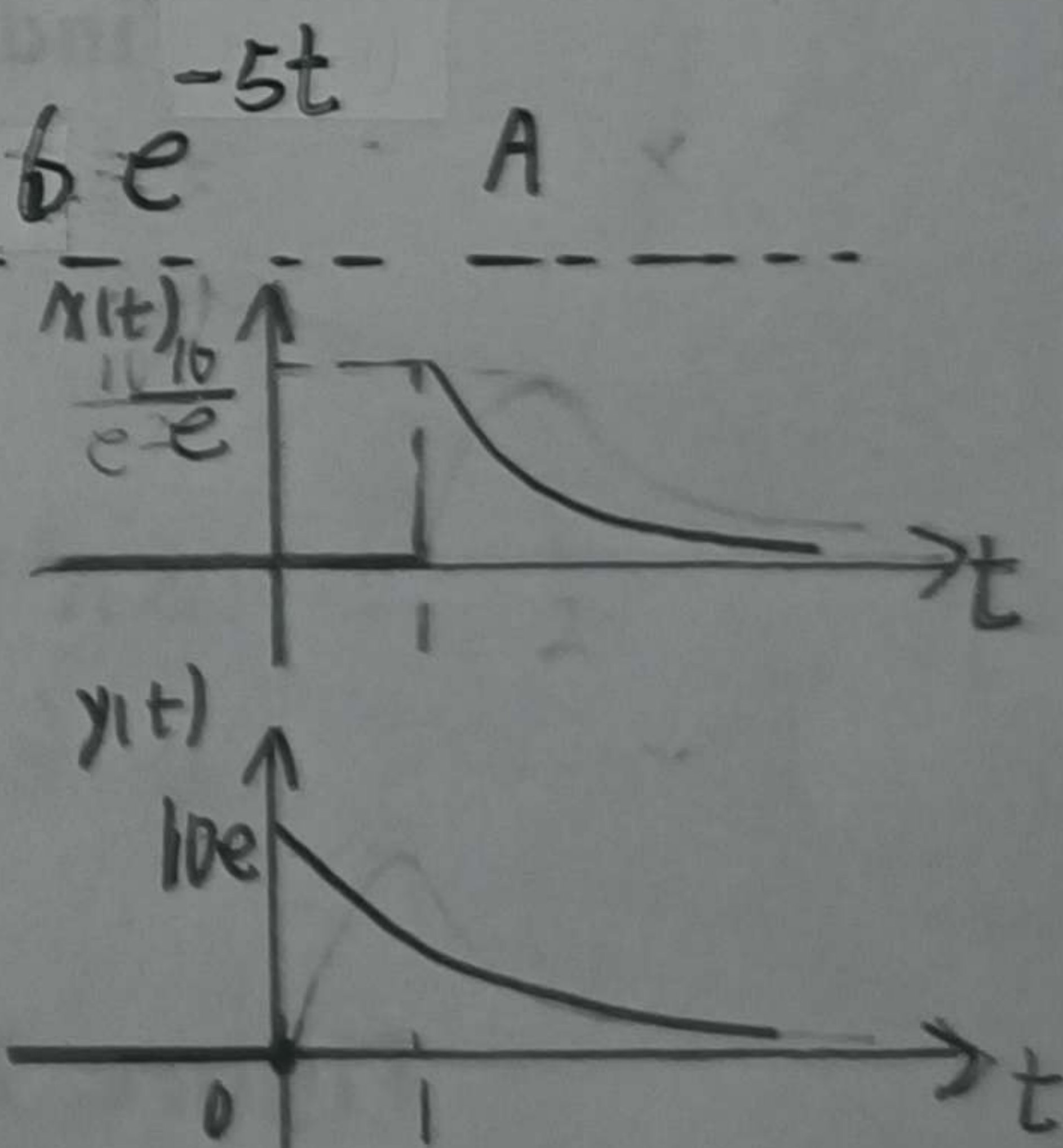c) $z(t) = \begin{cases} 0 & t \neq 1 \\ \cos 4 & t = 1 \end{cases}$



7.37 A circuit is described by

$$4 \frac{dv}{dt} + v = 10$$

(a) What is the time constant of the circuit?

(b) What is $v(\infty)$, the final value of v ?

(c) If $v(0) = 2$, find $v(t)$ for $t \geq 0$.

解: a) $\frac{dv}{dt} = \frac{10-v}{4}$

$$\int \frac{dv}{10-v} = \int \frac{1}{4} dt$$

$$v = 10 - Ae^{-\frac{1}{4}t}$$


$$\tau = 4$$

b) $t \rightarrow \infty$

$$v = \lim_{t \rightarrow \infty} (10 - Ae^{-\frac{1}{4}t}) = 10$$

c) $v(0) = 2 \Rightarrow 2 = 10 - A, A = 8$

$$v(t) = 10 - 8e^{-\frac{1}{4}t}$$

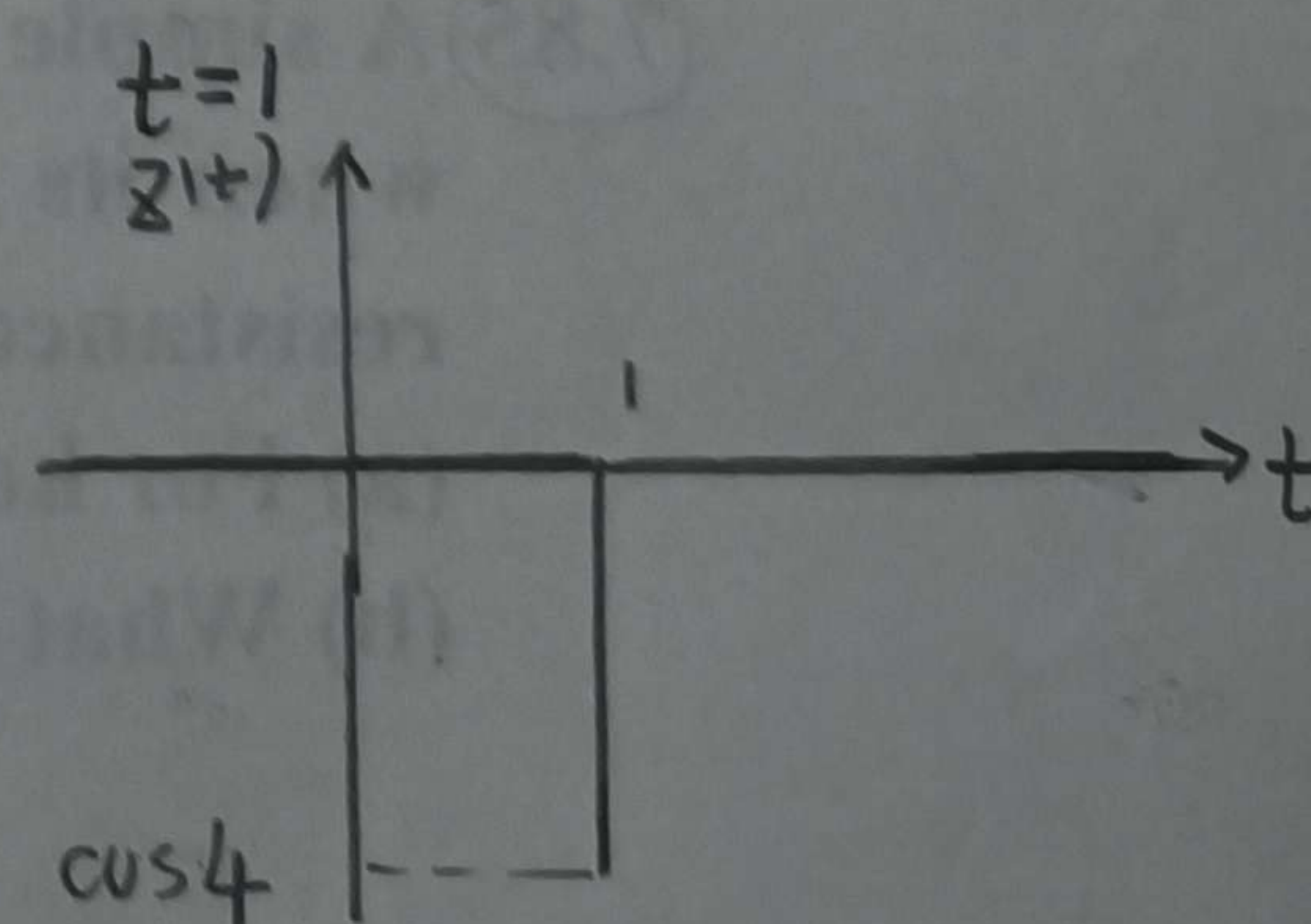

7.43 Consider the circuit in Fig. 7.110. Find $i(t)$ for $t < 0$ and $t > 0$. (10')



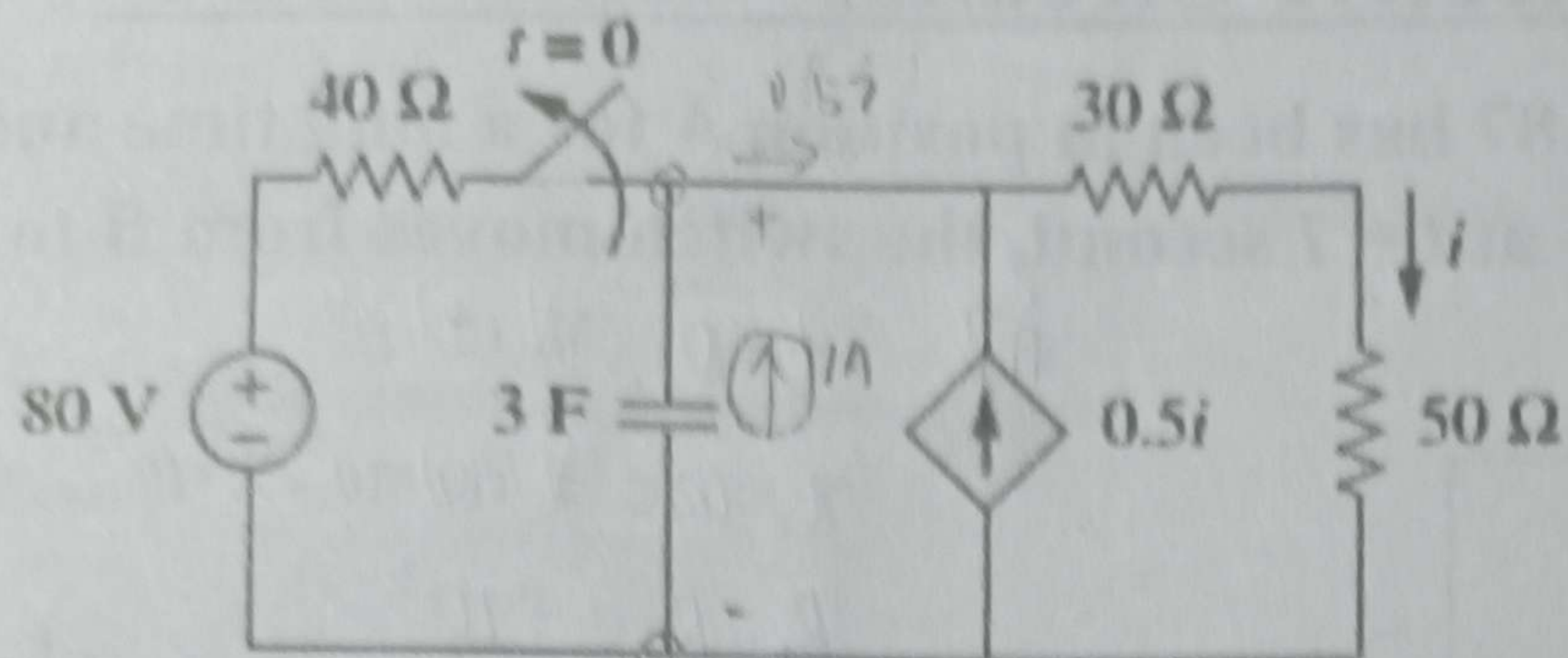


Figure 7.110

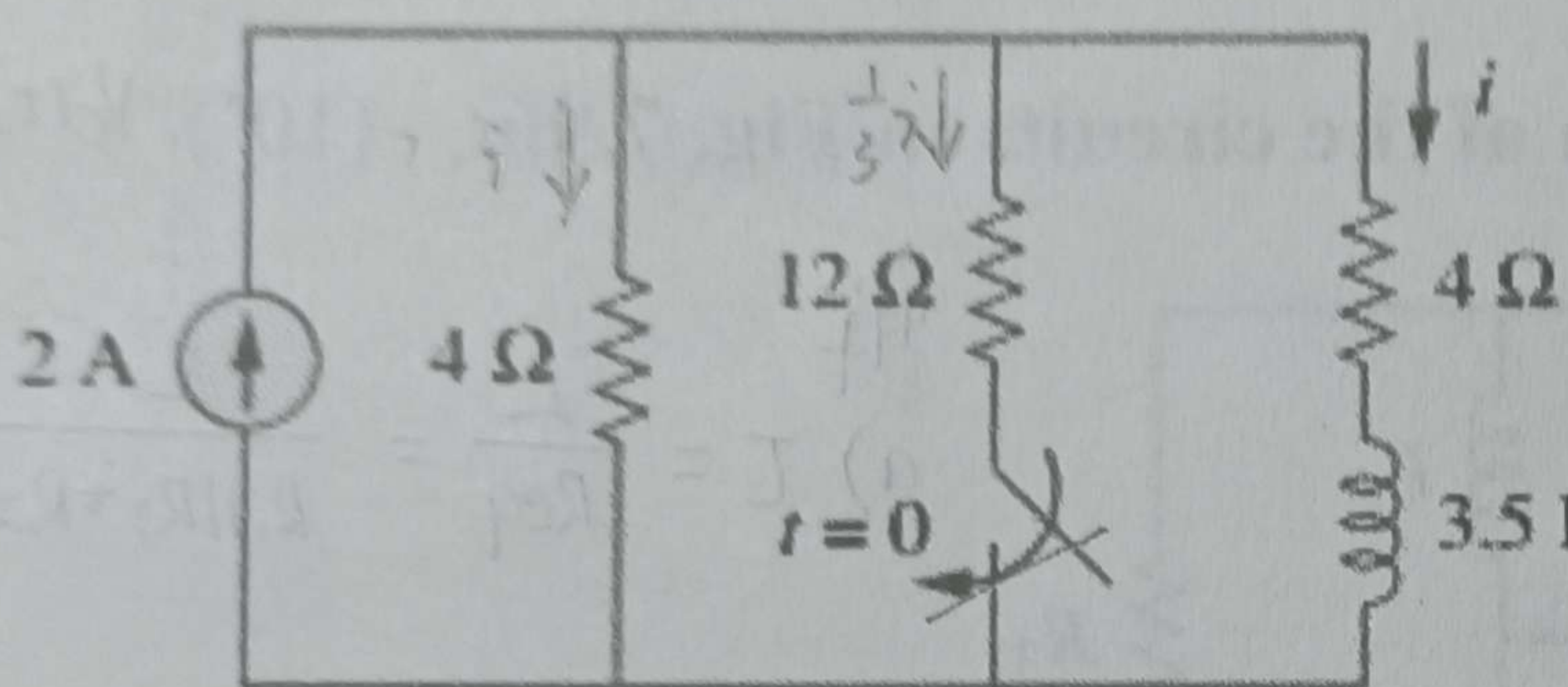7.54 Obtain the (inductor current) for both $t < 0$ and $t > 0$ in each of the circuits in Fig. 7.120. (15')



(a)

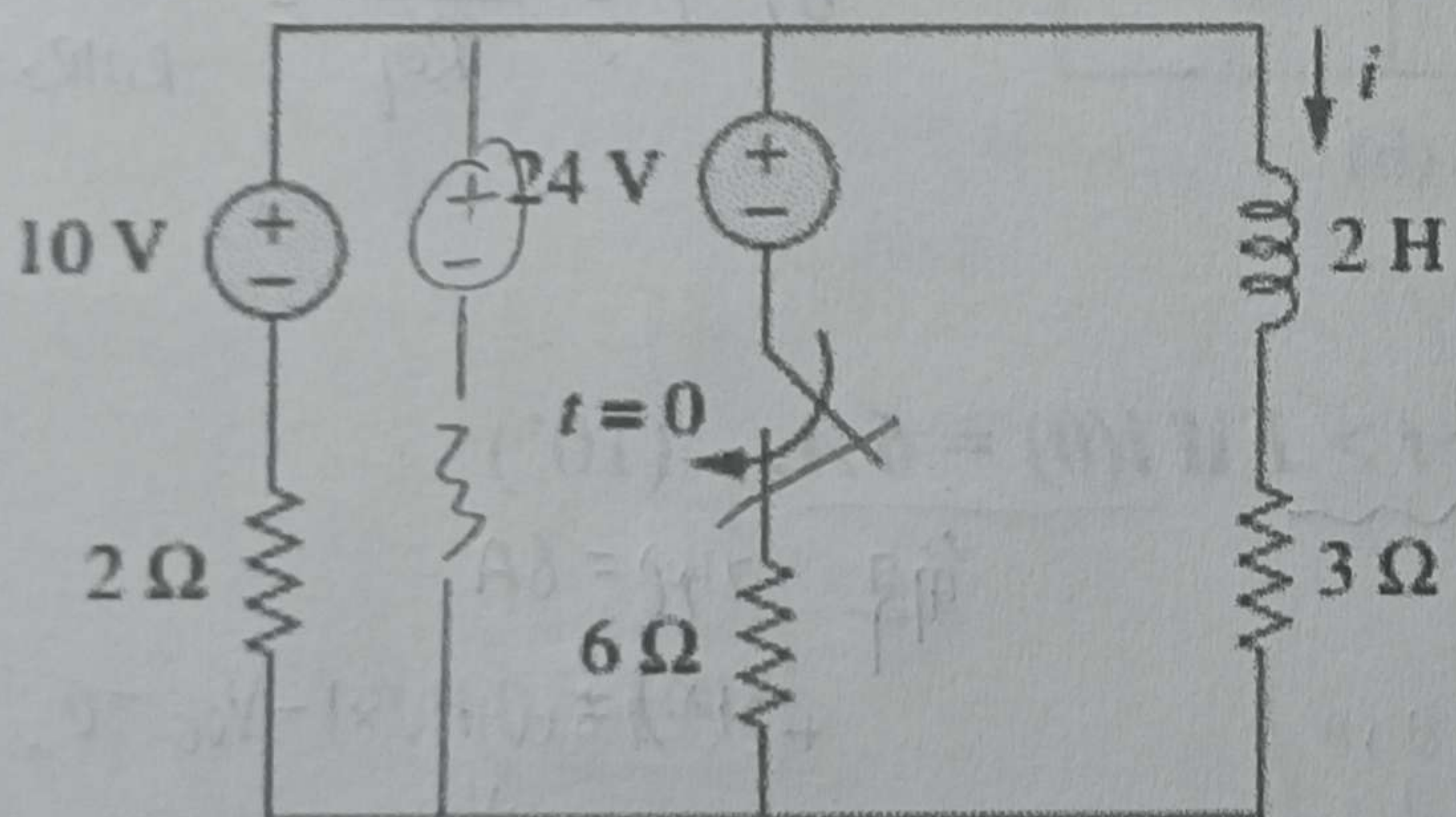

(b)

Figure 7.120

7.57 Find $i_1(t)$ and $i_2(t)$ for $t > 0$ in the circuit of Fig. 7.123. (10')

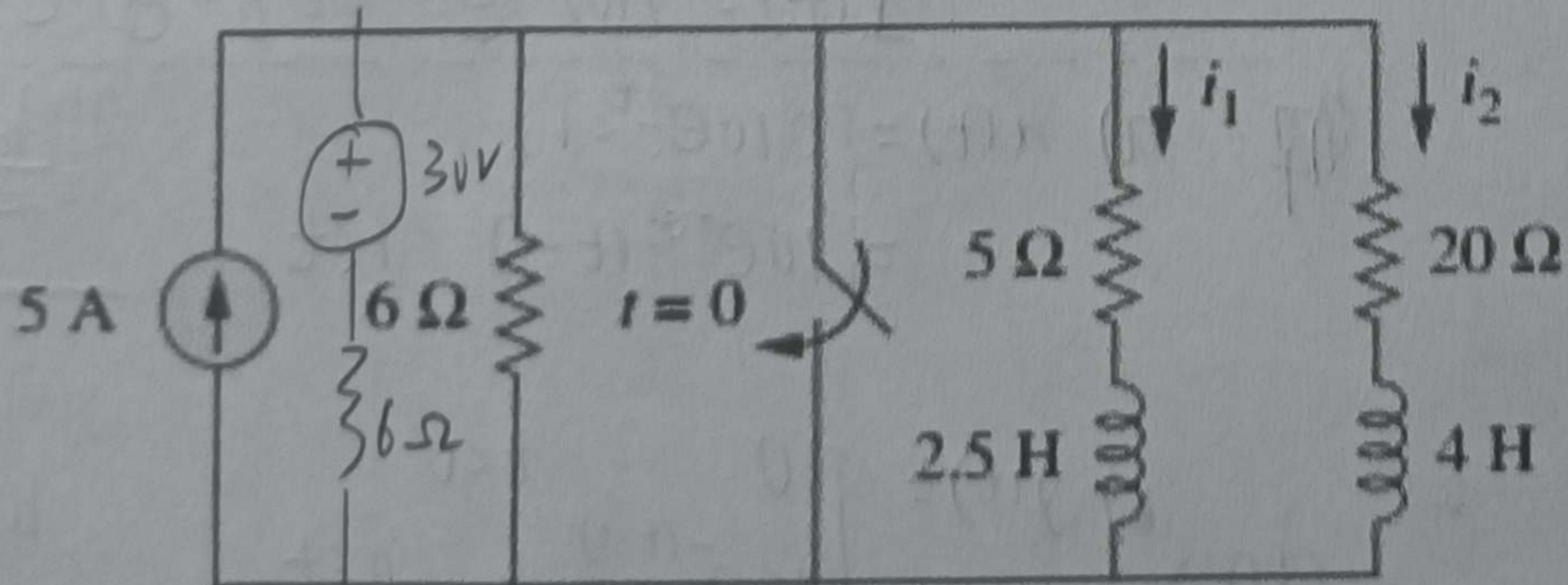


Figure 7.123

7.85 A simple relaxation oscillator circuit is shown in Fig. 7.145. The neon lamp fires when its voltage (reaches 75 V) and turns off when its voltage (drops to 30 V). Its resistance is 120Ω when on and infinitely high when off.

(a) For how long is the lamp on (each time the capacitor discharges)?

(b) What is the time interval between light flashes? (15')

解: $t < 0$,

$$-80 + 40 \times 0.5i + 80i = 0$$

$$i = 0.8A$$

$$V_C = (30 + 50) \times 0.8 = 64V, V_C(0) = 64V$$

$$t > 0, +1 + 0.5i - i = 0, i = 2A$$

$$-V_{OC} + 2 \times 80 = 0, V_{OC} = 160V$$

$$R_{eq} = \frac{V_{OC}}{I} = 160\Omega, \tau = R_{eq} \cdot C = 480$$

$$V(t) = 64e^{-t/480}$$

$$0.5i(t) \cdot R_{eq} = V(t) \\ i(t) = \frac{2 \times 64}{160} e^{-t/480} = 0.8e^{-t/480} A$$

解:

a) $t < 0$,

$$4(i - 2) + 4i = 0, i(0) = 1A$$

$$t > 0, i(\infty) = \frac{6}{7}A$$

$$R_{eq} = 4 + 4 \parallel 12 = 7\Omega$$

$$\tau = \frac{L}{R_{eq}} = 0.5$$

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

$$= \frac{6}{7} + \frac{1}{7}e^{-2t}$$

$$\therefore i(t) = \begin{cases} 1A & t < 0 \\ \frac{6}{7} + \frac{1}{7}e^{-2t} & t > 0 \end{cases} \quad \boxed{\text{Ans}}$$

b) $t < 0, i = \frac{10}{5} = 2A$

$$t > 0, i(\infty) = \frac{(\frac{10}{2} + \frac{24}{6})(2 \parallel 6)}{3 + 2 \parallel 6} = 3A$$

$$R_{eq} = 3 + 2 \parallel 6 = 4.5\Omega, \tau = \frac{L}{R_{eq}} = \frac{2}{4.5} = \frac{4}{9}$$

$$i(t) = 3 + (-1) \cdot e^{-\frac{9t}{4}}$$

$$\therefore i(t) = \begin{cases} 2A & t < 0 \\ 3 - e^{-\frac{9t}{4}} A & t > 0 \end{cases} \quad \boxed{\text{Ans}}$$

$$\text{解: } t < 0, i_1(0) = \frac{30}{6 + 5 \parallel 20} \times \frac{5 \parallel 20}{5} = 2.4A$$

$$i_2(0) = \frac{30}{6 + 5 \parallel 20} \times \frac{5 \parallel 20}{20} = 0.6A$$

$$t > 0, i_1(\infty) = 0 = i_2(\infty)$$

$$\tau_1 = \frac{2.5}{5} = 0.5, \tau_2 = \frac{4}{20} = 0.2$$

$$i_1(t) = i_1(\infty) + [i_1(0) - i_1(\infty)]e^{-t/\tau_1}$$

$$= 2.4e^{-2t} \quad (t > 0)$$

$$i_2(t) = i_2(\infty) + [i_2(0) - i_2(\infty)]e^{-t/\tau_2}$$

$$= 0.6e^{-5t} \quad (t > 0)$$


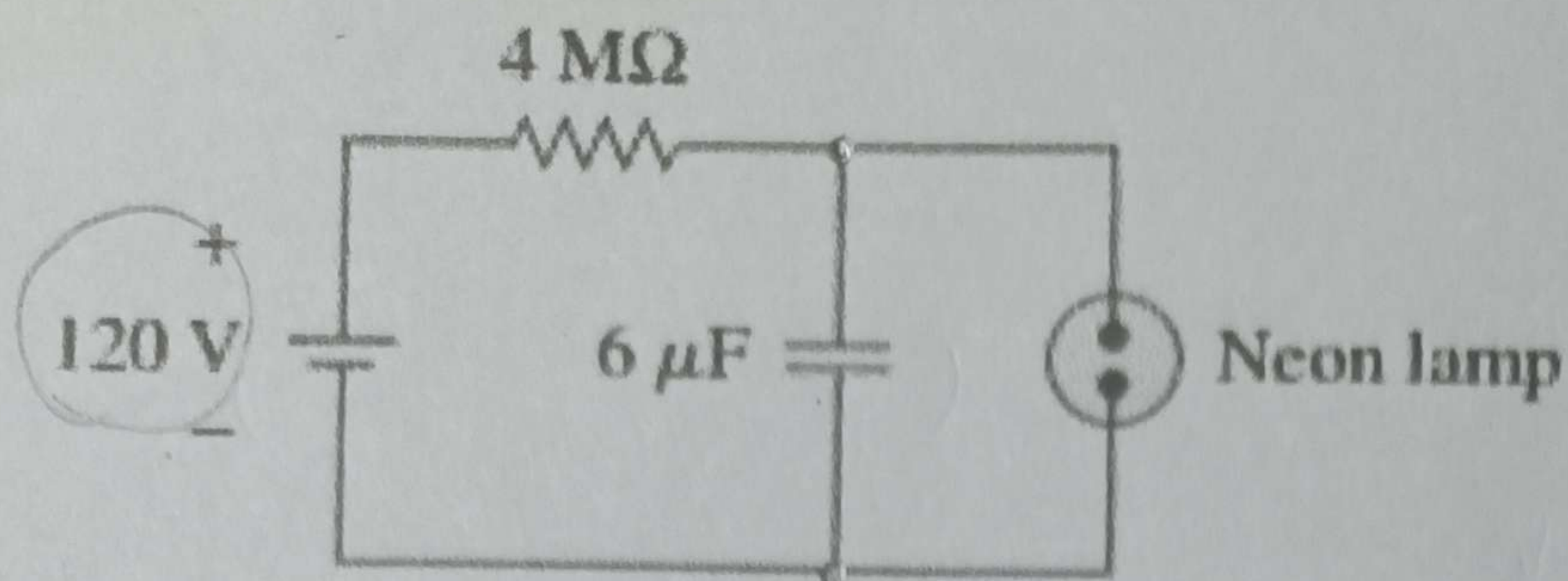


Figure 7.145

解: a) the lamp on

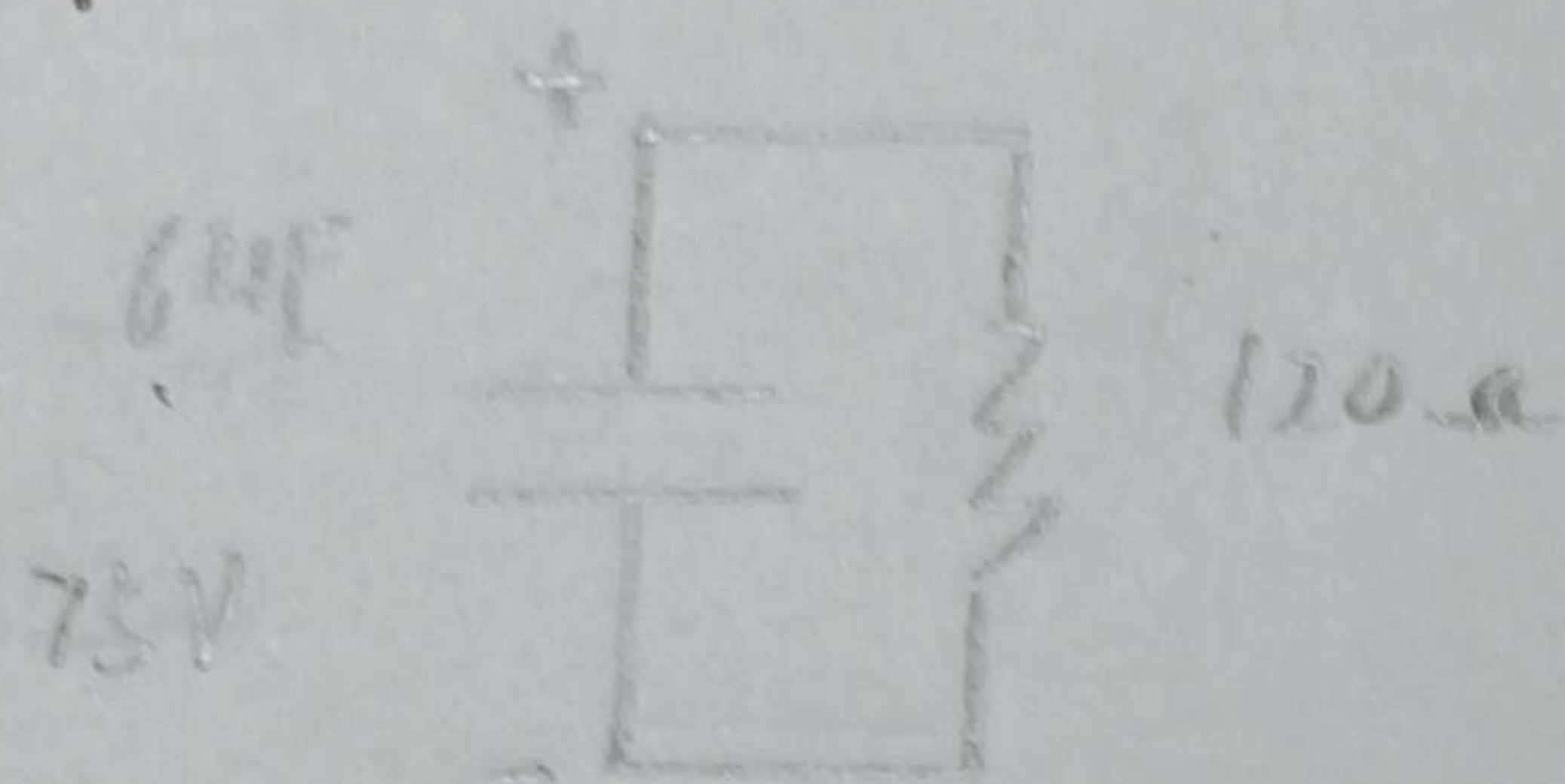


$$\tau = RC = 120 \times 6 \times 10^{-6} = 7.2 \times 10^{-4}$$

$$v(t) = 75 e^{\frac{-t}{7.2 \times 10^{-4}}} \text{ V}$$

$$75 e^{\frac{-t}{7.2 \times 10^{-4}}} = 30$$

$$t = 6.597 \times 10^{-4} \text{ s}$$

b)

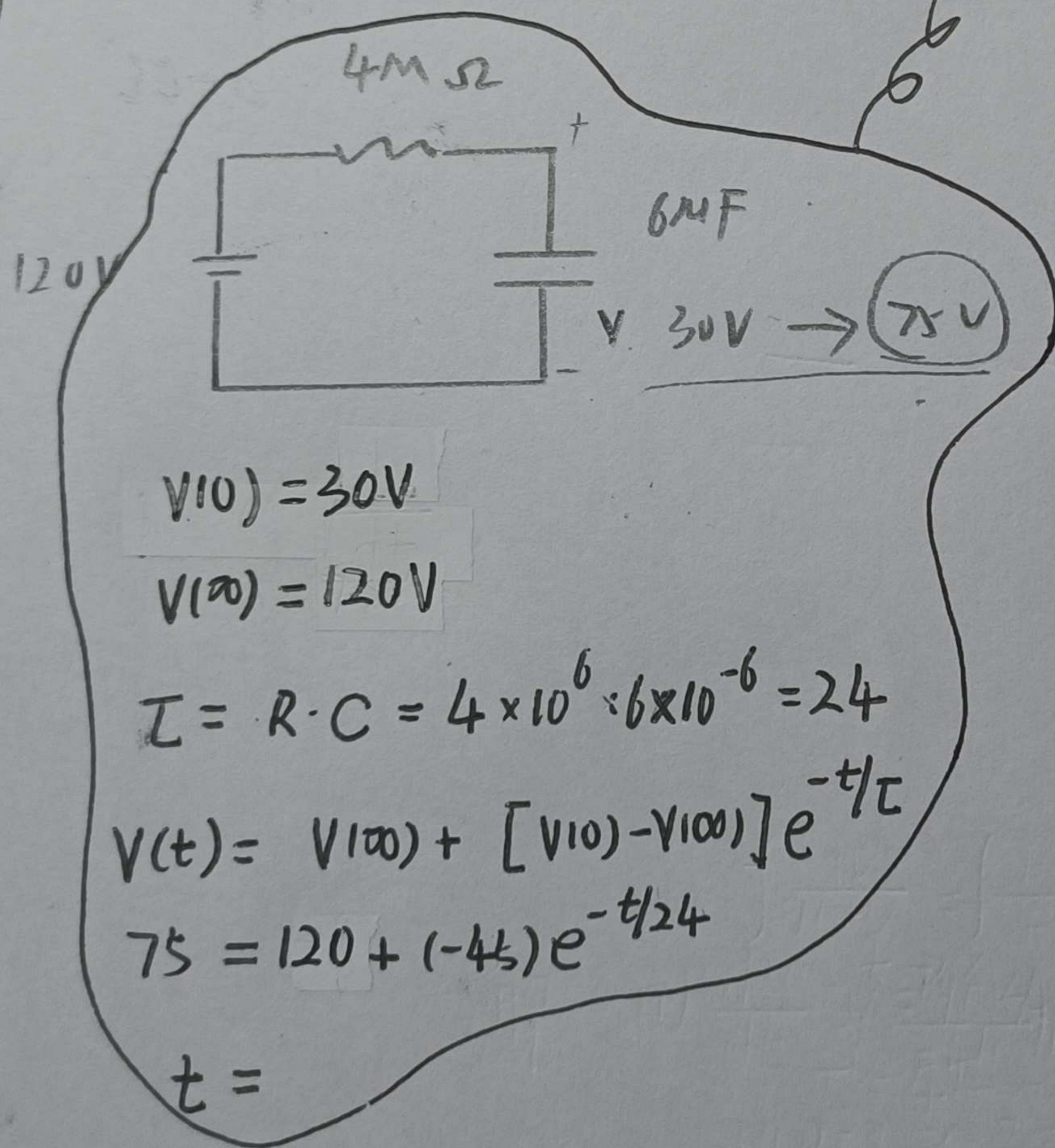

$$V_C(t) = V_C(\infty) + [V_C(0) - V_C(\infty)] e^{-t/\tau}$$

At t_1 , the lamp off
 t_2 on

$$\text{find } T = t_2 - t_1$$

$$V_C(t_1) = 30 \text{ V}, V_C(t_2) = 75 \text{ V}$$

$$V_C(\infty) = 120 \text{ V}$$

$$V_C(t_1) = V_C(\infty) + [V_C(0) - V_C(\infty)] e^{-t_1/\tau}$$

$$V_C(t_2) = V_C(\infty) + [V_C(0) - V_C(\infty)] e^{-t_2/\tau}$$

$$\frac{30 - 120}{75 - 120} = \frac{e^{-t_1/24}}{e^{-t_2/24}} = e^{\frac{1}{24}(t_2 - t_1)}$$

$$\frac{1}{24}(t_2 - t_1) = \ln \frac{90}{45}$$

$$T = 24 \ln 2 = 16.64 \text{ s}$$