

《Fundamentals of Electric Circuits》 homework CH.10&11

10.7 Use (nodal analysis) to find \underline{V} in the circuit of Fig. 10.56. (10')

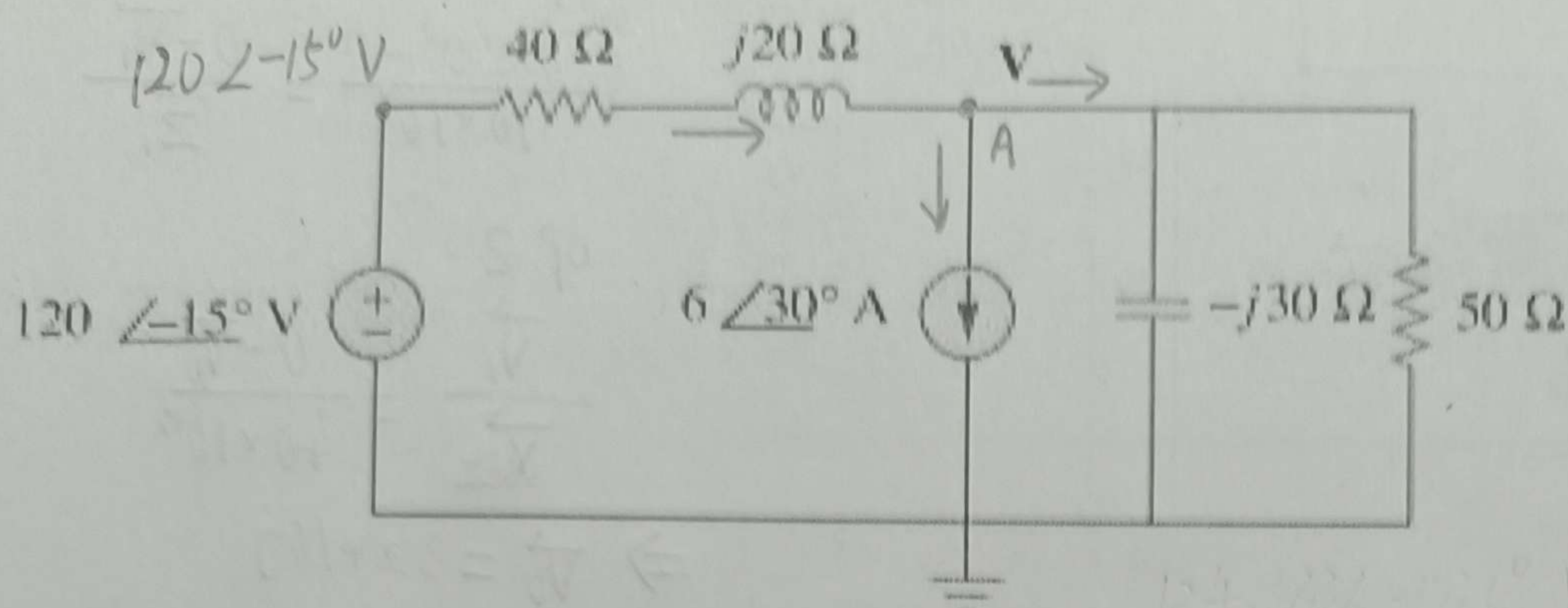


Figure 10.56

node A:

$$\frac{120\angle-15^\circ - \underline{V}}{40 + j20} = \frac{\underline{V}}{-j30} + \frac{\underline{V}}{50} + 6\angle30^\circ$$

$$\Rightarrow \left(\frac{1}{50} - \frac{1}{30j} + \frac{1}{40 + j20}\right)\underline{V} = 6\angle30^\circ + \frac{120\angle-15^\circ}{40 + j20}$$

$$\underline{V} = -11.5 - 54.47j$$

ANS

10.28 In the circuit of Fig. 10.76, determine the mesh currents i_1 and i_2 . (10')

Let $v_1 = 10 \cos 4t$ V and $v_2 = 20 \cos(4t - 30^\circ)$ V.

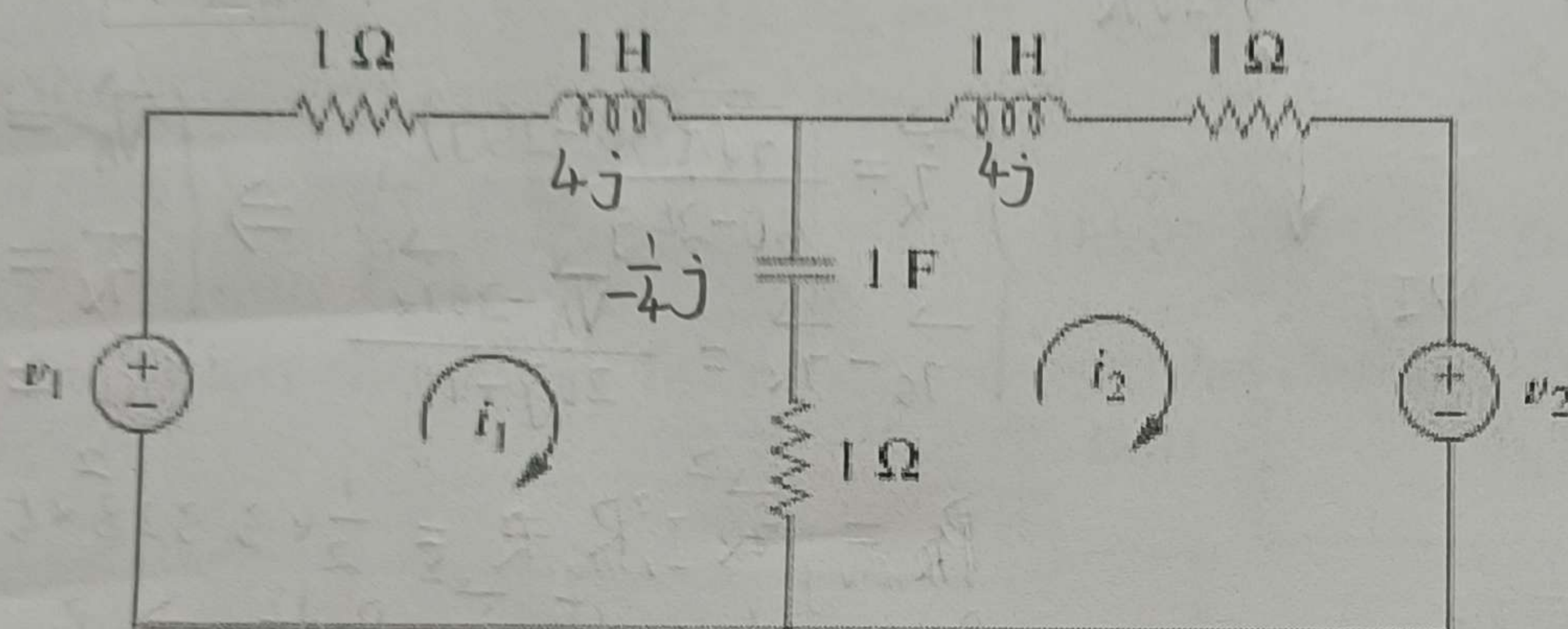


Figure 10.76

解: $\omega = 4$

$$\underline{V}_1 = 10\angle0^\circ \text{ V}, \underline{V}_2 = 20\angle-30^\circ \text{ V}$$

$$\frac{1}{j\omega C} = \frac{1}{j4 \times 1} = -\frac{1}{4}j$$

$$j\omega L = j4 \cdot 1 = 4j$$

mesh ①: $-10\angle0^\circ + \underline{i}_1(1 + 4j) + (-\frac{1}{4}j + 1)(\underline{i}_1 - \underline{i}_2) = 0$

mesh ②: $20\angle-30^\circ + (1 - \frac{1}{4}j)(\underline{i}_2 - \underline{i}_1) + \underline{i}_2(4j + 1) = 0$

$$\Rightarrow \underline{i}_1 = 2.067 - 1.800j, \underline{i}_2 = -0.1438 + 4.112j$$

10.45 Use (superposition) to find $i(t)$ in the circuit of Fig. 10.90. (10')

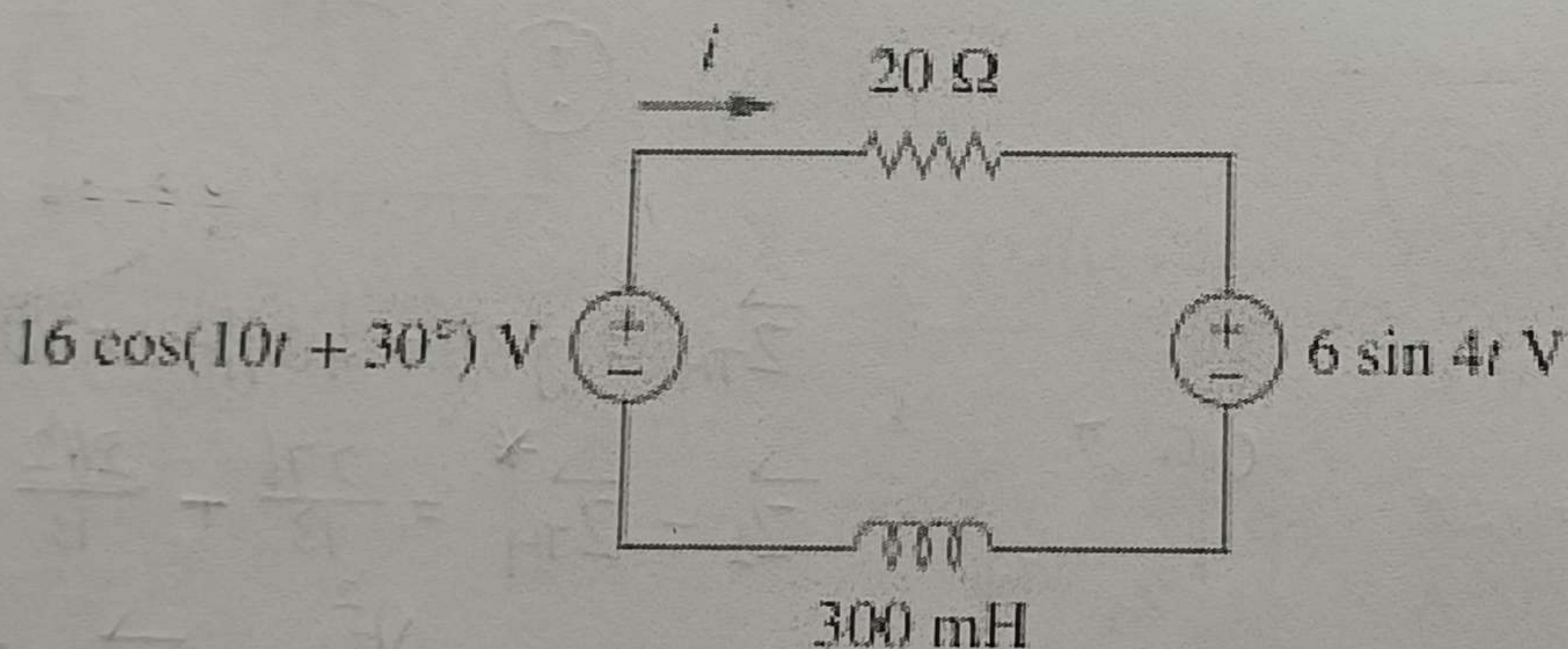


Figure 10.90

解:

① $\underline{V}_1 = 16\angle30^\circ \text{ V}, \omega_1 = 10$

$$j\omega L = j10 \times 300 \times 10^{-3} = 3j$$

$$\underline{i}_1 = \frac{16\angle30^\circ}{3j + 20} = 0.7363 + 0.2896j$$

$$\underline{i}_1(t) = 0.7912 \cos(10t + 21.47^\circ)$$

② $\underline{V}_2 = 6\angle-90^\circ \text{ V}, \omega_2 = 4$

$$j\omega L = j4 \times 300 \times 10^{-3} = 1.2j$$

$$\underline{i}_2 = \frac{6\angle-90^\circ}{1.2j + 20} = -0.01794 - 0.2994j$$

$$\underline{i}_2(t) = 0.2994 \cos(10t + 86.57^\circ)$$

$$\therefore \underline{i}(t) = \underline{i}_1(t) + \underline{i}_2(t) = 0.7912 \cos(10t + 21.47^\circ) + 0.2994 \cos(10t + 86.57^\circ)$$

ANS

10.66 At terminals a-b, obtain Thevenin and Norton equivalent circuits for the network depicted in Fig. 10.109. Take $\omega = 10$ rad/s. (10')

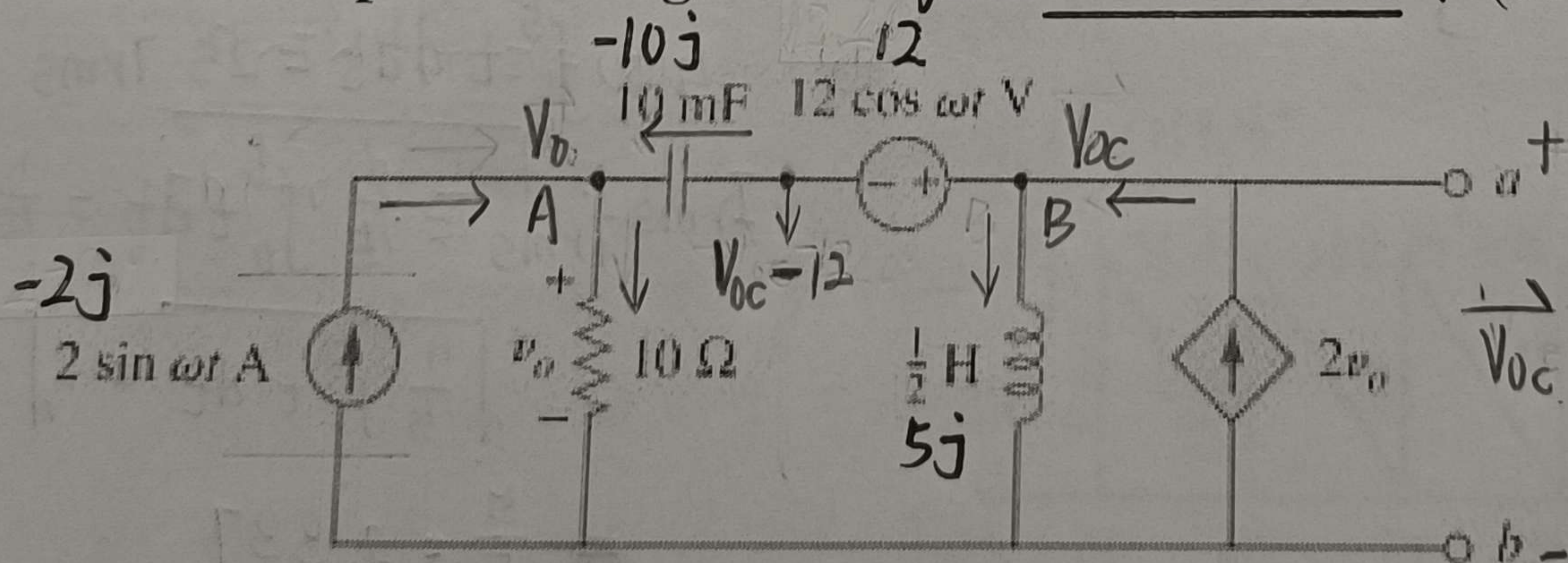


Figure 10.109

解:

$$\frac{1}{j\omega C} = \frac{1}{j \times 10 \times 10 \times 10^{-3}} = -10j$$

$$j\omega L = j \times 10 \times \frac{1}{2} = 5j$$


node A: $-2j + \frac{\underline{V}_{0c} - 12 - \underline{V}_0}{-10j} = \frac{\underline{V}_0}{10}$

(super) node B: $+2\underline{V}_0 = \frac{\underline{V}_{0c} - 12 - \underline{V}_0}{-10j} + \frac{\underline{V}_{0c}}{5j}$

$$\Rightarrow \underline{V}_{0c} = -29.90 - 2.095j$$

ANS

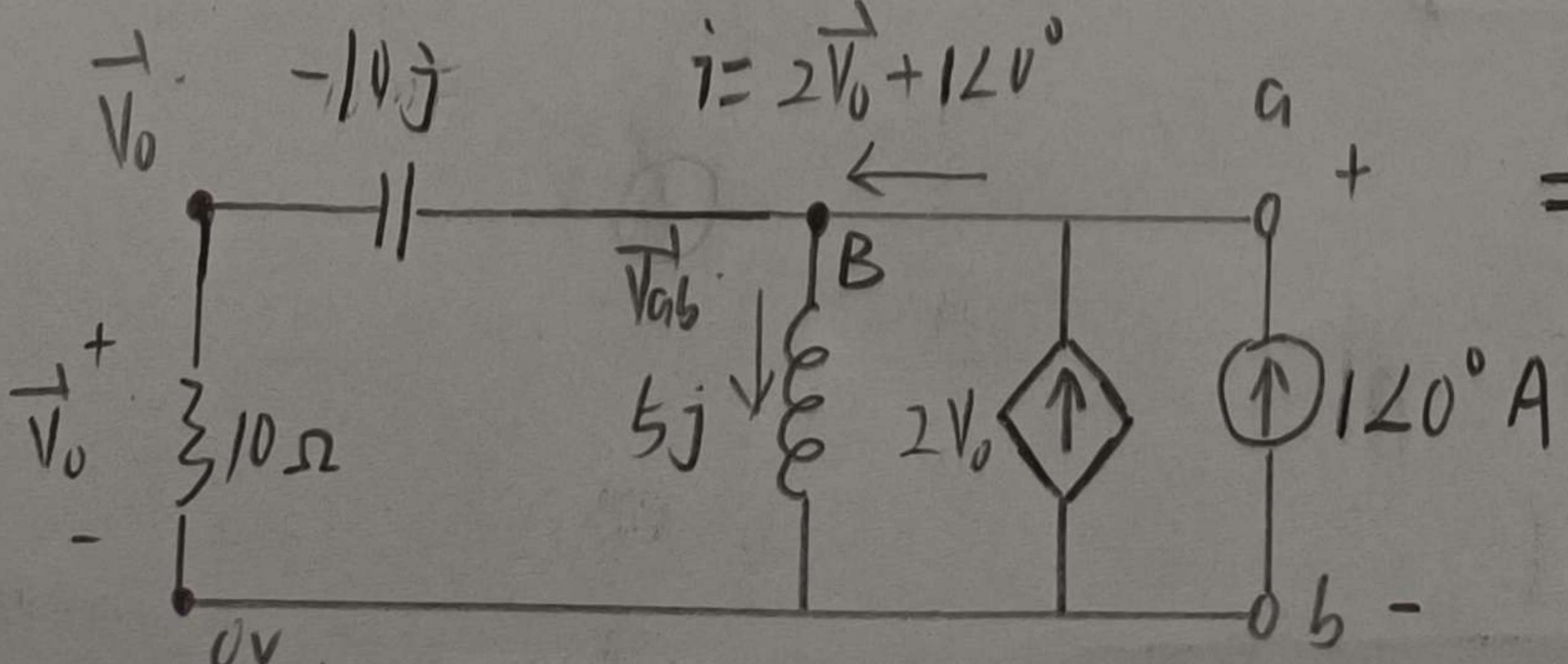10.79 For the op amp circuit in Fig. 10.122, obtain $v_o(t)$.



node B: $+2\underline{V}_0 + 120^\circ = \frac{\underline{V}_{ab} - \underline{V}_0}{-10j} + \frac{\underline{V}_{ab}}{5j}$

后接

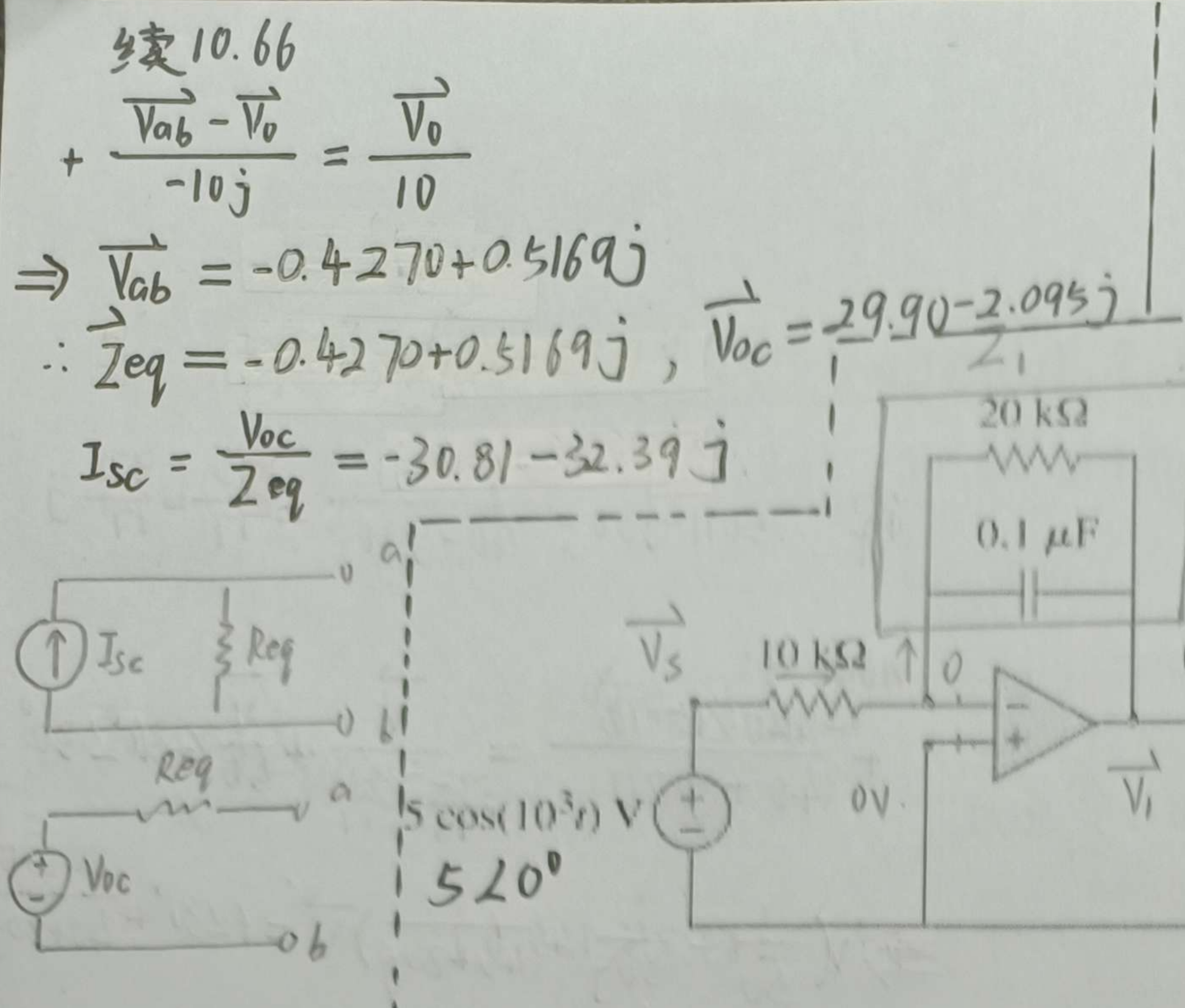


Figure 10.122

11.6 For the circuit in Fig. 11.38 $[i_s = 6 \cos 10^3 t A]$ Find the average power absorbed by the 50Ω resistor. (10')

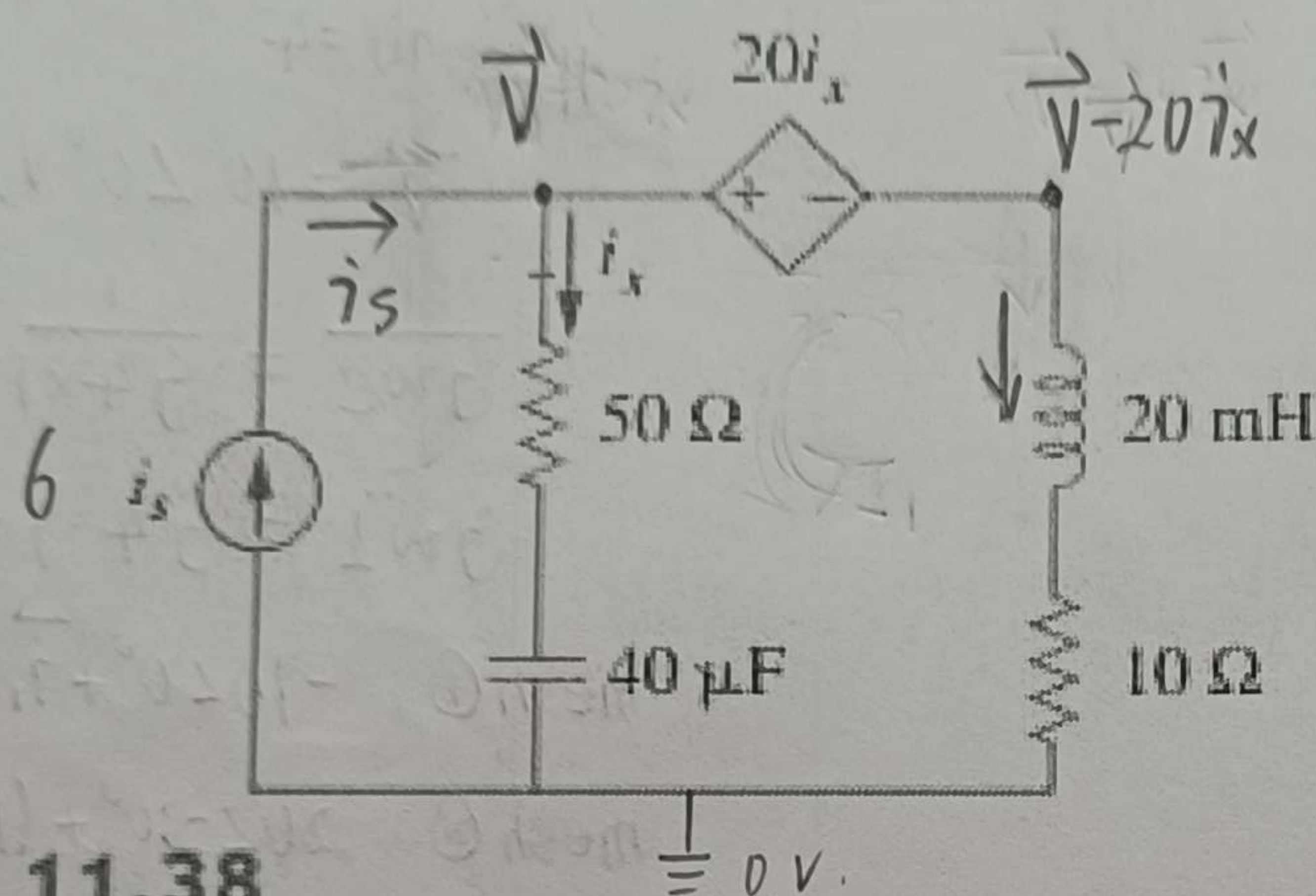


Figure 11.38

11.18 Find the value of Z_L in the circuit of Fig. 11.49 for maximum power transfer. (10')

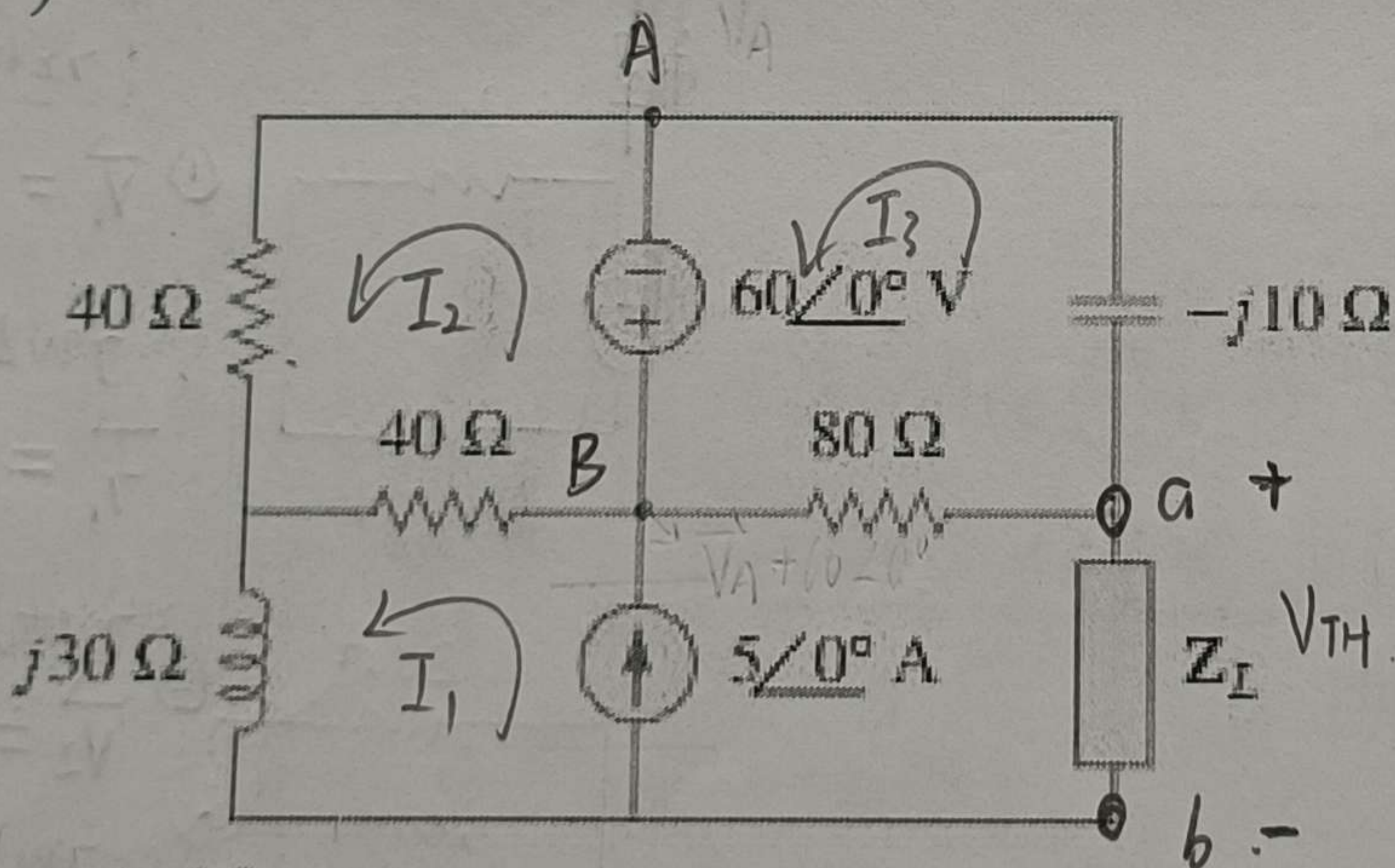


Figure 11.49

11.27 Calculate the [rms value] of the current waveform of Fig. 11.58. (10')

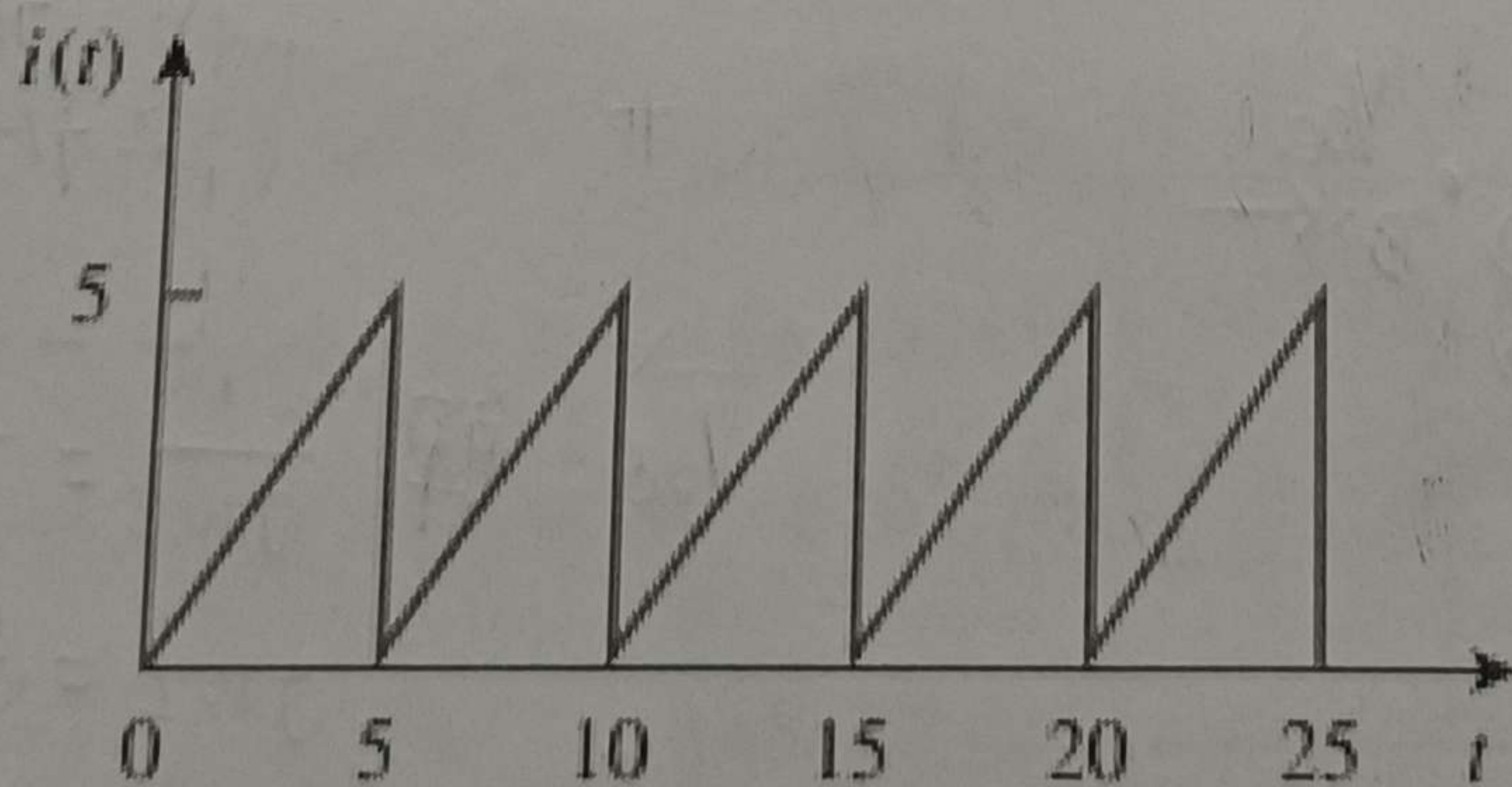


Figure 11.58

11.41 Obtain the (power factor) for each of the circuits in Fig. 11.68. Specify each power

10.79 解: $\omega = 10^3$

$$\vec{X}_{C1} = \frac{1}{j\omega C_1} = \frac{1}{j \times 10^3 \times 0.1 \times 10^{-6}} = -10^4 j$$

$$\vec{X}_{C2} = \frac{1}{j\omega C_2} = \frac{1}{j \times 10^3 \times 0.2 \times 10^{-6}} = -5 \times 10^3 j$$

$$\vec{Z}_1 = 20 \times 10^3 \parallel -10^4 j = \frac{-2 \times 10^8 j}{2 \times 10^4 - 10^4 j} = 4000 - 8000j$$

op 1:

$$\frac{5 \angle 0^\circ - 0}{10 \times 10^3} = \frac{0 - \vec{V}_1}{\vec{Z}_1}$$

op 2:

$$\frac{\vec{V}_1}{\vec{X}_{C2}} = \frac{0 - \vec{V}_0}{40 \times 10^3}$$

$$\Rightarrow \vec{V}_0 = 32 + 16j$$

$$V_0(t) = 35.78 \cos(10^3 t + 26.57^\circ) V$$

解: $\omega = 10^3$


$$\vec{X}_C = \frac{1}{j\omega C} = \frac{1}{j \times 10^3 \times 40 \times 10^{-6}} = -25j$$

$$\vec{i}_s = 6 \angle 0^\circ, \vec{X}_L = j\omega L = j \times 10^3 \times 20 \times 10^{-3} = 20j$$

$$\begin{cases} \vec{i}_x = \frac{\vec{V}}{50 - 25j} \\ \vec{i}_s - \vec{i}_x = \frac{\vec{V} - 20j\vec{i}_x}{20j + 10} \end{cases} \Rightarrow \vec{i}_x = 1.108 + 3.138j$$

$$= 3.328 \cos(10^3 t + 70.55^\circ)$$
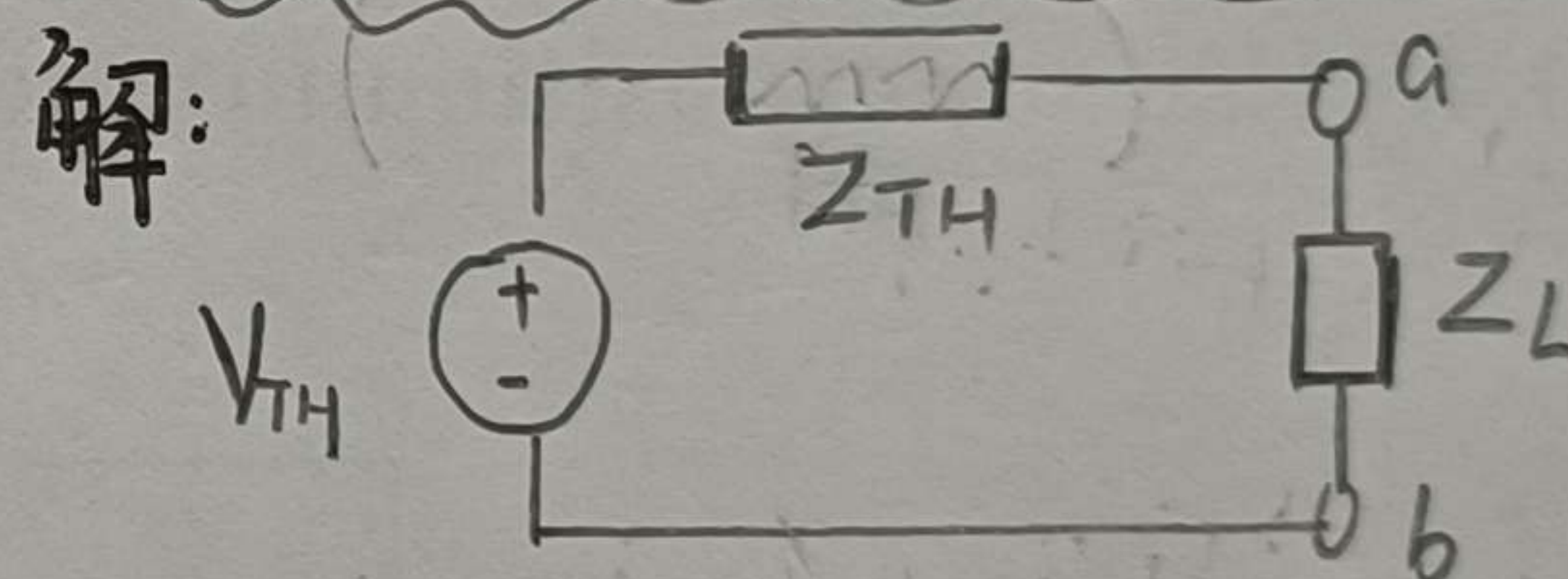
$$P_{R,avg} = I_{rms}^2 R = \frac{1}{2} \times 3.328^2 \times 50 = 276.9 W$$



$$\vec{Z}_{TH} = j30 + 40 \parallel 40 + 80 \parallel -j10 = \frac{276}{13} + \frac{262}{13}j$$

$$\vec{Z}_L = \vec{Z}_{TH}^* = \frac{276}{13} - \frac{262}{13}j \text{ 时}$$

$$P_{L,max} = \frac{V_{TH}^2}{8R_{TH}}, \vec{Z}_L = 21.23 - 20.15j$$


解: $i(t) = t \quad 0 < t < 5$

$$I_{rms} = \sqrt{\frac{1}{5} \int_0^5 i^2(t) dt}$$


$$= \sqrt{\frac{1}{5} \int_0^5 t^2 dt} = \sqrt{\frac{1}{5} \times \frac{1}{3} \times 5^3}$$

$$= \frac{5}{\sqrt{3}} = 2.887$$

factor as [leading or lagging.] (10')

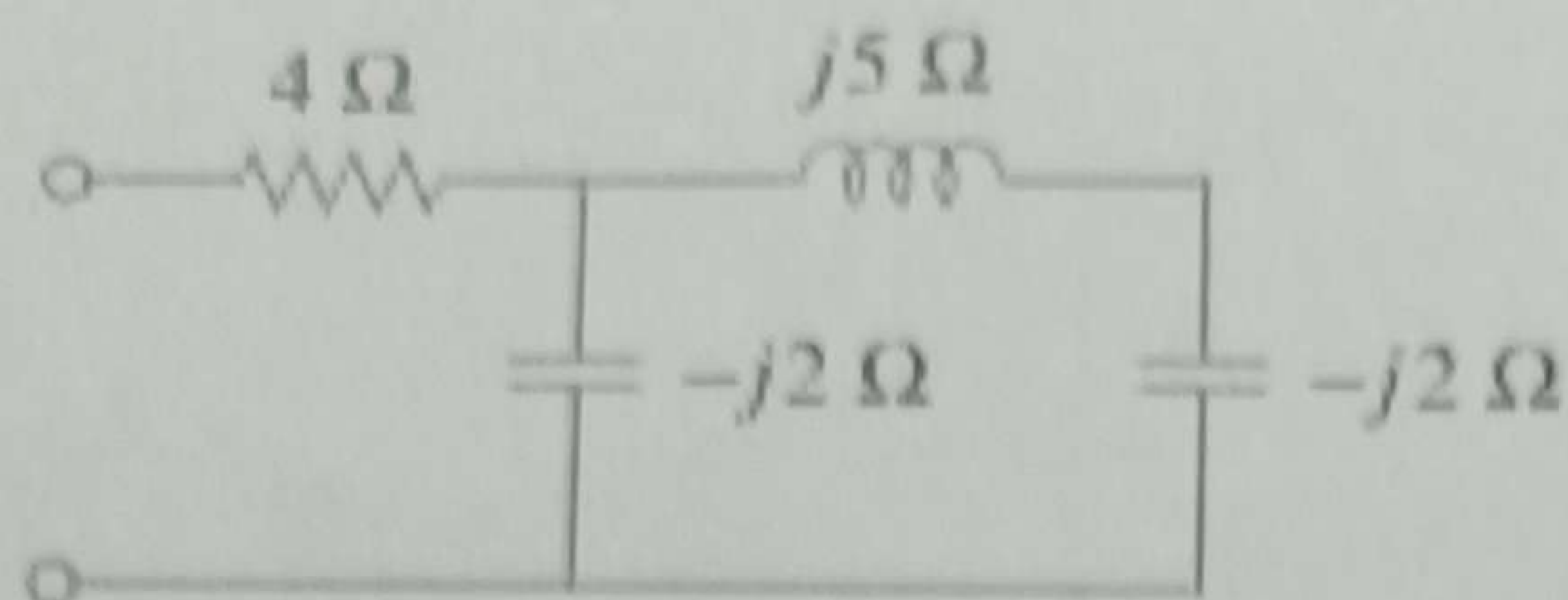

(a)

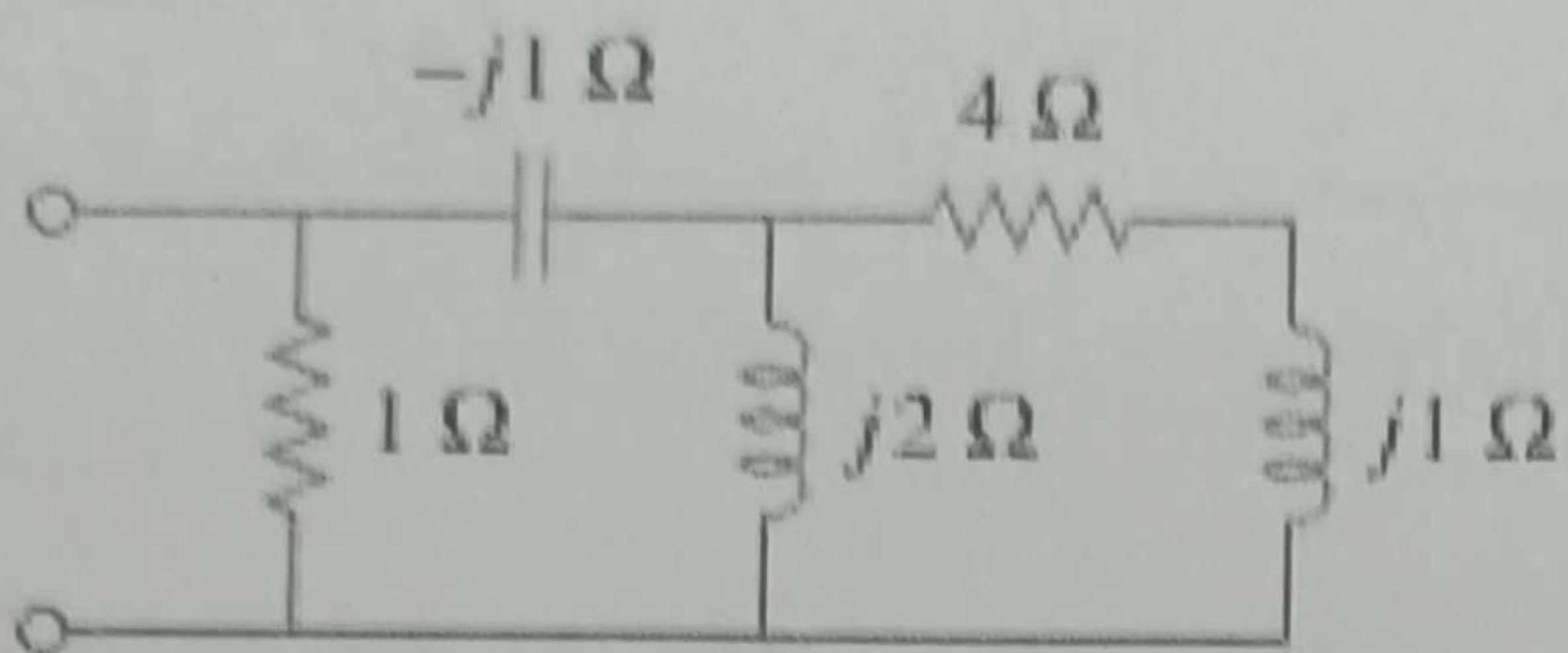

(b)

$$\text{解: a) } \underline{Z} = 4 + (5j - 2j) \parallel -2j$$

$$= 4 - 6j$$

$$= \sqrt{16+36} \angle -56.31^\circ$$

$$\text{pf} = \cos(-56.31^\circ) = 0.5547, \text{ leading pf}$$

$$\text{b) } \underline{Z} = [(4+j) \parallel 2j - j] \parallel 1$$

$$= \frac{33}{74} + \frac{13}{74}j$$

$$= \sqrt{\left(\frac{33}{74}\right)^2 + \left(\frac{13}{74}\right)^2} \angle 21.50^\circ$$

$$\text{pf} = \cos(21.50^\circ) = 0.9304, \text{ lagging pf}$$

Figure 11.68

11.53 In the circuit of Fig. 11.72, load A receives 4 kVA at 0.8 pf leading. Load B receives 2.4 kVA at 0.6 pf lagging. Box C is an inductive load that consumes 1 kW and receives 500 VAR.

(a) Determine I.

(b) Calculate the power factor of the combination. (10')

$$\underline{S}_C = 1000 + 500j = \frac{1}{2} \underline{V}_C \cdot \underline{I}_C^*$$

$$\underline{S} = P + jQ$$

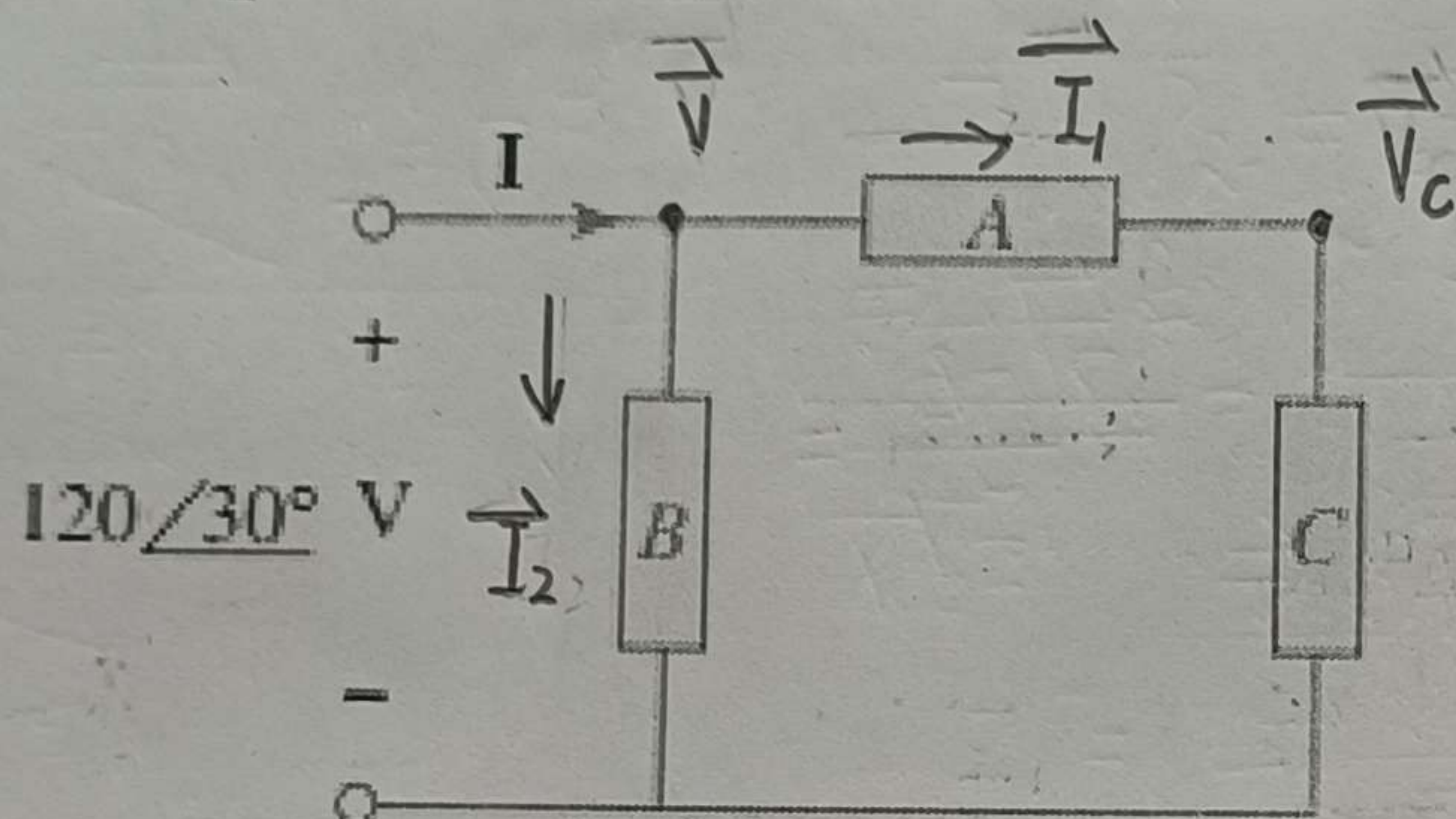


Figure 11.72

$$\text{解: a) } \underline{S}_A = \frac{1}{2} (\underline{V} - \underline{V}_C) \underline{I}_1^* = \frac{1}{2} 120 \underline{I}_1 \angle 30^\circ - \phi_1 - (1000 + 500j) = 4000 \angle -\cos^{-1} 0.8 = 3200 - 2400j$$

$$\underline{S}_B = \frac{1}{2} \underline{V} \cdot \underline{I}_2^* = \frac{1}{2} 120 \underline{I}_2 \angle 30^\circ - \phi_2 = 60 \underline{I}_2 \angle 30^\circ - \phi_2 = 2400 \angle \cos^{-1} 0.6 = 1440 + 1920j$$

$$\underline{S}_C = \frac{1}{2} \underline{V}_C \underline{I}_1^* = 1000 + 500j$$

$$\Rightarrow I_2 = 40 \quad I_1 = 76.83$$

$$\phi_2 = -23.13^\circ \quad \phi_1 = +54.34^\circ$$

$$\underline{I}_2 = 40 \angle -23.13^\circ \quad \underline{I}_1 = 76.83 \angle +54.34^\circ$$

$$\underline{I} = 40 \cos(23.13^\circ) - 40 \sin(23.13^\circ)j + 76.83 \cos(54.34^\circ) + 76.83 \sin(54.34^\circ)j$$

$$= 81.57 + 46.71j = 94.00 \angle 29.80^\circ \text{ A}$$

$$\text{b) } \underline{Z} = \frac{\underline{V}}{\underline{I}} = \frac{V_m}{I_m} \angle 30^\circ - 29.80^\circ$$

$$\text{pf} = \cos 0.2^\circ = 1 \quad \text{lagging pf}$$